
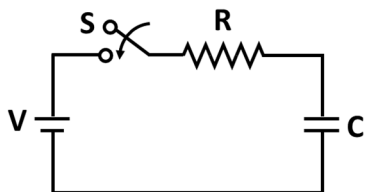


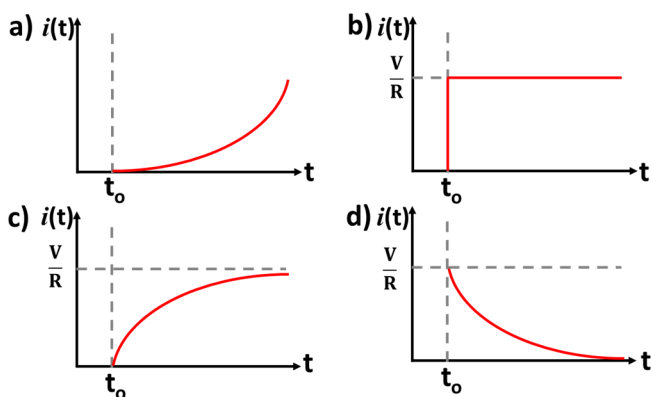1. Consider the following circuit which was open until time $t = t_0$, at time t_0 the switch was closed. Which of the following best represents the current $[i(t)]$ through the circuit?




Options:



Ans: d


2. The RC circuit in the figure is a:

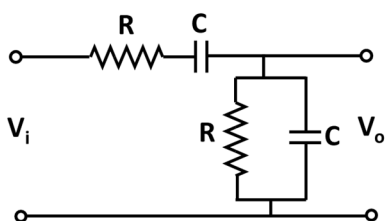
- a) High-pass filter
- b) Low-pass filter
- c) Band-pass filter
- d) Band-reject filter



Ans: c

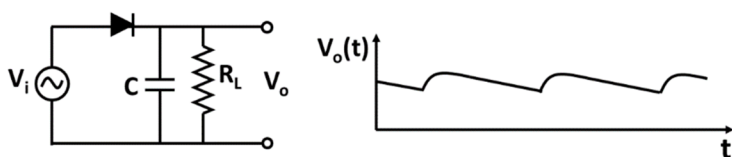3. Consider the half-wave rectifier circuit with a capacitor filter. Its output waveform is also shown in the figure. Which of the following waveforms approximately represents the current through the diode?



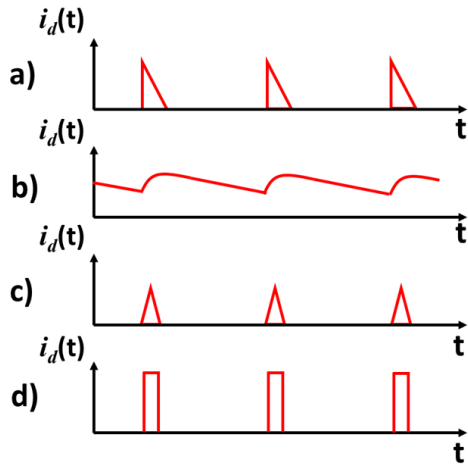


Ans: a

4. For the circuit shown below, the input (V_i) is a square wave. What will be the output (V_o)?

Each symbol represents their usual meaning.

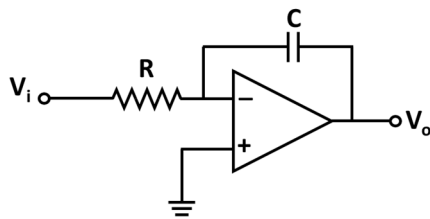
- a) sinusoidal wave
- b) train of pulses
- c) triangular wave
- d) ramp.



Ans: c


5. Consider an npn silicon transistor in CE-configuration. If the input port of the circuit is connected to the supply as shown in figure, approximately what would be the output voltage (V_o)?

- a) 0.2 V
- b) 5 V
- c) 1 V
- d) 2.5 V

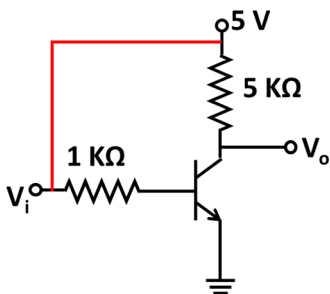


Ans: a

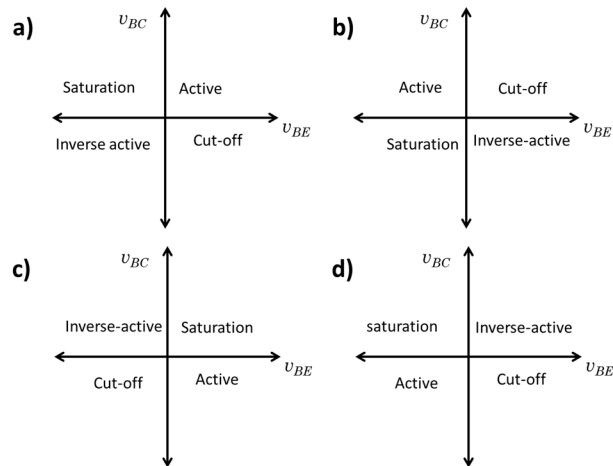6. Which one is the correct set of biasing conditions for the four modes of operation of an **npn** BJT?



Ans: c

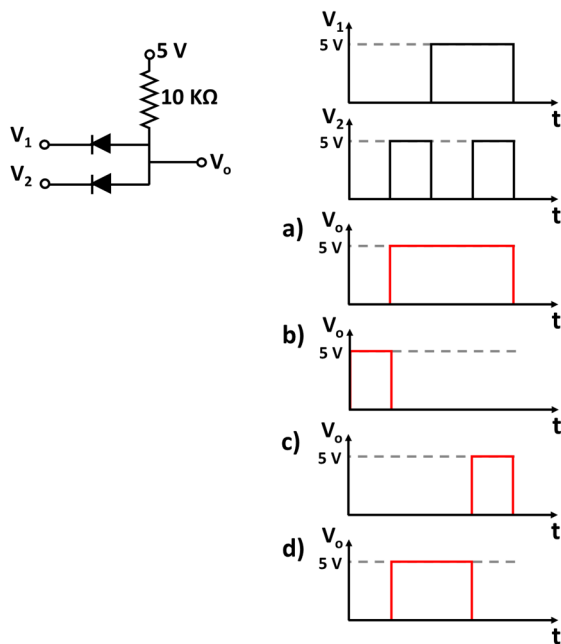7. Consider the following circuit consisting of ideal diodes, the input waveforms V_1 and V_2 are shown. Which of the following waveforms nearly represents the output voltage?



Ans. c

8. A 100 nF capacitor in parallel with 10 nF produces resultant capacitance of:

- a) 9 nF b) 100 nF c) 110 nF d) Cannot be determined

Ans: c

9. To measure current through a resistor in a circuit the multimeter is connected:

- a) in series with resistor b) in parallel with the resistor
- c) either in series or in parallel d) none of the above

Ans: a

10. In a RC circuit with $R=1\text{ k}\Omega$ and $C = 4.7\text{ }\mu\text{F}$, the time constant of the circuit is

- (a) 3.75 ms (b) 4.7ms (c) 4.7 μs (d) 10.3 ms

Ans: b

11. An ideal Operational Amplifier has

- (a) Infinite output impedance (b) Zero input impedance
- (c) Infinite bandwidth (d) All of the above


Ans. c

12. Cathode ray oscilloscope (CRO) displays graph of waveforms based on A and the amplitude of waveforms represents the B value.

- (a) A: current; B: peak to peak (b) A: current; B: RMS
- (c) A: voltage; B: average value (d) A: voltage; B: peak to peak value

Ans. d

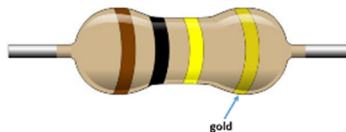13. The resistance value of the resistor shown in figure is



- (a) 110 $\text{k}\Omega$ (b) 10 $\text{k}\Omega$ (c) 100 $\text{k}\Omega$ (d) 1000 $\text{k}\Omega$

Ans. c

14. In a series RC circuit, the output voltage is taken across the resistor. The circuit acts as _____ filter.

- (a) low pass (b) high pass
- (c) band pass (d) band reject

Ans. b


15. The capacitance value of the capacitor shown in figure is



- (a) 10 nF (b) 100 nF (c) 10000 nF (d) 104 pF

Ans. b

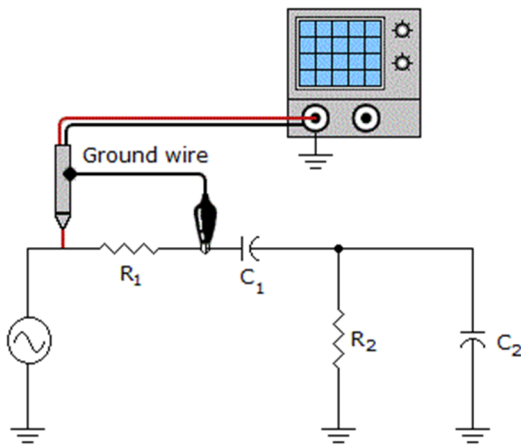16. Connecting the oscilloscope as shown in the given figure will ____.



- (a) measure the voltage across the source (b) measure the voltage across C_1 , R_2 , and C_2
(c) short R_1 (d) short C_1 , R_2 , and C_2


Ans. d

17. When checking a diode using a multimeter, the low resistance readings in both ways indicate that it is

- (a) Zener diode (b) photodiode (c) faulty diode (d) working just fine

Ans. c

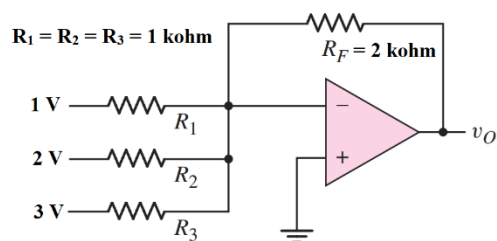
18. The output of the circuit shown below is



- (a) -6 V
- (b) $+6\text{ V}$
- (c) $+12\text{ V}$
- (d) -12 V

Ans: d

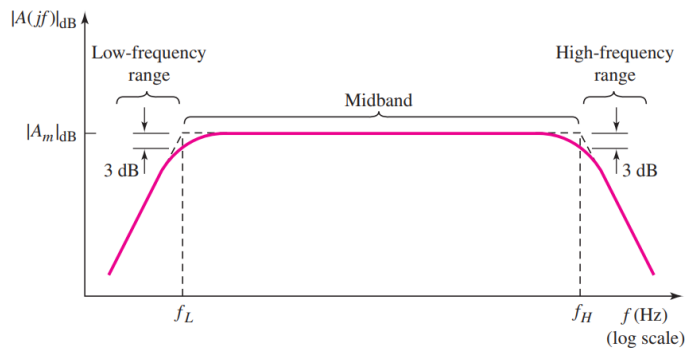19. Following figure shows the gain vs frequency response of a CE amplifier. Decrease in gain in the low frequency region is due to A and the same in the high frequency region is due to B.




- (a) A: coupling and bypass capacitors; B: stray capacitance and transistor capacitances
- (b) A: stray capacitance and transistor capacitances; B: coupling and bypass capacitors
- (c) A: coupling capacitors; B: bypass capacitors
- (d) A: bypass capacitors; B: coupling capacitors

Ans: a

20. For the following common emitter circuit estimate the V_{CE} .


Consider, $\beta = 200$ and $V_{BE(on)} = 0.7\text{ V}$.

- (a) 10 V
- (b) 4 V
- (c) 0
- (d) 6.5 V

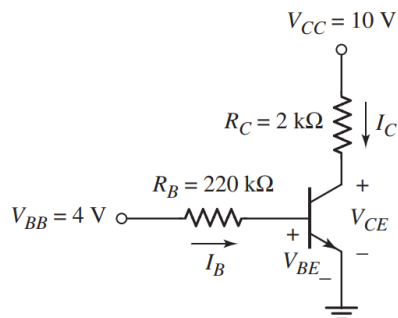

Ans: b

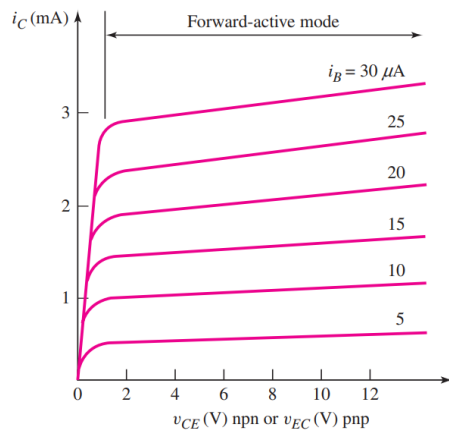
21. Following figure shows the output characteristics of a BJT operating in CE mode. The gradual increase in collector (i_c) in the active region is due to A and the current gain is \approx B .







- (a) A: Decrease in neutral base width; B: 100
 (b) A: Increase in neutral base width; B: 200
 (c) A: Heating of transistors; B: 10
 (d) A: Early effect and self-heating; B: cannot be estimated

Ans. a

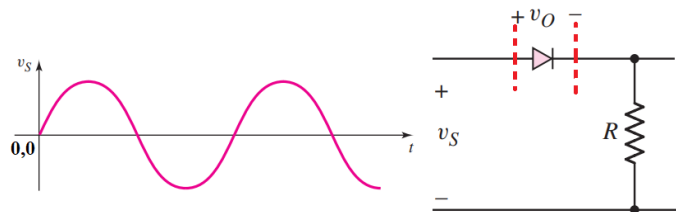22. In the following circuit v_s is a sinusoidal signal. The diode is a regular diode ($V_\gamma \neq 0$). Identify the correct waveform of v_o .



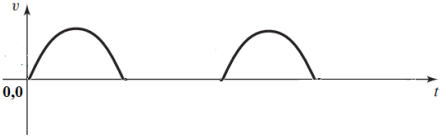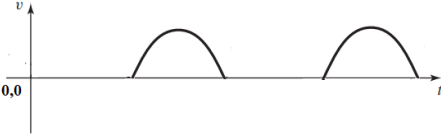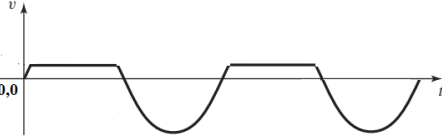- (a) 
 (b) 
 (c) 
 (d) 


Ans. c





23. You are using a general purpose digital multimeter to measure the amplitude of a time varying signal. This multimeter can correctly measure RMS voltage if the voltage waveform is

- (a) square only (b) sinusoidal only
(c) triangular only (d) either sinusoidal or square

Ans. b

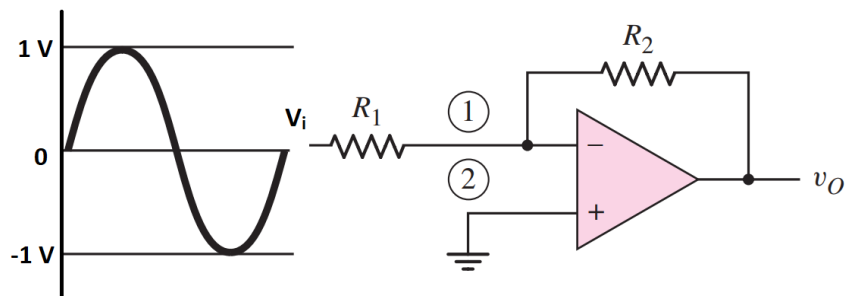24. A sinusoidal signal (v_i) as shown in the following figure is applied to the op-amp circuit. If $R_1 = 1 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$, the output (v_o) will look like




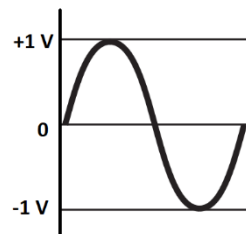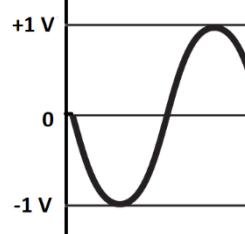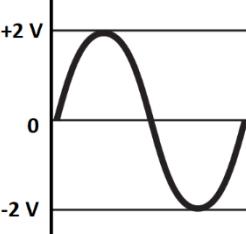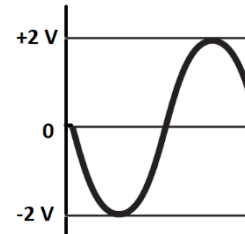- (a)  (b) 
(c)  (d) 

Ans. b

25. When the capacitor C_E is not connected across the resistor R_{E2} in the following amplifier circuit, what happens?

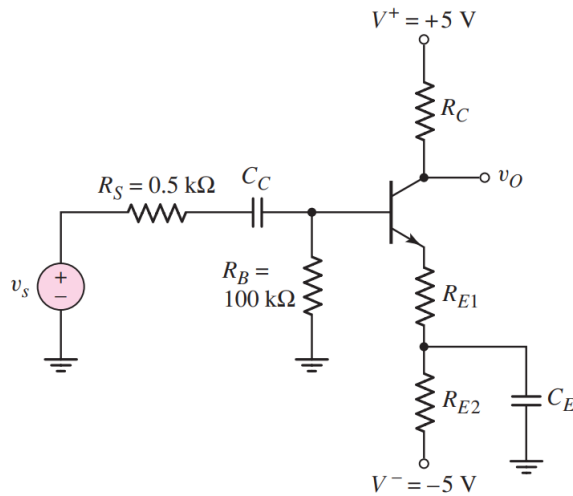- (a) gain decreases (b) gain increases
(c) input resistance decreases (d) none of the above



Ans. a

26. The secondary specification of a center-tapped transformer is 12-0-12 V. Then the peak-to-peak voltage between the two extreme terminals of the secondary is

- (a) 12 V (b) 16.97 V (c) 24 V (d) 33.9 V

Ans. d

27. A 4 V DC voltage source is connected to a voltage regulator using a Zener diode with $V_Z = 6$ V. The load voltage is

- (a) 0 V (b) 4 V (c) 6 V (d) depends on the load resistance value

Ans. 4

28. The input voltage to a half-wave rectifier without a filter is $v_i = 18.84 \sin 314.2t$. The dc component at the output is

- (a) 4.25 V (b) 6 V (c) 9.42 V (d) 13.3 V

Ans. b

29. The rms value of a 12 V dc signal is

- (a) 0 (b) 8.48 V (c) 12 V (d) 16.97 V

Ans. c

30. In a R-C circuit with $R = 1$ kΩ and $C = 4.7$ μF, the time constant τ is equal to

- (a) 4.7 mS (b) 3.76 mS (c) 4.7 μS (d) 10.34 mS

Ans. a

31. The biasing resistors of a CE amplifier with $f_o \approx 500$ kHz, 3-dB bandwidth = 1 MHz and voltage gain $A_v = -10$ are changed to obtain a gain value of $A_v = -100$. Then the following statement is approximately correct for the new amplifier:

- (a) A_v is 17 dB at 1 MHz (b) A_v is 37 dB at 1 MHz
(c) A_v is 37 dB at 50 kHz (d) A_v is 37 dB at 100 kHz

Ans. c

32. In an electronic circuit, current can be directly measured by a

- (a) multi-meter (b) function generator (c) volt meter (d) CRO

Ans. a

33. A sinusoidal voltage source is connected to a RL circuit. Then at very high frequency, phase of the resistor voltage with respect to the input voltage

- (a) lags by 90° (b) leads by 90° (c) 0 (d) none of these

Ans. a

34. The high frequency operation of a CE amplifier is limited because of

- (a) biasing resistors (b) the input and output coupling capacitors
(c) Miller effect (d) emitter bypass capacitor

Ans. c

35. DC biasing is used in a CE amplifier to

- (a) set the transistor gain (b) set the transistor in active regime
(c) both a and b (d) none of a and b

Ans. c


36. The function of the input and output coupling capacitors in C_E amplifier are to

- (a) limit the lower cut-off frequency (b) enhance the higher cut-off frequency
(c) improve the small signal gain (d) provide dc isolation between the amplifier and signal source

Ans. d

37. In the given circuit, what is the peak value of the output wave (v_o), if the input (v_i) fed is 20 V (peak-to-peak) sine wave?


- (a) 10 V (b) 9 V (c) 5 V (d) 4.7

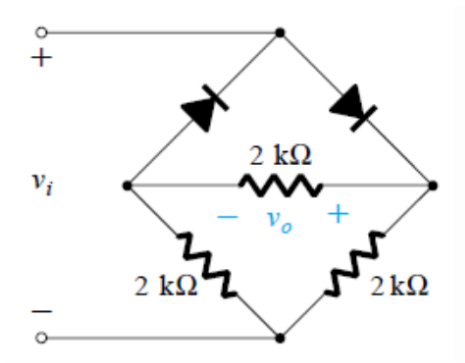

Ans. c

38. Figure shows an electronic voltage regulator. The Zener diode requires a minimum current of 25 mA for satisfactory operations. The value of R (in ohms) required for satisfactory voltage regulation of the circuit is _____


- (a) 70 (b) 80 Ω (c) 100 Ω (d) 400 Ω

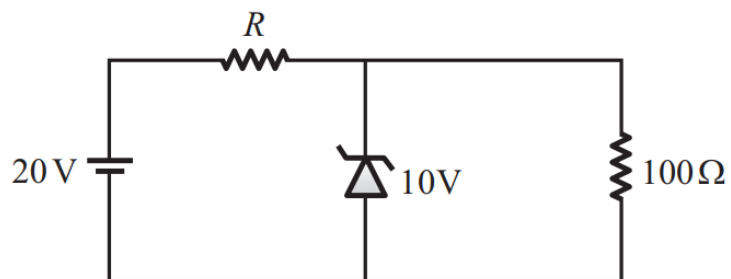

Ans. b

39. The diodes and capacitors in the circuit shown are ideal. The voltage $v(t)$ across the diode D_1 is

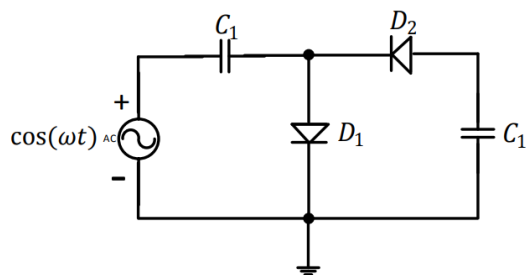- (a) $\cos(\omega t) - 1$ (b) $\sin(\omega t)$
 (c) $1 - \cos(\omega t)$ (d) $1 - \sin(\omega t)$



Ans. a

40. In a series RC circuit, 12 V(rms) is measured across the resistor and 15 V(rms) is measured across the capacitor. The rms source voltage is

- (a) 27 V (b) 19.2 V (c) 1.9 V (d) 3 V

Ans. b