

EC21101
Basic Electronics

Sudip Nag

Book: Electronic Circuits: Analysis & Design
Author: D. A. Neamen

Syllabus (brief):

1. RC circuit theory
2. Diodes
3. Transistors: BJTs & FETs
4. Op-amps
5. Digital circuits

Assessments:

- | | | |
|----------------------|------|-----------------------------|
| 1. Attendance | : 5 | (De-registration by IITKGP) |
| 2. Class Tests 1 & 2 | : 10 | |
| 3. Assignments 1 & 2 | : 10 | |
| 4. Mid-sem | : 25 | |
| 5. End-sem | : 50 | |

RC Circuit Theory: Filters

$R \rightarrow$ Resistors ; $C \rightarrow$ Capacitors ; $L \rightarrow$ Inductors

\swarrow Component's resistance to an AC.

Reactance by ' R ' $= R = X_R$

" " ' C ' $= \frac{1}{\omega C} = \frac{1}{2\pi f C} = X_C$

" " ' L ' $= \omega L = 2\pi f L = X_L$

\swarrow Electronic filters

Filters: 1) Passive & Active (types)

2) Low pass, high pass, band pass, band stop & all pass (types)


3) First order, second order, (types)

4) Butterworth, Chebyshev, Bessel, etc. (types)


\rightarrow Filters are primarily freq. selective circuits.

\rightarrow Passive filters utilize a combination of R, C & L .

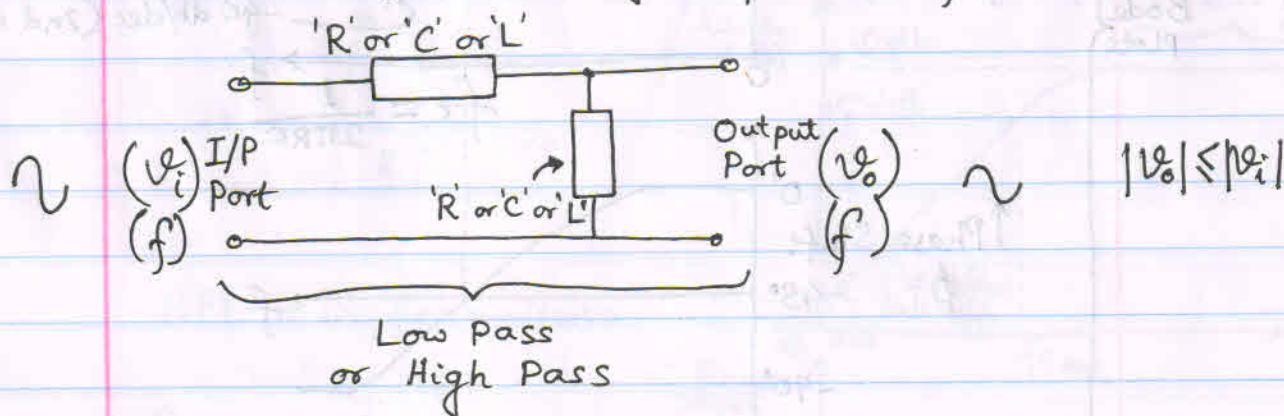\rightarrow Structure/circuit of a passive filter:



1. Low pass filter

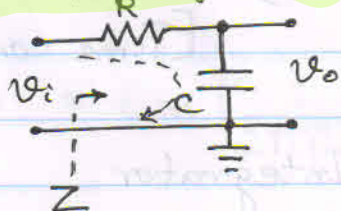


$$V_o = V_i \times \left(\frac{Z_2}{Z_1 + Z_2} \right)$$


$$Z_1 = R ; Z_2 = X_C ; Z = \sqrt{R^2 + X_C^2}$$

$$\Rightarrow v_o = v_i \cdot \frac{X_c}{Z}$$

Low-pass frequency response:

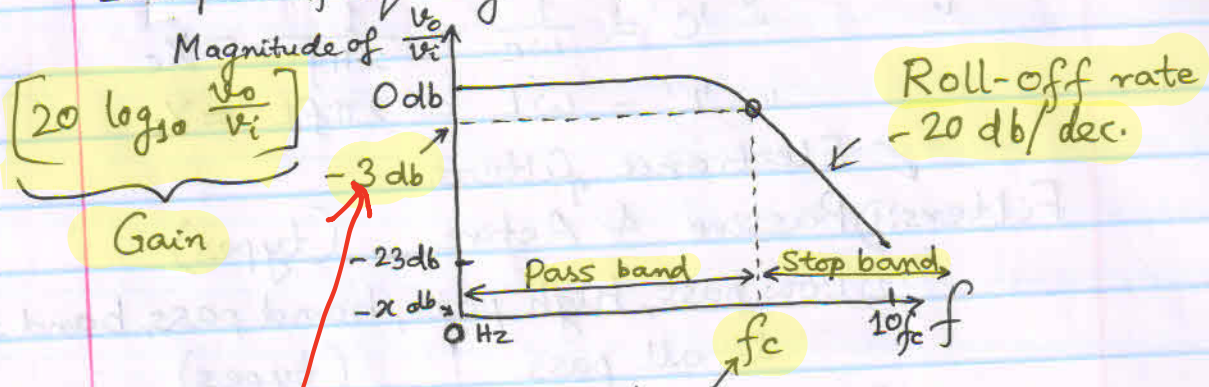

Critical/Cut-off freq

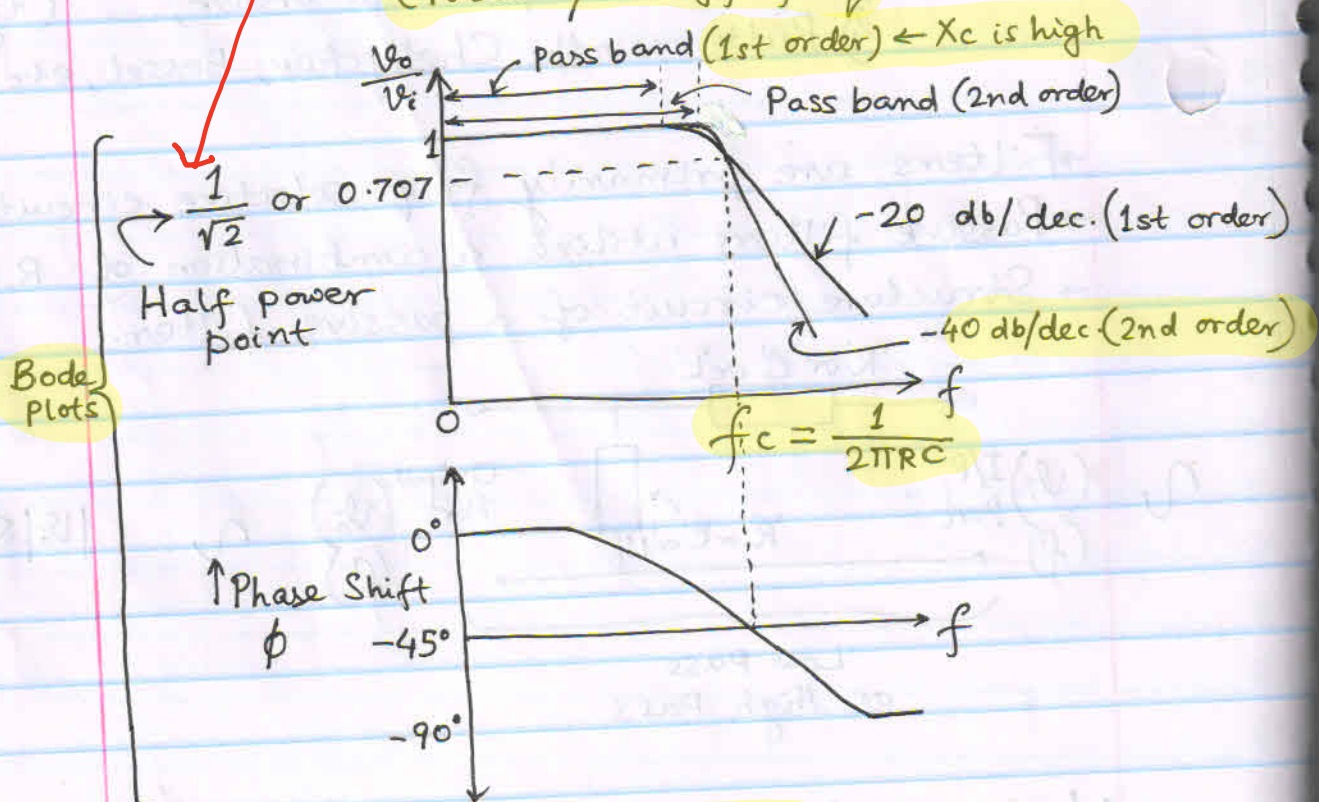


$$\phi = -\tan^{-1}(2\pi f RC)$$

$$\tau = R.C$$

[Time constant]

Low Pass Filter \rightarrow Integrator

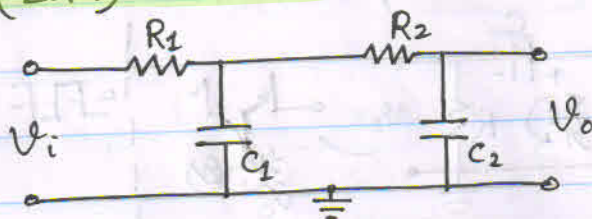Second (2nd) order LPF $(-40 \text{ dB/dec. roll-off})$




$$f_c = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}}$$

$$f_{(-3\text{dB})} \approx f_c \sqrt{2^{\left(\frac{1}{n}\right)} - 1} \quad [n = \text{Order}]$$

Cascading of passive RC stages introduces attenuation. Max. O/P cannot be 0 dB. It is less than 0 dB in the passband (undesired). Therefore, active filters are used for larger/higher order filters.


2. High Pass Filter: 1st order (HPF)

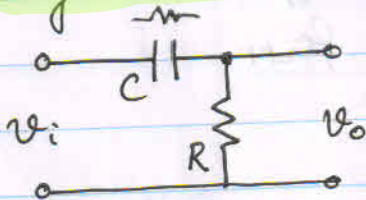

HPF \rightarrow Differentiator


$$f_{\text{CHPF}} = \frac{1}{2\pi RC}$$
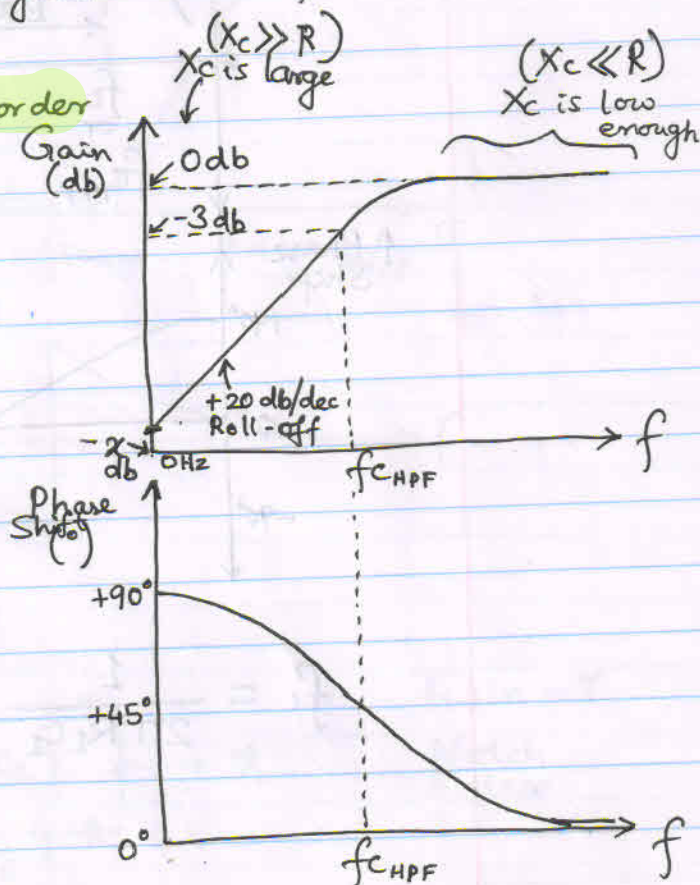
$$\phi = \tan^{-1}\left(\frac{1}{2\pi f RC}\right)$$




Sq. Wave Output


Input Wave

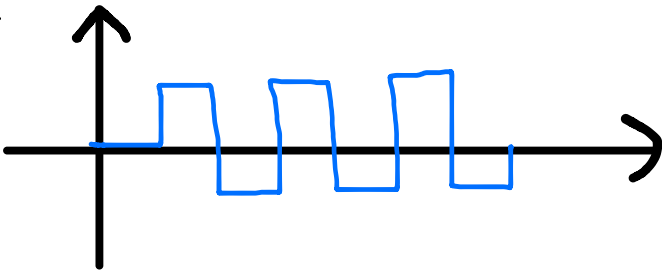


LPF

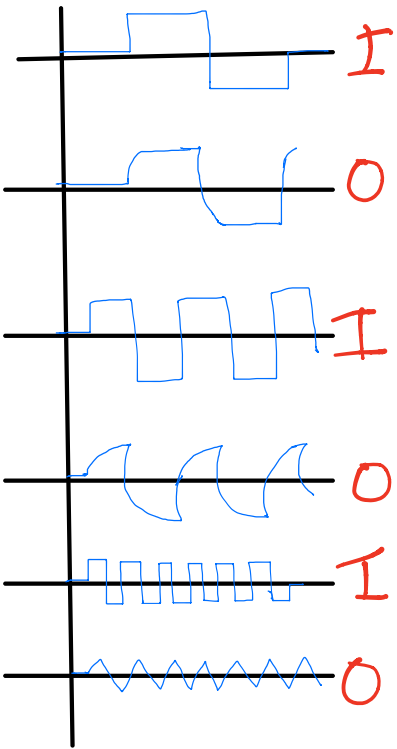


HPF

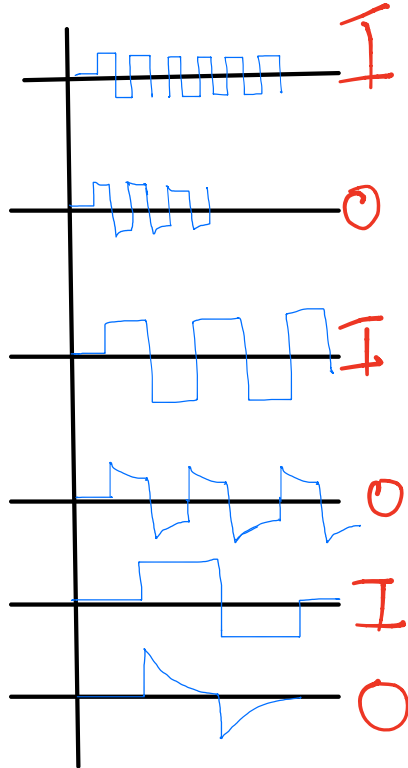


$$V_m(1 - e^{-\frac{t}{RC}})$$

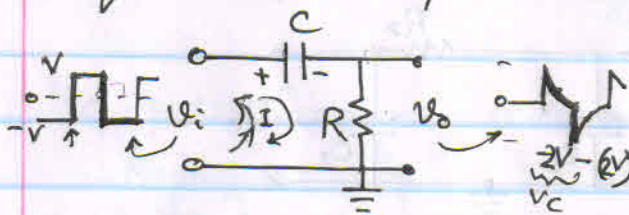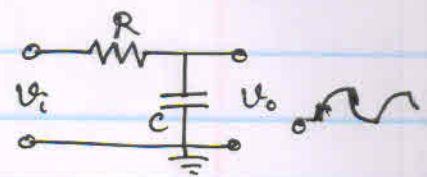
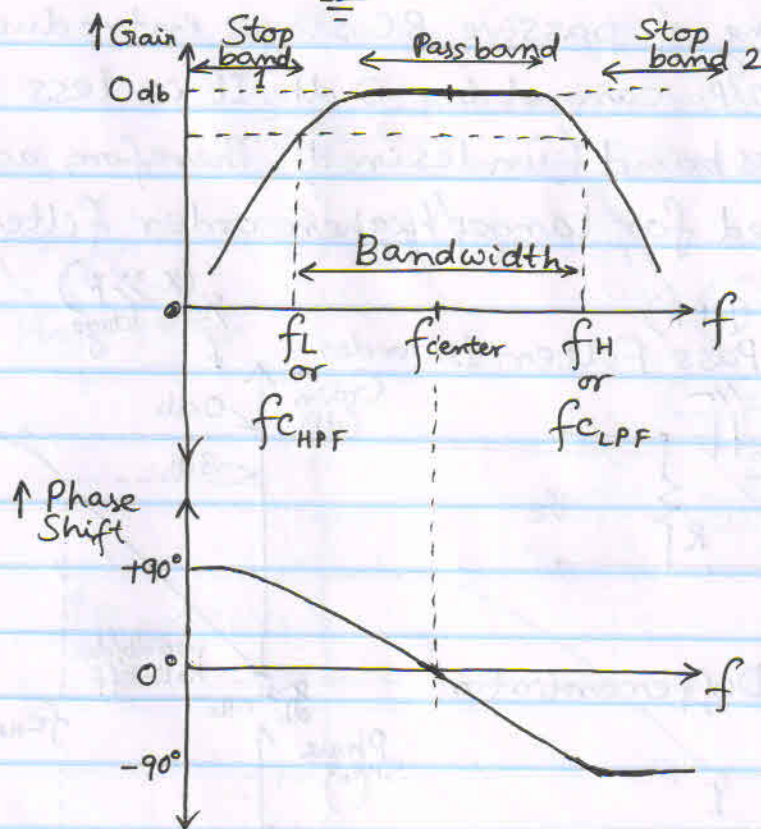
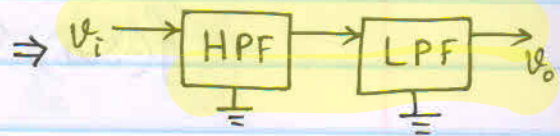
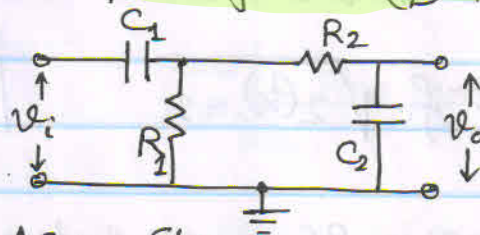
Square wave input: HPF



LPF




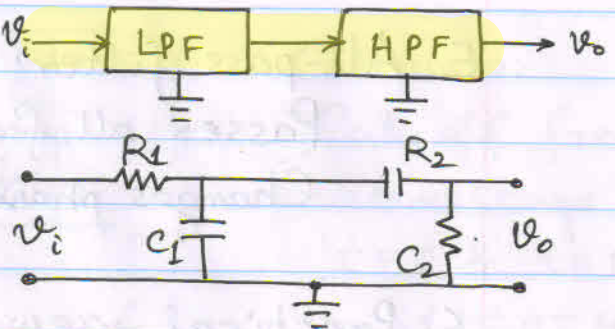3. Band-pass filter (BPF):





$$f_L = \frac{1}{2\pi R_1 C_1} \quad ; \quad f_H = \frac{1}{2\pi R_2 C_2}$$


BPF could also be: $V_i \rightarrow$ [LPF] \rightarrow [HPF] $\rightarrow V_o$



4. Band-stop filter: BSF or notch filter

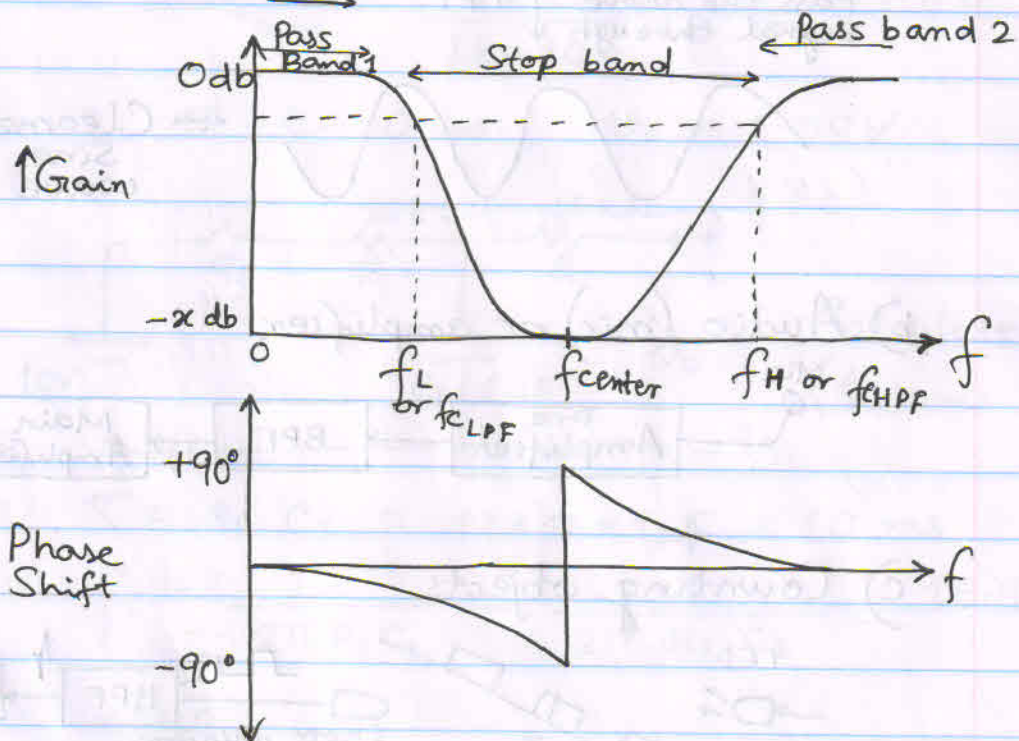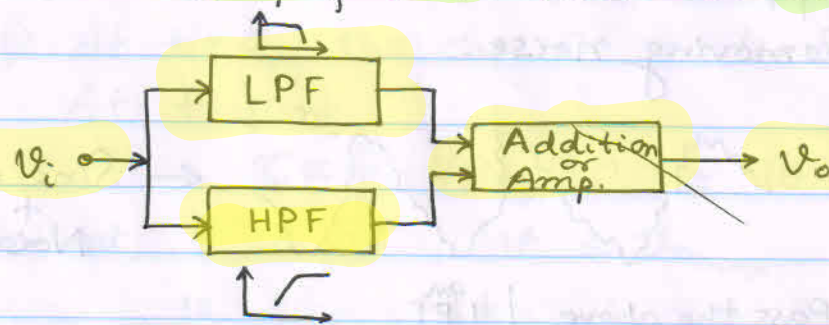

Ckt:

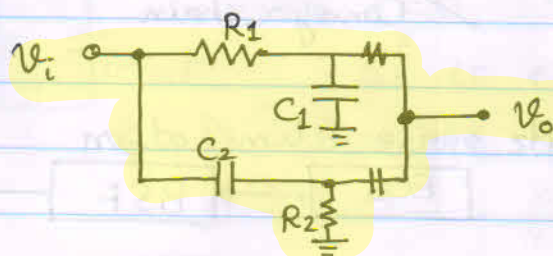


Twin-T
Notch
Filter


5. All-pass filter: Usually active type.
Passes all freq. at a constant gain.
Changes phase shift w.r.t. freq.

6. Practical view-points on filters:
Applications:


a) Removing noise:

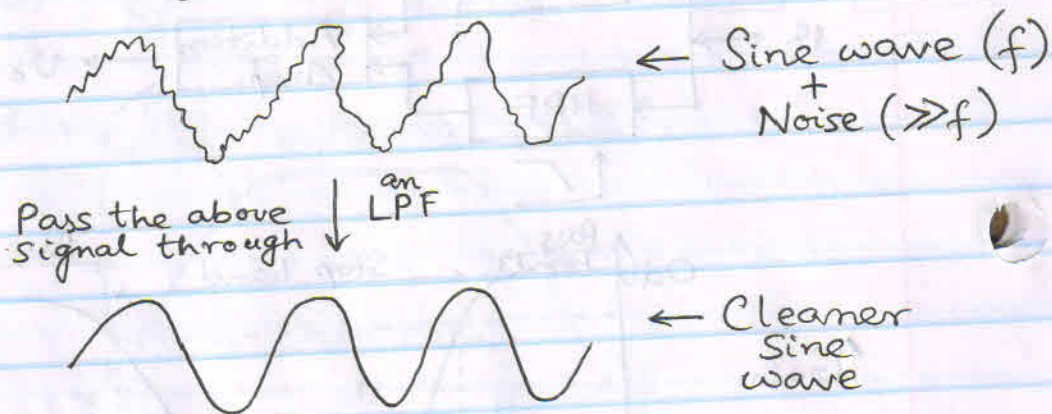

b) Audio (mic) or amplifier:

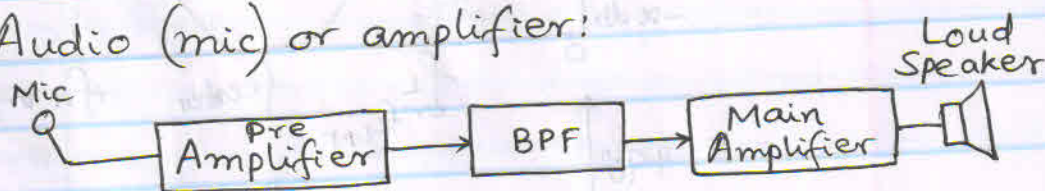


c) Counting objects:

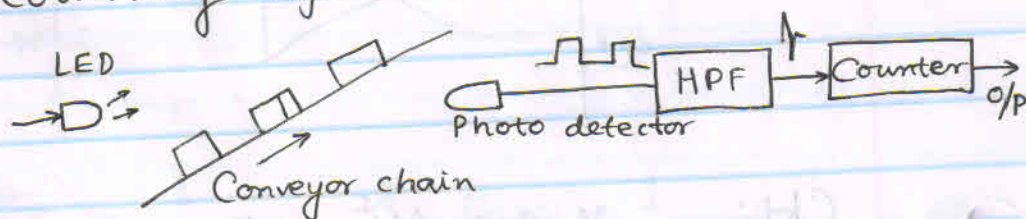

d) 50Hz noise elimination



Tutorial (RC Circuits)

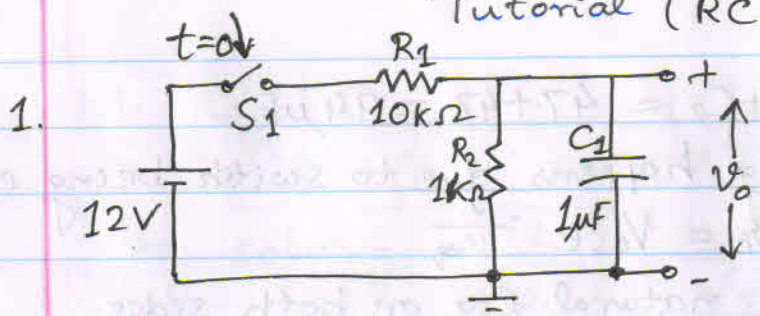

Calculate:

- i) Cut-off freq.
- ii) O/P voltage at $t=0$ & $t=10\text{ms}$

Solⁿ i) $f_c = \frac{1}{2\pi(R_1 \parallel R_2)C} = \frac{1}{2\pi \times (10k \parallel 1k) \times 1\mu F} = 175.07\text{ Hz (Ans)}$


- ii) At $t=0$, the cap. C_1 is discharged; $V_0 = 0\text{V}$ (Ans)
At $t=10\text{ms}$:

$$\tau = (R_1 \parallel R_2) \cdot C_1 = 909\mu\text{s}$$

at, $t \gg 5\tau$, $V_0 \approx V_{0\text{max}}$

$$V_{0\text{max}} = \frac{1k}{1k+10k} \cdot 12 = 1.09\text{V}$$

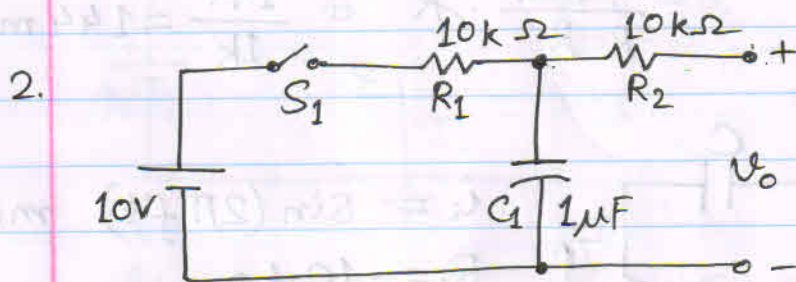
\therefore at $t=10\text{ms}$, $V_0 = 1.09\text{V}$ (Ans)



Calculate τ & f_c
(Assume $R_2 = \infty$)

Solⁿ $\tau = R_1 \cdot C_1 = 10k\Omega \times 1\mu F = 10\text{ms}$ (Ans)
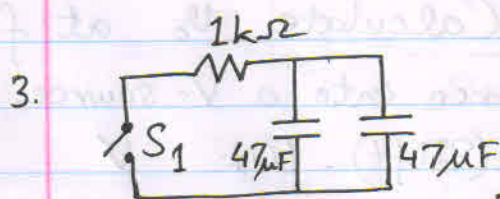
$$f_c = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi \cdot 10k \cdot 1\mu F} = 15.91\text{ Hz (Ans)}$$



At $t=0$, $V_c = 12\text{V}$ &

S_1 is closed

- i) Calculate time when $V_c = 6\text{V}$
- ii) Calc. P_{max} for the resistor.

Solⁿ. i) $C_{eq} = C_1 + C_2 = 47 + 47 = 94 \mu F$

Discharging happens due to switch being closed.

$$\therefore V_c = V_0 \cdot e^{-\frac{t}{R C_{eq}}}$$

Taking natural log on both sides,

$$\ln\left(\frac{V_c}{V_0}\right) = -\frac{t}{R \cdot C_{eq}}$$


$$\Rightarrow t = -R \cdot C_{eq} \cdot \ln\left(\frac{V_c}{V_0}\right)$$

$$= -1k \cdot 94 \mu \cdot \ln\left(\frac{6}{12}\right) = 65.15 \text{ ms} \quad (\text{Ans})$$

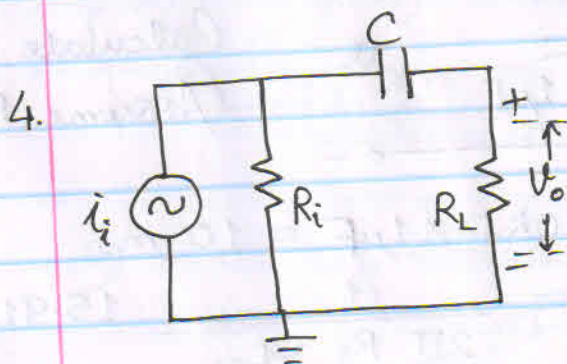ii) Power rating of a resistor:

$$P_{max} = I_{peak}^2 \cdot R$$

$$= \frac{V_{peak}^2}{R \cdot R} \cdot R = \frac{144}{1k} = 144 \text{ mW} \quad (\text{Ans})$$



$$i_i = \sin(2\pi f t) \text{ mA}$$

$$R_i = 10 \text{ k}\Omega$$

$$f = 10 \text{ kHz} \text{ \& } 100 \text{ kHz}$$


$$C = 2.2 \text{ nF}$$

$$R_L = 10 \text{ k}\Omega$$

Calculate V_o at f .

Solⁿ. Transform the I-source into a V-source.
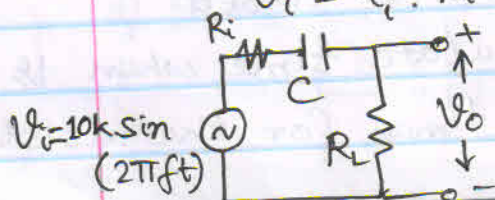
$$V_i = i_i \cdot R_i = \sin(2\pi f t) \cdot 10k \text{ V}$$



$$\left| \frac{V_o}{V_i} \right| = \frac{R_L}{\sqrt{R_L^2 + (X_C + R_i)^2}}$$


by solving, $\left| \frac{V_o}{V_i} \right| = \frac{\omega R_L C}{\sqrt{1 + \omega^2 C^2 (R_i + R_L)^2}}$

At 10 kHz, $\left| \frac{V_o}{V_i} \right| = 0.47$

$\therefore V_o|_{10\text{kHz}} = 4.7 \sin(20 \times 10^3 \pi t) \text{ V (Ans)}$

At 100 kHz, $\left| \frac{V_o}{V_i} \right| = 0.499$

$\therefore V_o|_{100\text{kHz}} = 5 \sin(20 \times 10^4 \pi t) \text{ V (Ans)}$

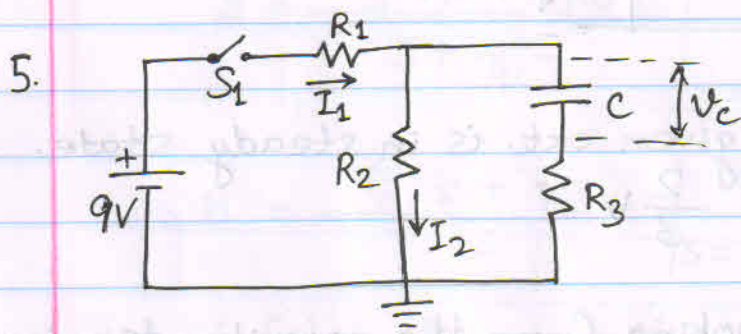

$V_c = 0 \text{ at } t < 0$

$R_1 = 10 \text{ k}\Omega$

$R_2 = 10 \text{ k}\Omega$

$R_3 = 1 \text{ k}\Omega$

$C = 10 \mu\text{F}$

At $t = 0$, S_1 is closed i) Find I_1 & I_2 at $t = 0, 1 \text{ s}$.

At $t = 2 \text{ s}$, S_1 is opened ii) " " " " " $t = 2 \text{ s}$.

Solⁿ i) At $t = 0$, C is like a short.

$$I_1|_{0s} = \frac{9}{R_1 + (R_2 || R_3)} = \frac{9}{10\text{k} + (10\text{k} || 1\text{k})} = 0.825 \text{ mA}$$

$$I_2|_{0s} = \frac{R_3 \cdot I_1(0s)}{R_2 + R_3} = \frac{1\text{k} \times 0.825\text{m}}{10\text{k} + 1\text{k}} = 75 \mu\text{A}$$

$$\tau = R_{eq} \cdot C = [(R_1 || R_2) + R_3] \cdot C = 6\text{k} \cdot 10\mu = 60 \text{ ms}$$

$$\therefore 1s \gg \tau$$

at 4.5V

At 1s, C is fully charged \rightarrow No 'I' through C.

$$\therefore I_{1(1s)} = I_{2(1s)} = \frac{9}{R_1 + R_2} = \frac{9}{20k} = 0.45mA \quad (\text{Ans})$$

ii) At $t = 2s$, battery is disconnected.

$$I_{1(2s)} = 0$$

$$I_{2(2s)} = \frac{4.5}{R_2 + R_3} = \frac{4.5}{10k + 1k} = 409\mu A$$