

# TIME & FREQUENCY DOMAIN REPRESENTATIONS

FT  
(Fourier Transform)  
IFT

→ V  
→ I  
→ Q

SIGNALS

→ Sine wave  
→ Square  
→ Ramp

Time domain

Frequency domain

Video


Audio

(Type)

(Shape)



(Representation)

(Applications)

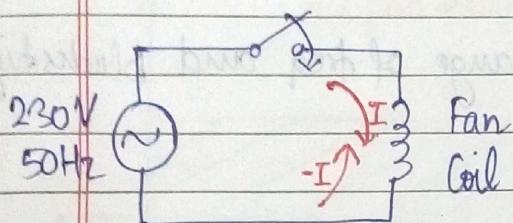


Fan  
Coil

Time  
Domain

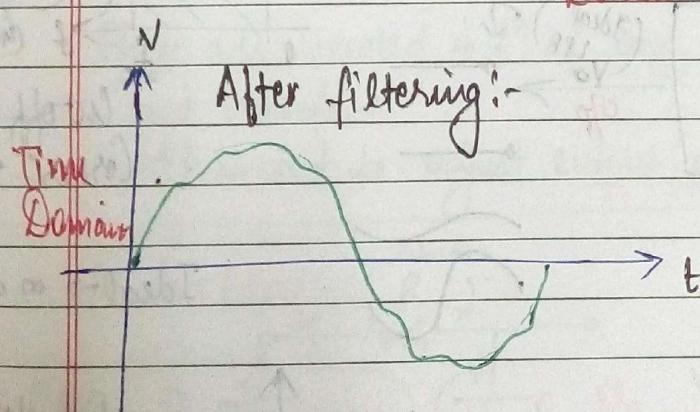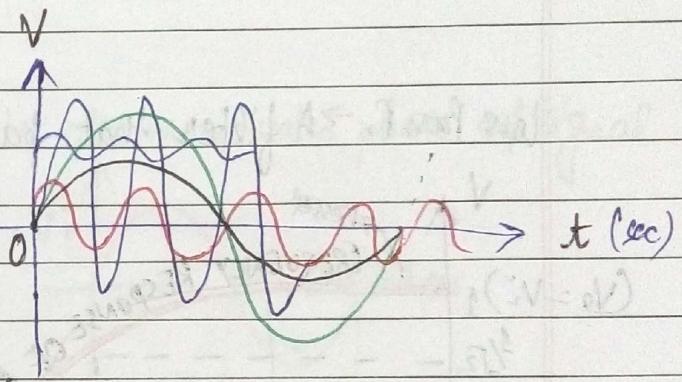

Freq. V2  
Domain

$\sum$  1 = +ve

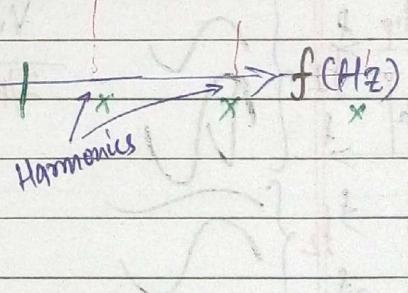

## FILTERS

Group of Electronic circuits that accept certain band & ~~reject~~ reject certain other bands. (also, bands of frequency)

## FILTERS

- Low Pass
- High Pass
- Band Pass
- Band Stop
- All Pass

(Type)

- RC
- RL
- RLC
- LC

(Realization Components)

- Butterworth  $\rightarrow^A$
- Chebyshev  $\rightarrow^A$
- Bessel  $\rightarrow^A$

Passive






Active


Generally A

Semiconductor devices

(Response)



Low Pass F. → A filter that passes low range of freq and blocks high freq.

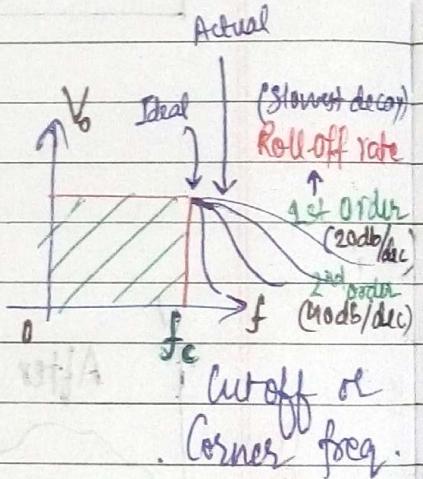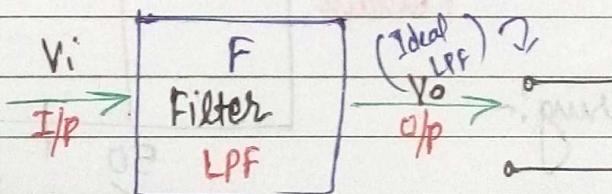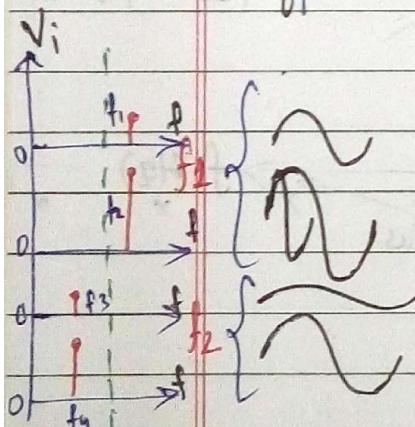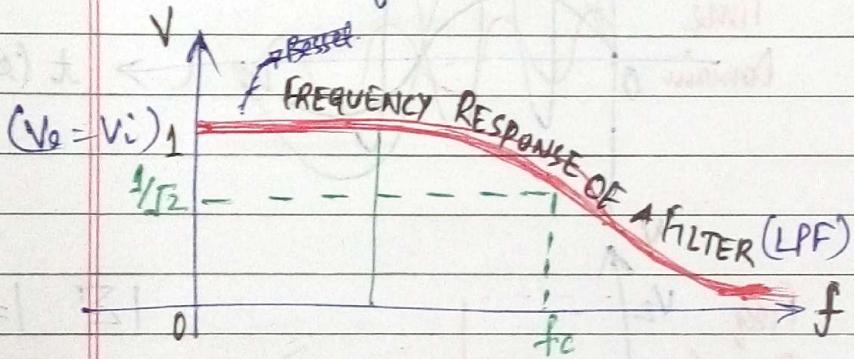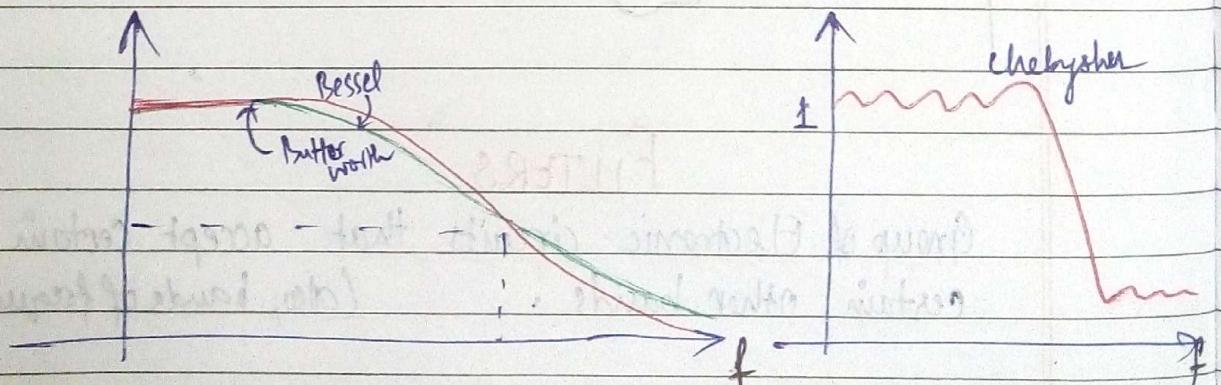Ideal  $\rightarrow \infty$  db/dec

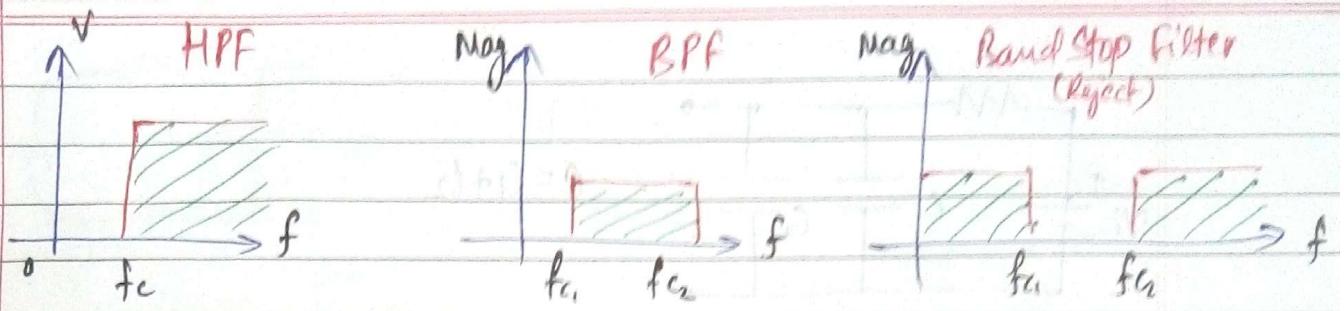

All pass filter


filter also manipulates phase of signal

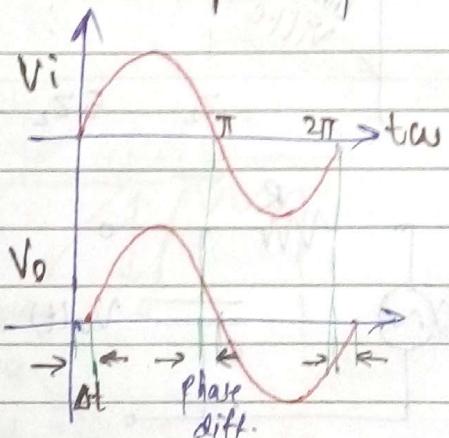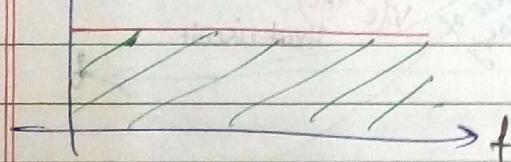

Phase diff can never become 0,  
hence, there is some phase shift.

Phase diff created is  $f^n$  of freq  
and waveform.

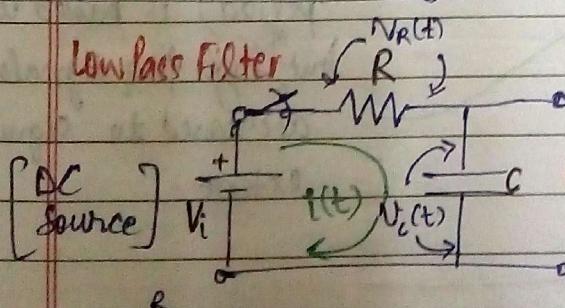APP is used to adjust output phase angle.







$$i(t) = \frac{V_i - V_c(t)}{R}$$

Capacitor can be  
assumed to be a  
battery.

\* Super Capacitor

$t=0^+$  (instant when switch is closed)

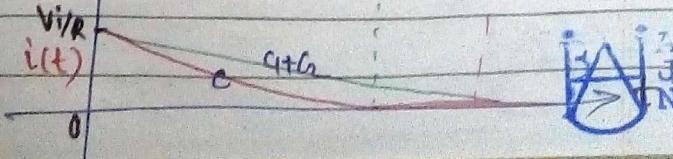
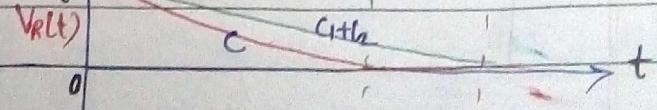
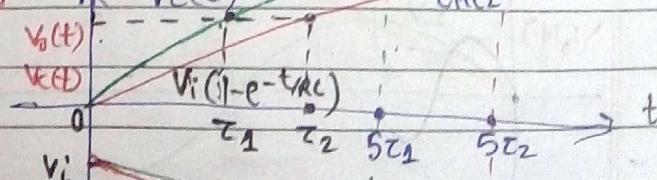


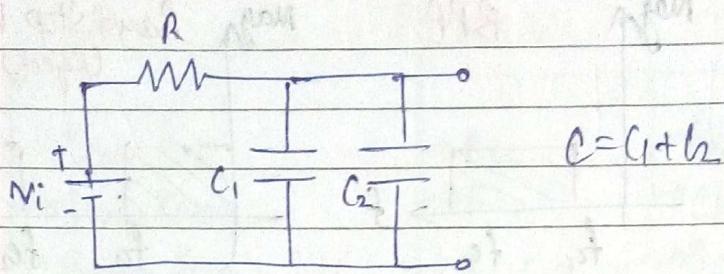

$\tau$  = Time Const.



$$\tau = R C \text{ (sec)}$$

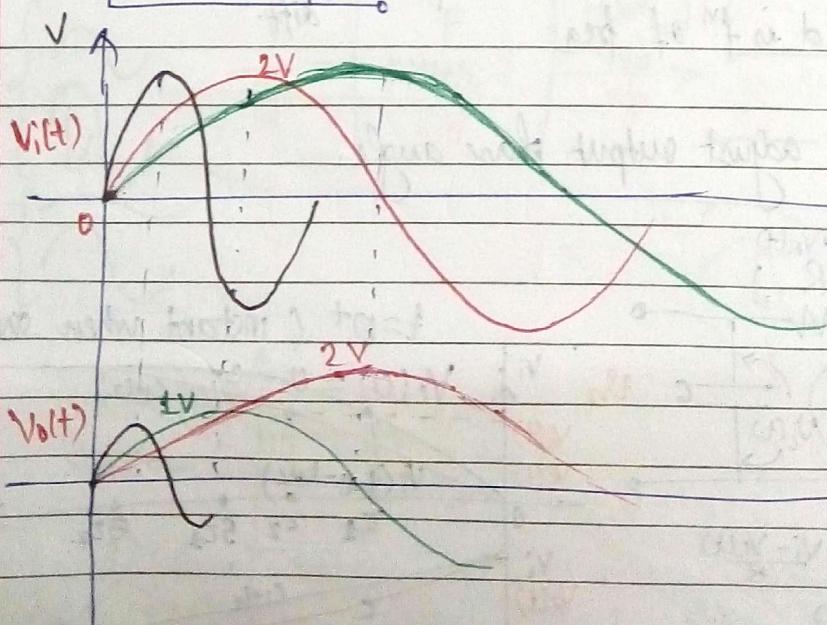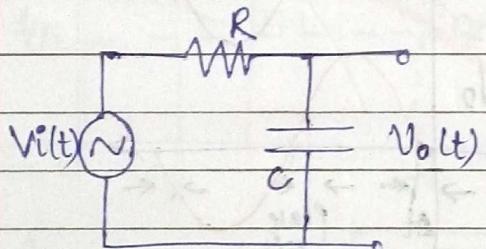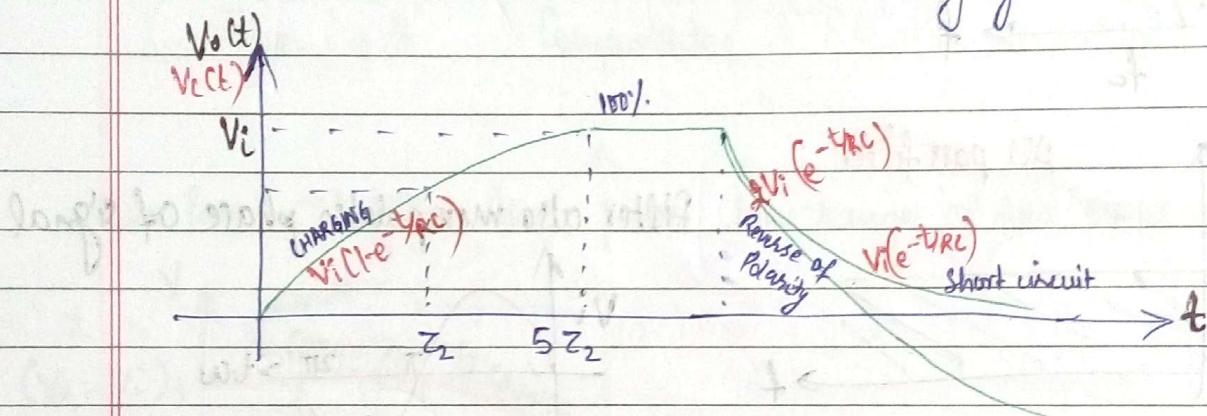$5\tau \rightarrow 99.7\%$   $\approx 100\%$  charging.



Working of LPF:-

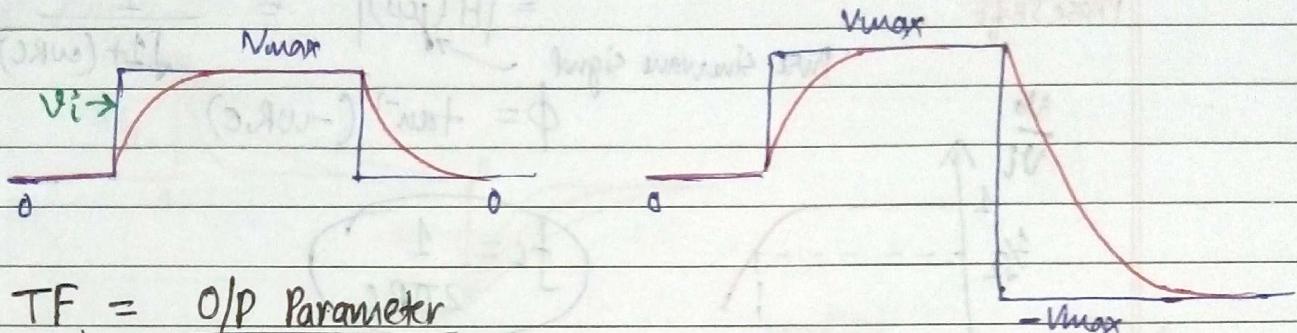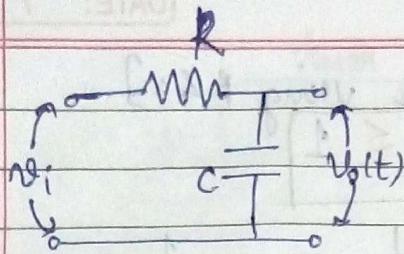Amplitude of signals with low freq (high time period) is passed unchanged but high freq signals are decreased to significant extent.




- $\text{TF} = \frac{\text{O/P Parameter}}{\text{I/P Param.}}$   
Transfer function


(Impedance of Resistor)  $Z_R = R$

(Imp. of Capacitor)  $Z_C = \frac{1}{sC}$

complex freq

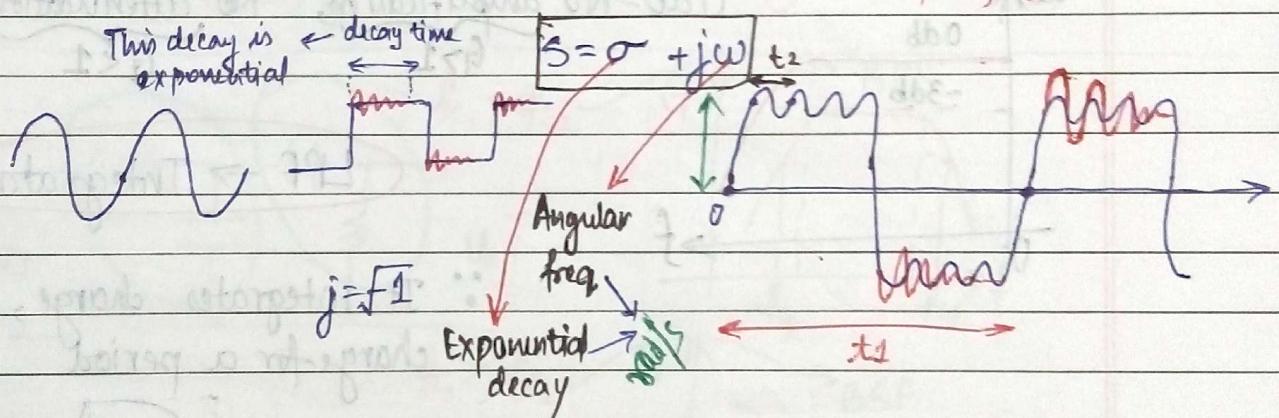

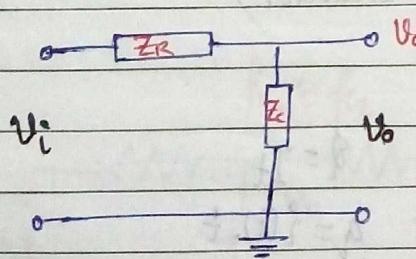\* For a steady state sine wave,  $\sigma = 0 \Rightarrow s = j\omega$




$$V_o = \frac{Z_C}{Z_R + Z_C} V_i$$

$$= \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_i = \left( \frac{1}{sRC + 1} \right) V_i$$

$$\text{TF} \rightarrow H(s) = \frac{V_o}{V_i} = \frac{1}{sRC + 1}$$

$$\Rightarrow V_o \leq V_i$$

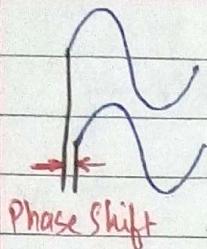( $\sigma = -\omega$  in case of active filters)




[Passive low pass filter using  $R$  &  $C$ ]

$$[Gain = G = |H_C(s)| \leq 1]$$

$$= |H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

Pure sine wave signal

$$\phi = \tan^{-1}(-\omega RC)$$

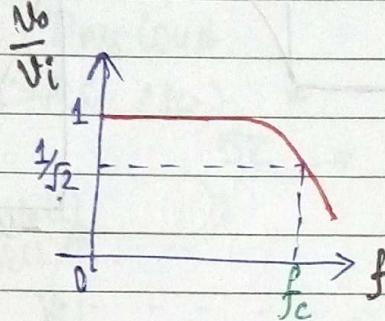

$$f_c = \frac{1}{2\pi RC}$$

\* Gain is expressed in db

$$G_{db} = 20 \log_{10} \left( \frac{V_o}{V_i} \right)$$

$G_{db}$

0 db

-3 db


0 db = No amplification, No attenuation

$G > 1$


$G < 1$

LPF  $\rightarrow$  Integrator

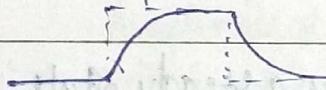$\therefore$  It integrates charge, holds that charge for a period




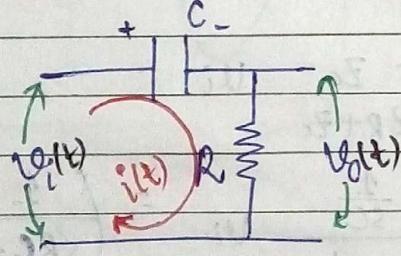HIGH PASS FILTER (HPF  $\rightarrow$  Differentiator)





$$Q = It$$

$$q = i(t) \cdot t$$

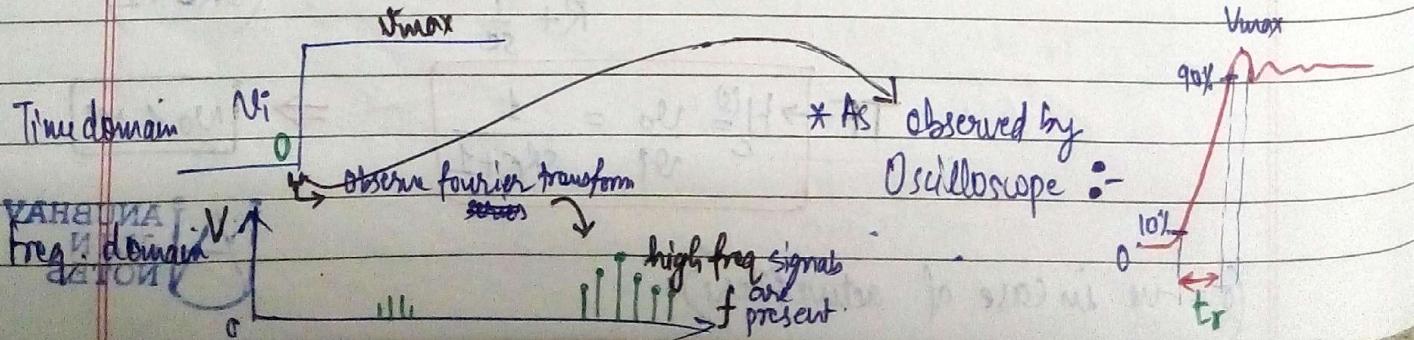




Unison

(Loud)

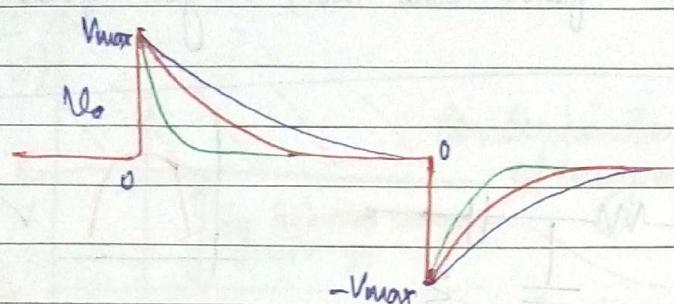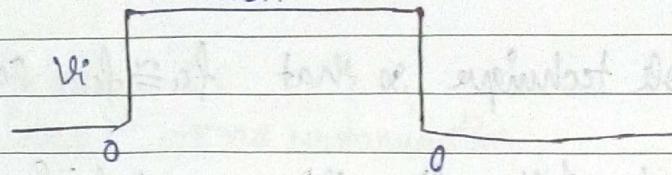

High freq.

Low freq.

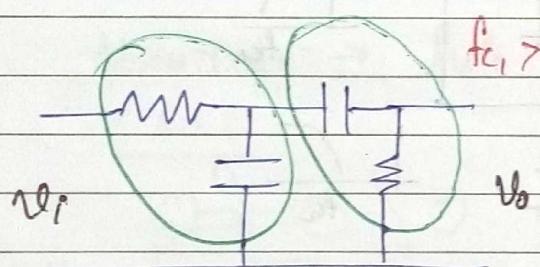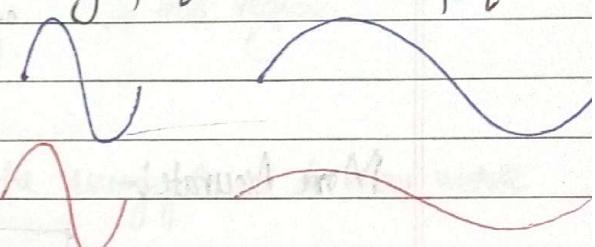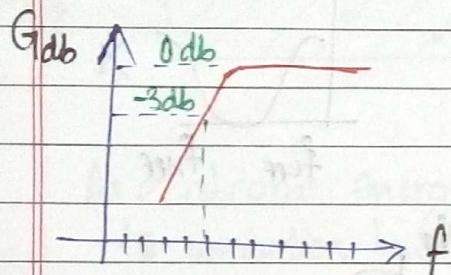


$f_{c1} > f_{c2}$   $G \uparrow$   $\rightarrow$  BPF

$f_{c1} < f_{c2}$   $G \uparrow$   $\rightarrow$  BSF



(Accurate version  $\rightarrow$  PTO)

$f_{c1} \approx f_{c2}$

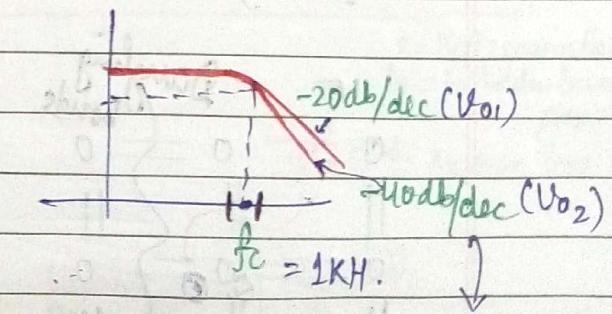

Rate of decrease

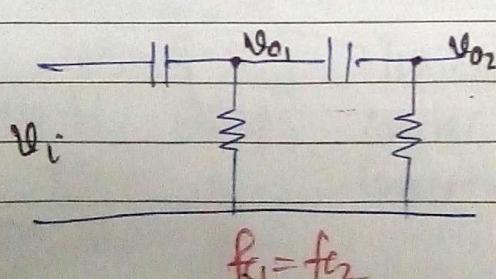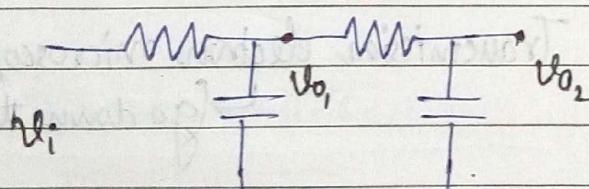BAJANIEHATABLES AS  
NOTES  $f_{c1} \approx f_{c2}$






We use split pole technique so that  $f_{c1} \approx f_{c2}$  (approx. equal)


Hence, if we cascade filters like this, we get higher order filters.

BSF.

Cascadic :-  
Version

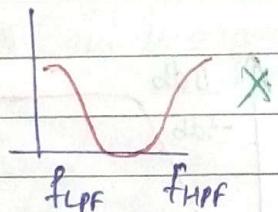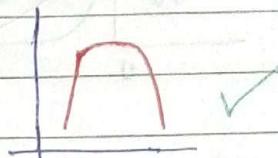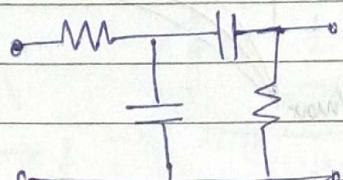

More Accurate:-

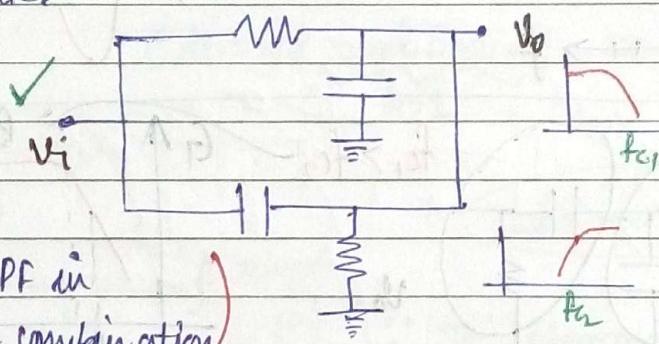


(LPF & HPF in  
parallel combination)
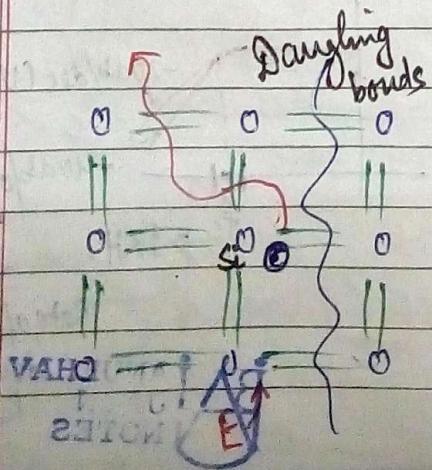
## SEMICONDUCTORS

(IV)


Si } 4 e<sup>-</sup> in valence shell. → Lattice Structure  
Ge }



Transmission electron microscope


↳ (go down to Å level)

## Intrinsic S-C

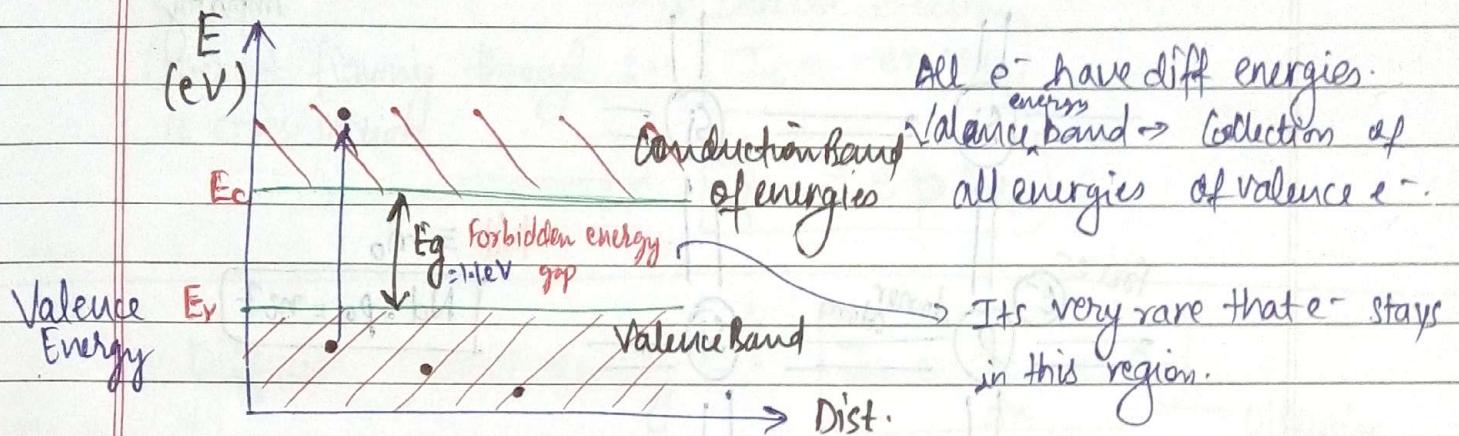(Pure)  $\rightarrow$  no contamination.

As  $e^-$  absorbs energy, it rises up the energy level & may move to conduction band.

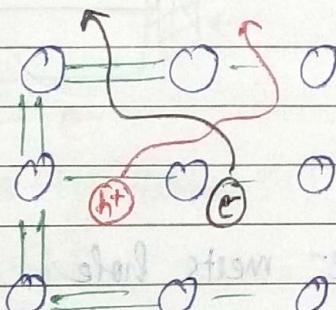Absence of  $e^- \rightarrow$  hole (when  $e^-$  is expected but actually not present)



Thermal Equilibrium

Intrinsic Carrier Concentration

$$n_i = B T^{3/2} e^{-E_g/2kT}$$

const.  $\downarrow$   $\downarrow$   $\downarrow$   
 $S_i$   $g_i$   $C$

 $k = \text{Boltzmann Const}$  $E_g = \text{forbidden energy gap}$  $T = \text{Absolute Temp (K)}$ 


27/07/16

 $T = 300 \text{ K. or } 27^\circ \text{C.}$ 

$$n_i p_i = n_i^2$$

No. of  $e^-$  No. of  $h^+$

Intrinsic carrier concentration

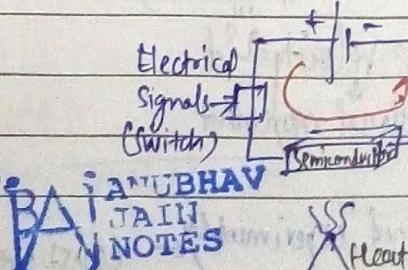


Current is  $f^n$  of Temp.

Heat (change  $T$ ).



Extrinsic S-C  
(Impure)

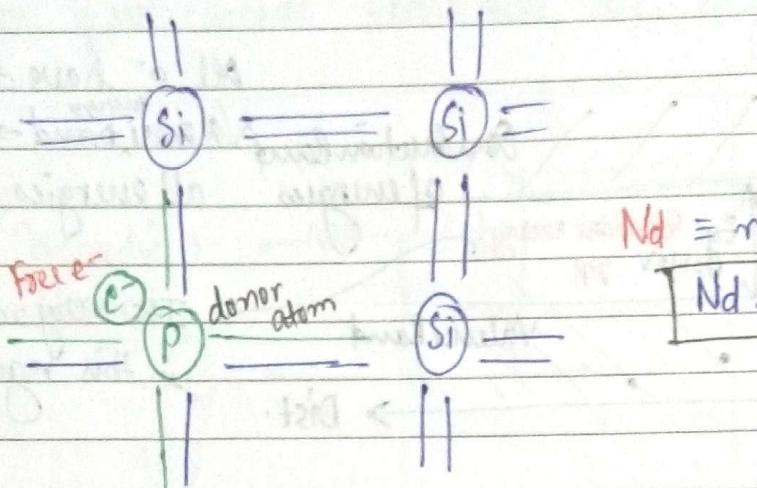✓ (S-C) ✓  
3 4 5  
(Boron) Impurity  
P(Phosphorus)



$$N_d = n_0$$

$$N_d \cdot p_0 = n_i^2$$

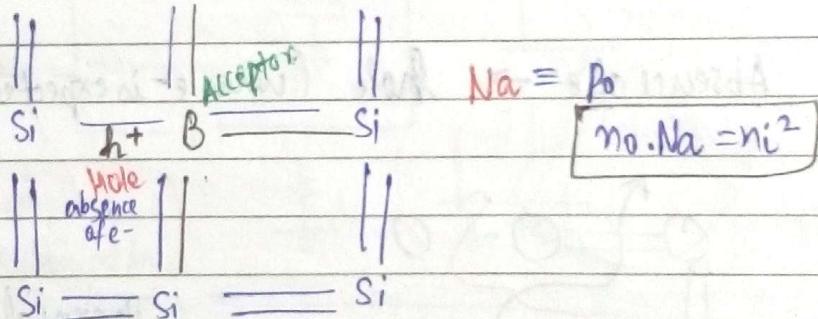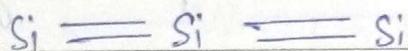

\* Recombination :- free  $e^-$  meets hole ( $e^-$ -hole pair)

DRIFT & DIFFUSION

In presence of any kind of energy, movement of charge carriers is called drift (e.g. stirring).

speed of stirring.

Drift velocity =  $\frac{d}{t}$   
directional movement

happens in absence of ext. energy.

Drift vel. of an  $e^-$  in any extrinsic S-C

$$V_{dm} = -\mu n E$$

Elec. field

Mobility

Agility of charge particle

determined experimentally  
const value

$$n_{dp} = + \mu_p \cdot E$$

Mobility:  $\text{cm}^2/\text{V-s}$   $\mu_n \rightarrow 1350$   
 $\mu_p \rightarrow 480$

Drift Current Density

Current flowing through :-  
a cross section

$$J_n = -e n v_{dn}$$

$$J_p = + e p v_{dp}$$

Diffusion Current density :-

$$J_n = \frac{dn}{dx} e D_n$$


Diffusion const.

$$J_p = \frac{dp}{dx} e D_p$$

Silicon Flux.  $Si_{15} + B_5$

$Si_{14} + B_3$

27/07/16

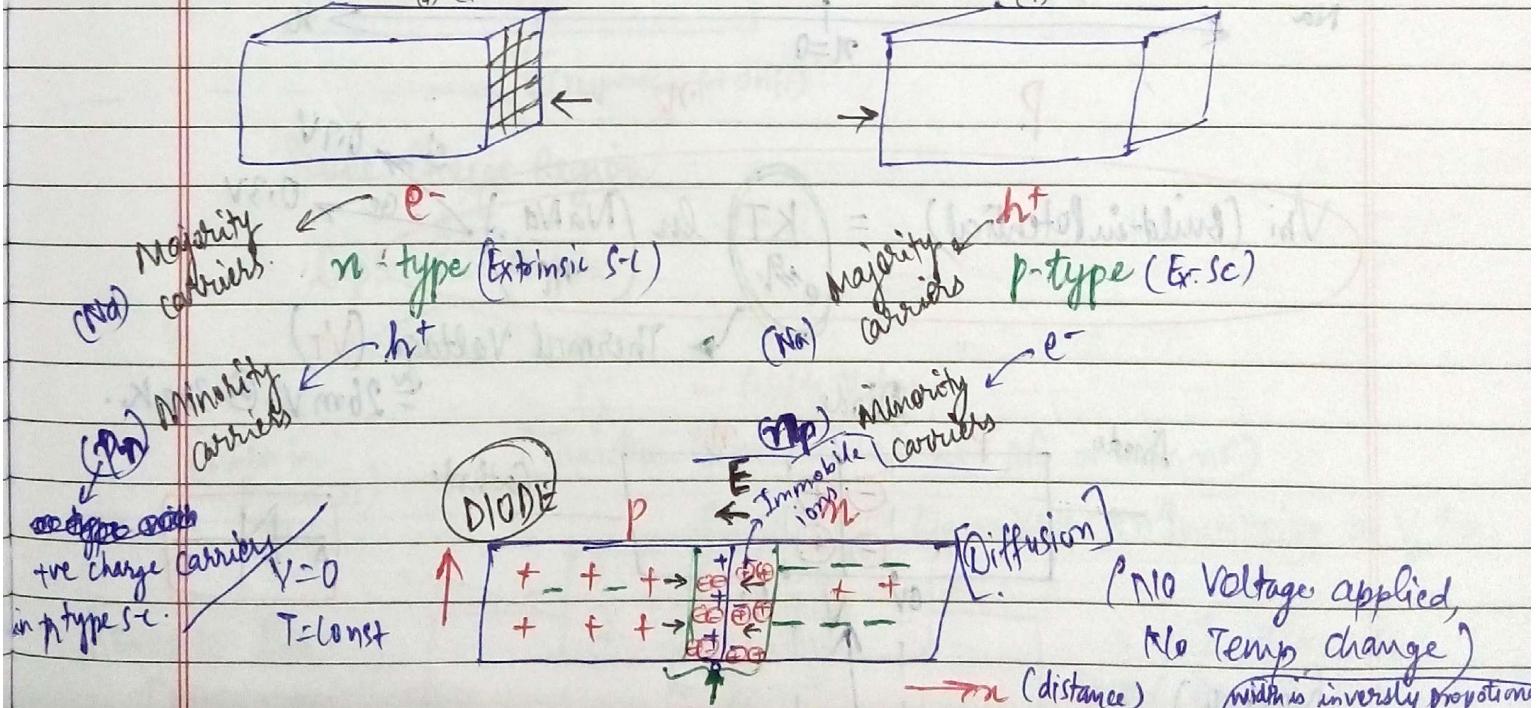

Metallurgical Junction (p-n Junc)  $\rightarrow$  Space Charge Region

At junction, recombination happens.

Keeps on happening till eqb. state

Immobilized ions block path of other mobile ions.

$V_{bi}$  (Build-in Potential)  
 ANUHAI  
 NOTES

Equilibrium condition  $\leftrightarrow$  holes  $\rightarrow$  Diffusion  $\leftrightarrow$  Drift.  $\rightarrow$  E generated from n to p

(Drift = Diffusion)


No. of charge carriers moved by drift = -diffusion

Immobilized ions  $\equiv$  Net movement is zero.

Mobility of e is higher

\*  $\mu_n > \mu_p$

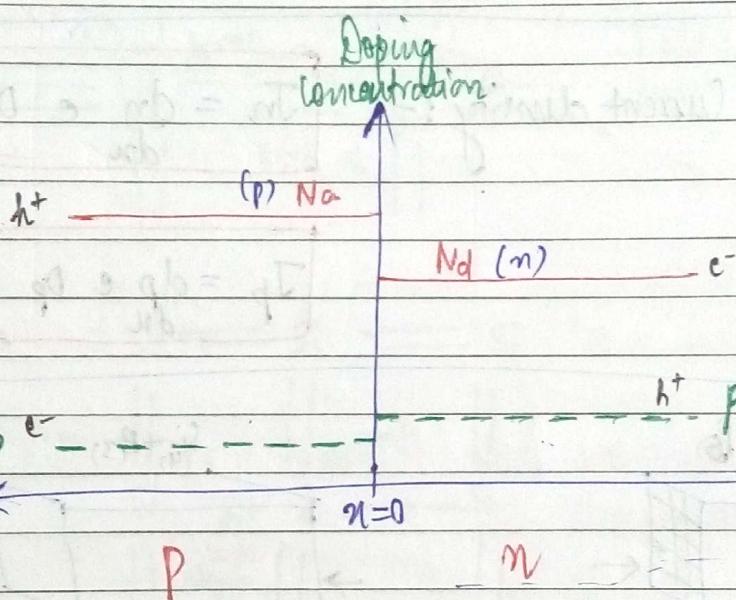To compensate that, Na is kept greater than Nd.




$$\frac{n_i^2}{Na} = \frac{n_p p_0}{Na} e^- \quad h^+ - p_{n_0} = \frac{n_i^2}{Na}$$

$$V_{bi} (\text{Build-in Potential}) = \frac{kT}{e} \ln \left( \frac{Na Na}{n_i^2} \right)$$


Thermal Voltage ( $V_T$ )

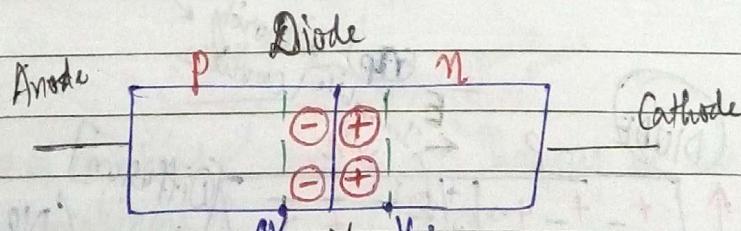$\approx 26 \text{ mV.} @ 300 \text{ K.}$



$\{N_{\text{ext}}=0\}$   
 $\{T=\text{const}\}$

VAHESUNA  
NIT  
SETON

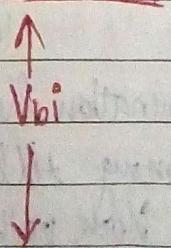

Doping: Addition of impurities.

Mass action law:  $n_i^2 = n_0 p_0$

$$n_i^2 = n_0 \left( \frac{n_i^2}{n_0} \right) = N_d p_0 : n\text{-type}$$

Pure

Extrinsic


$$n_i^2 = \left( \frac{n_i^2}{N_a} \right) p_0 = n_0 N_a : p\text{-type}$$

If  $N_a \uparrow$ ,  $N_p \downarrow$  as minority charge carriers starts recombination with increased majority charge carriers.

(I) (E)

$$p_0 \rightarrow N_d$$

$$N_d \gg n_0$$

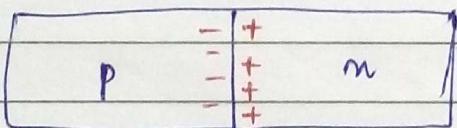

Confined  $E$  (responsible for drift)

Space Charge Region  
or

Depletion Region

$$V_{bi}$$

(built-in potential)


$C_j$  - Finite Value.

(Junction Capacitance)  $\rightarrow$  (pF or max. nF)

Space Charge Region keeps on Increasing as  $V \uparrow$ .

REVERSE BIAS

CONDITION

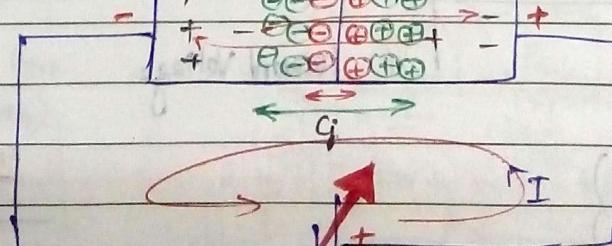

$I \rightarrow$  very low

Range ( $fA \rightarrow nA$ )

nanometre  
 $nm \rightarrow$  Depletion Region  
 $\mu m$


Breakdown (VBR)

Reverse Voltage

Avalanche  
(Permanent)


Zener

(Reversible)

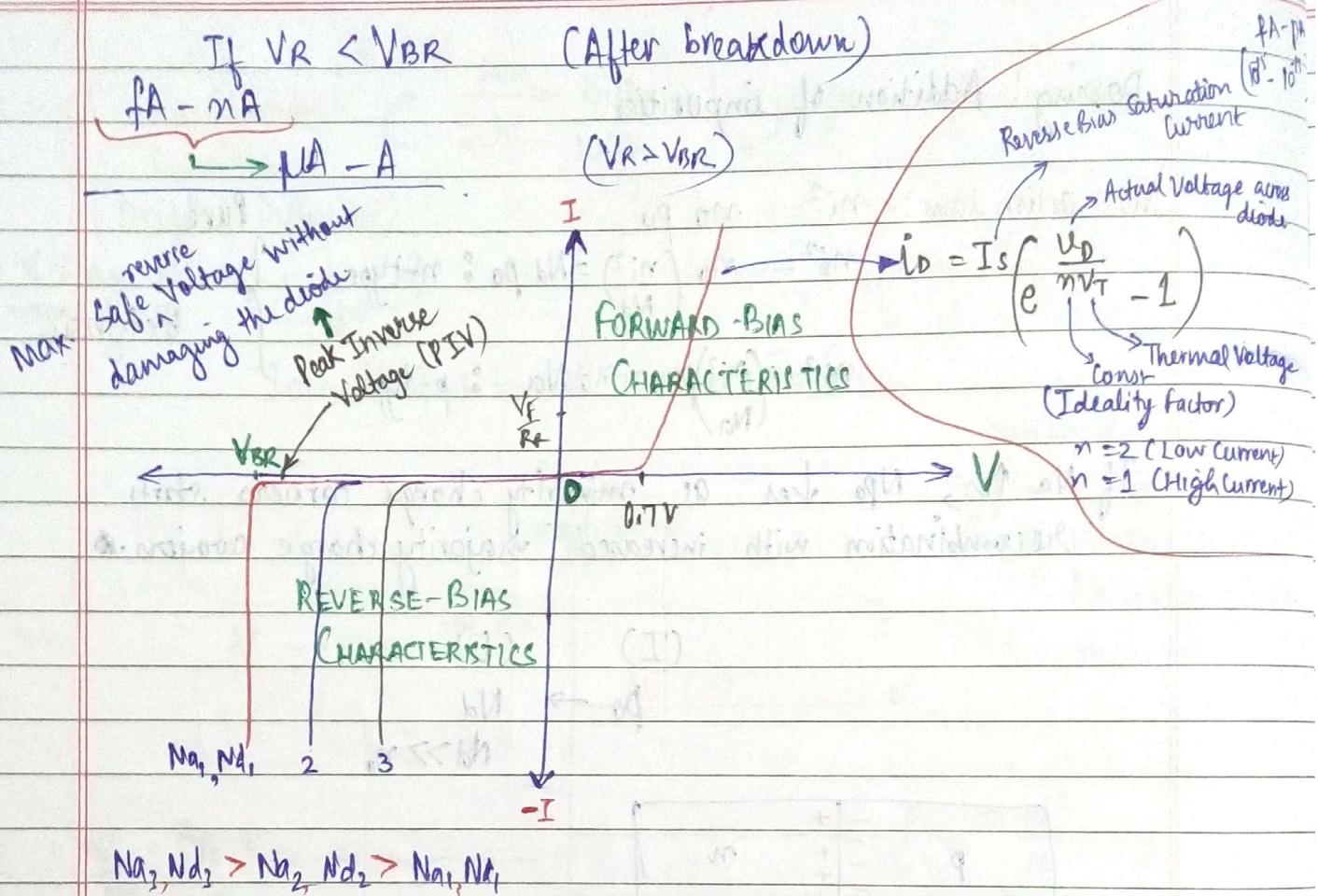


Space Charge Region  $\downarrow$  (Nullifies)

FORWARD BIAS CONDITION

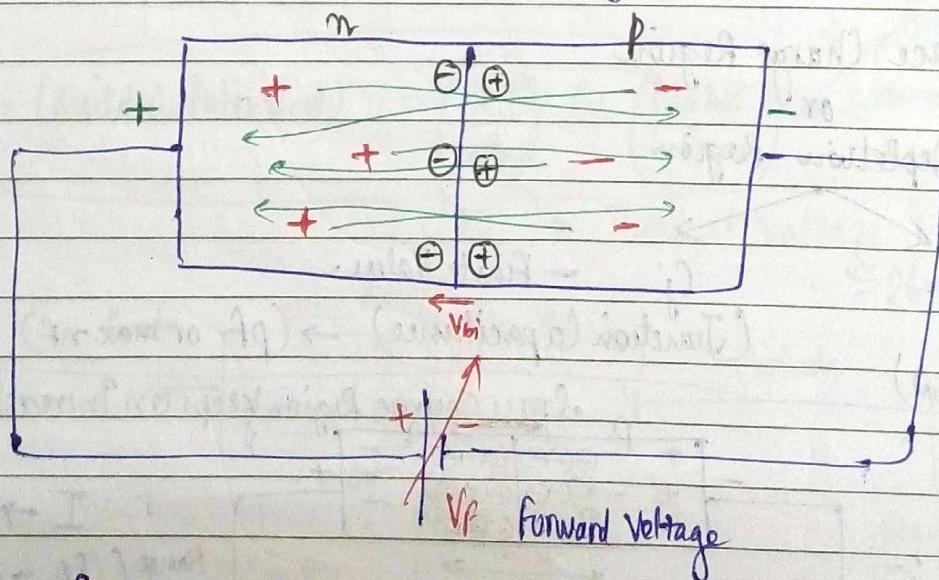

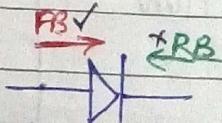
$$V_{bi} = \begin{cases} 0.7V & (\text{Si}) \\ 0.3V & (\text{Ge}) \end{cases}$$









Diode :-

FB - ON

RB - OFF

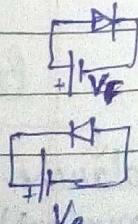

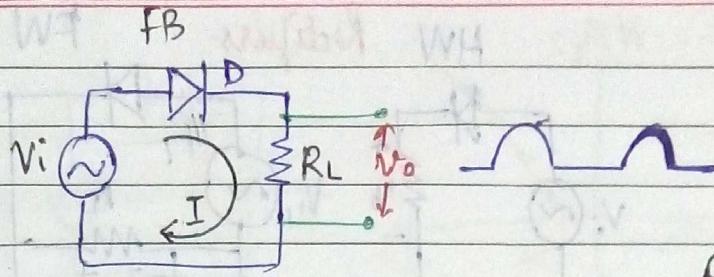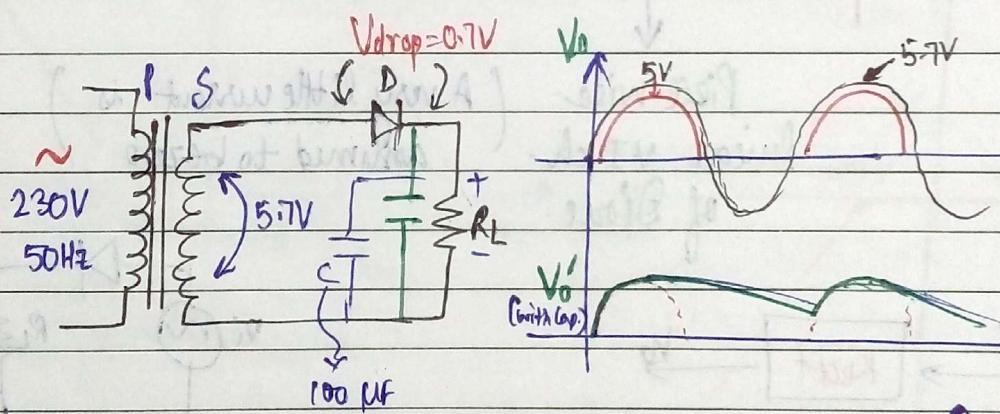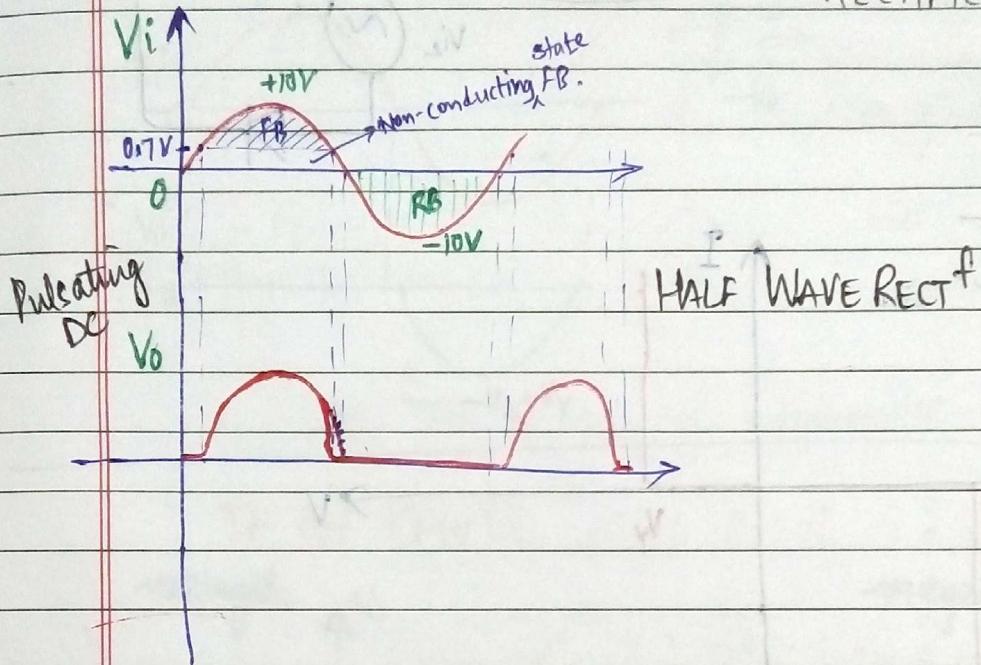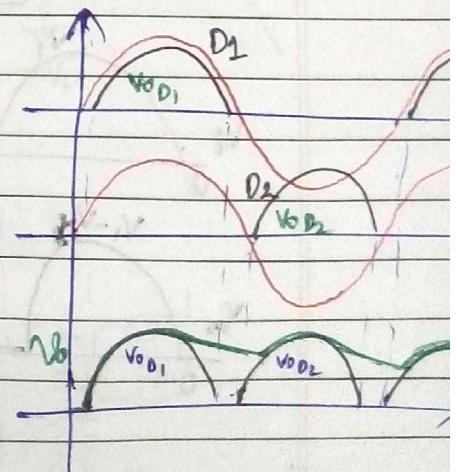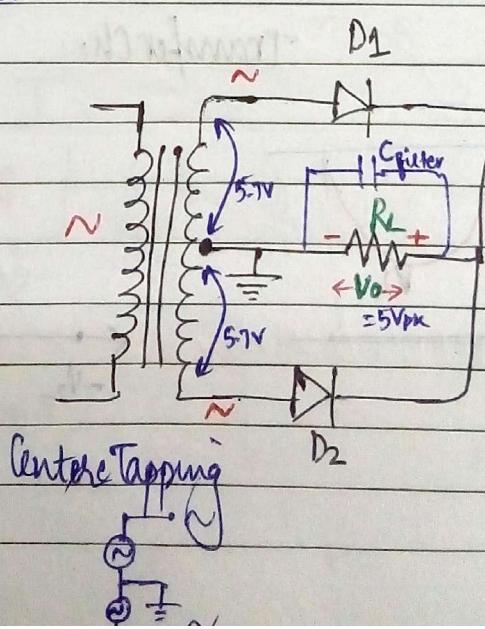
RECTIFICATION  $\rightarrow$  AC  $\rightarrow$  DC||  $\rightarrow$  Iron Core||  $\rightarrow$  Ferride Core  
(High freq)||  $\rightarrow$  Air Core

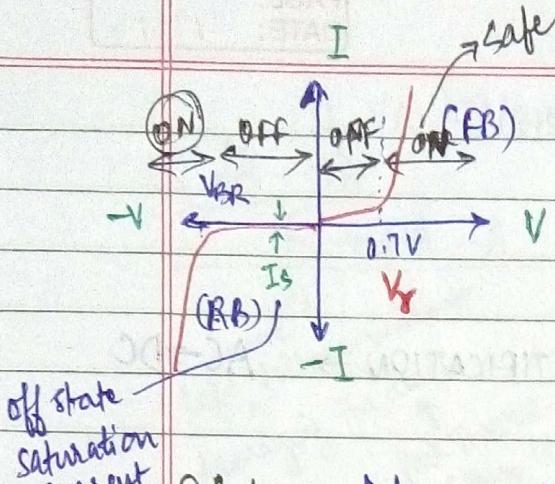



off state  
saturation current

Diode



ON OFF

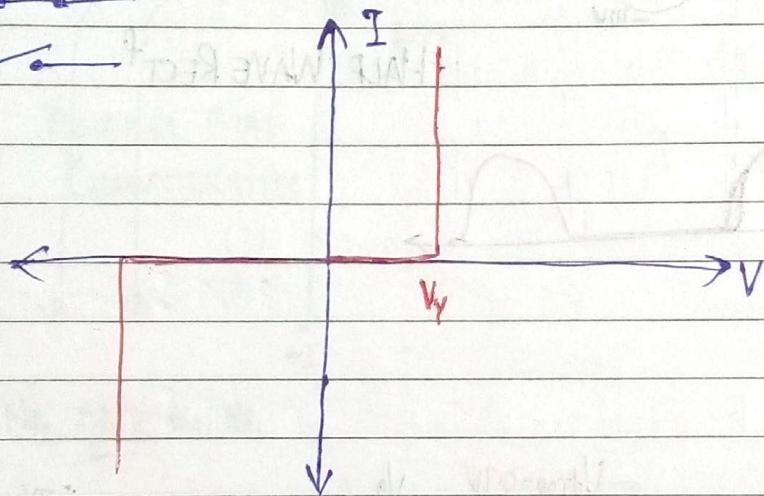


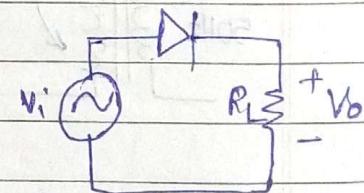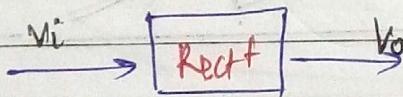Piece-wise linear V-I ch. (A very little current is assumed to be zero)  
of Diode.




Transfer ch.

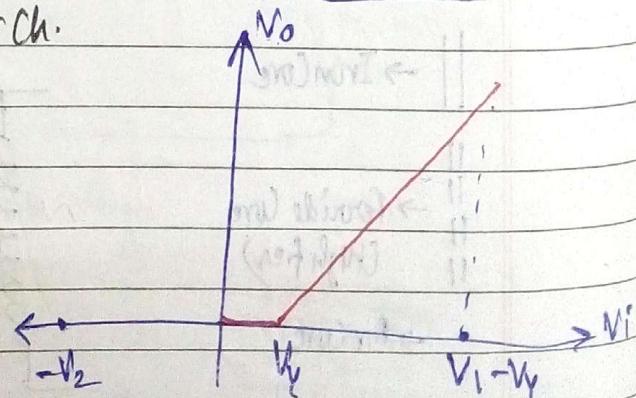
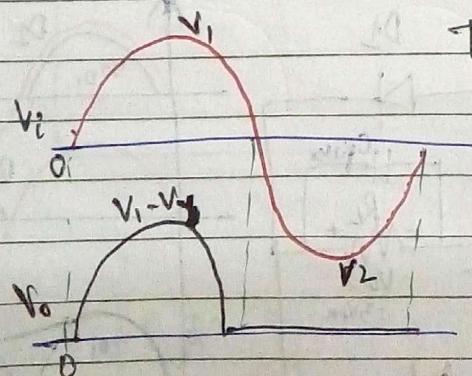


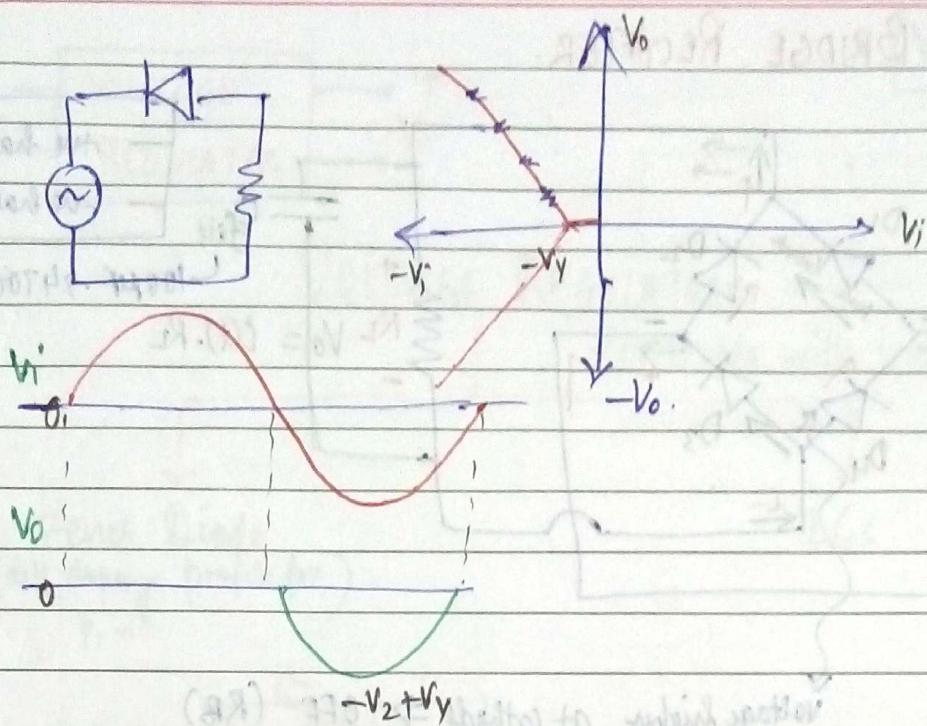


TF CH (CW)

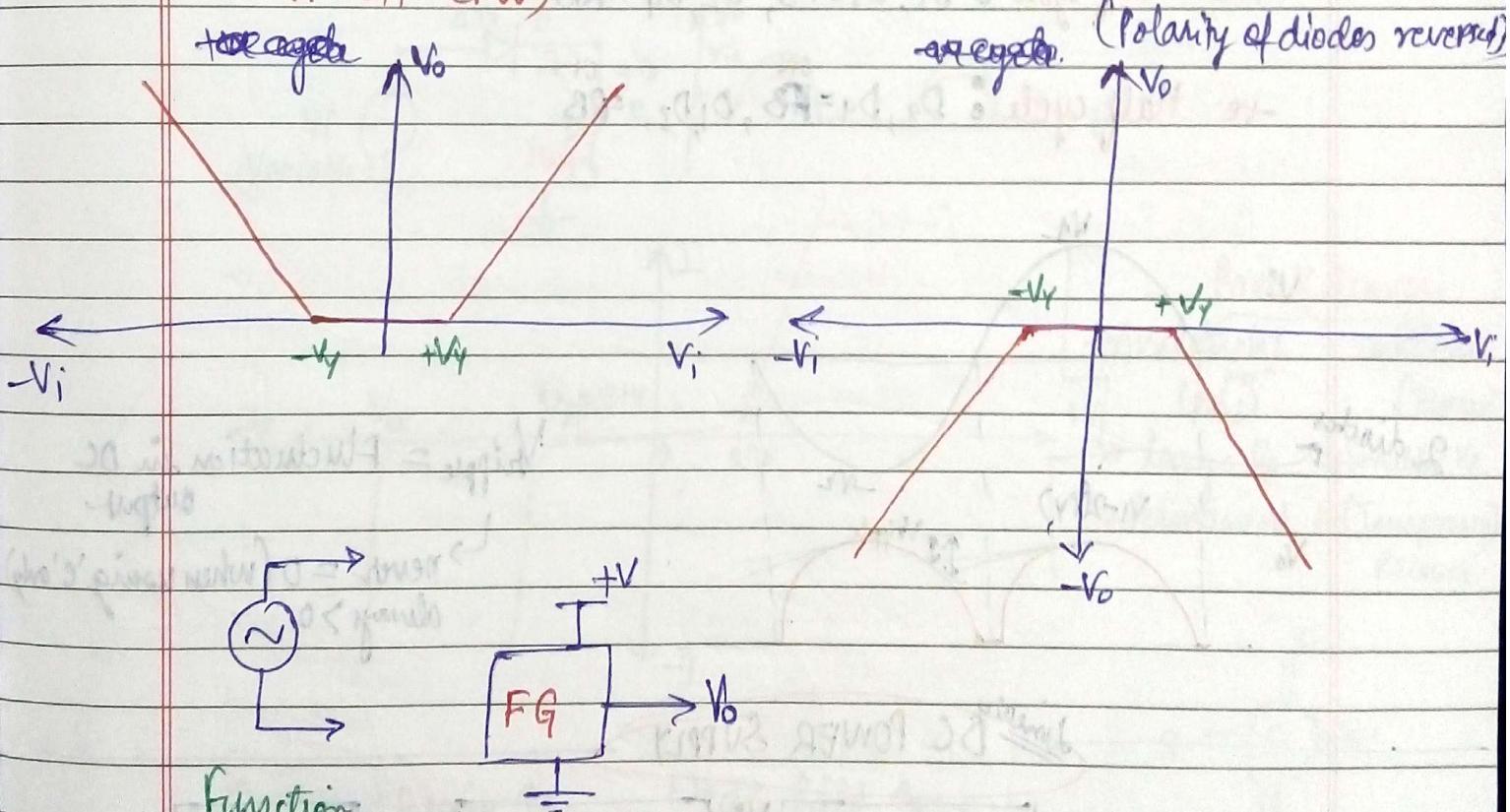Function  
Generator

(No input, only output)

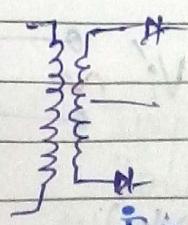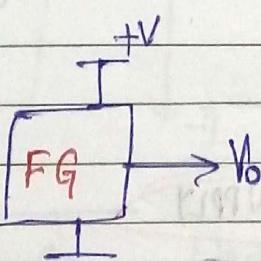


## BRIDGE RECTIFIER.

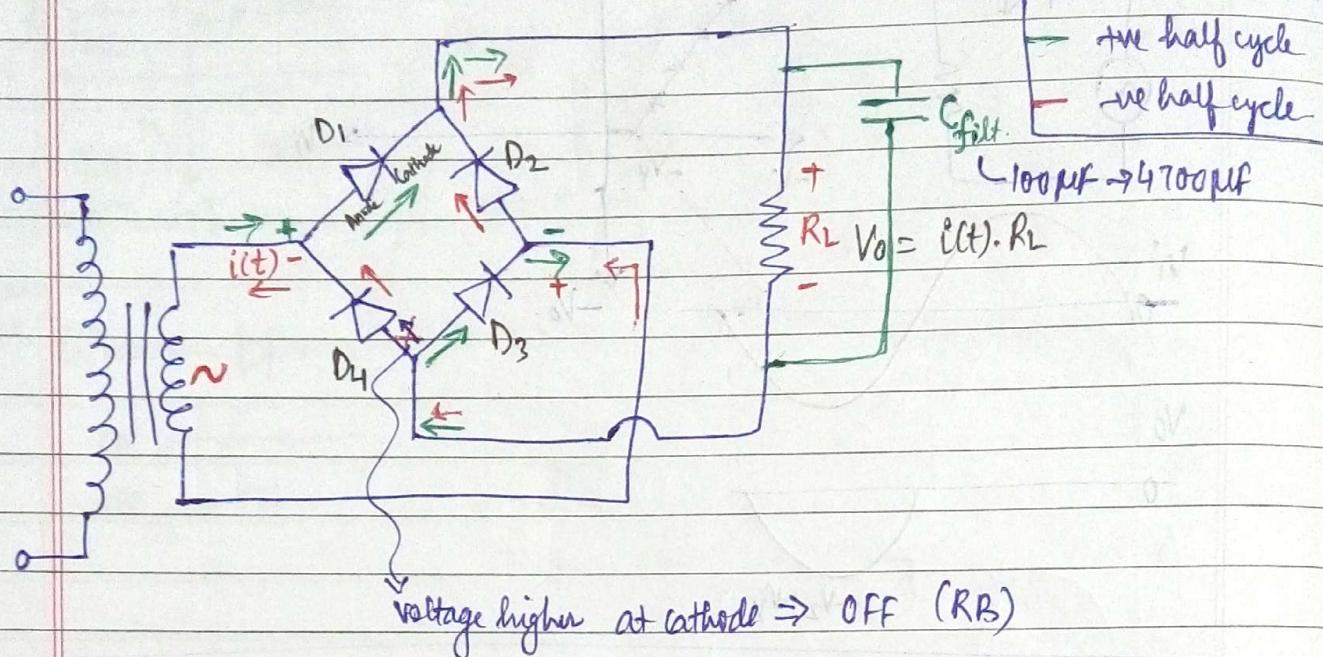

+ve Half cycle :  $D_1, D_3 = \text{ON}$ ,  $D_2, D_4 = \text{OFF}$

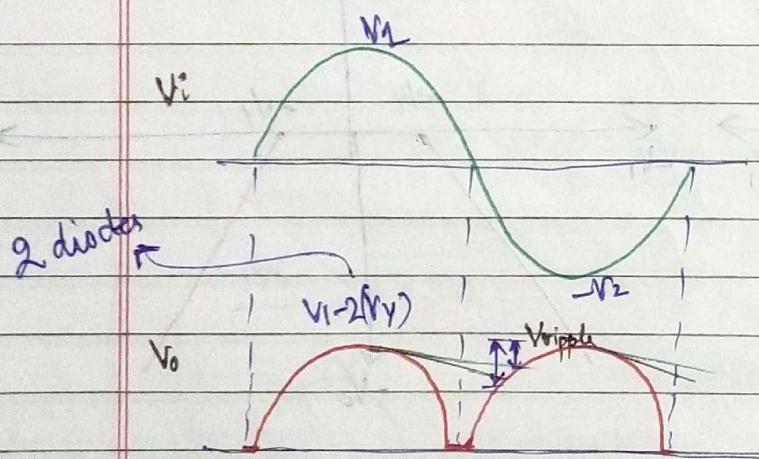
-ve Half cycle :  $D_2, D_4 = \text{ON}$ ,  $D_1, D_3 = \text{OFF}$




Nipple = Fluctuation in DC output

$\hookrightarrow$  never = 0 (when using 'C' only)  
always  $> 0$

linear DC POWER SUPPLY

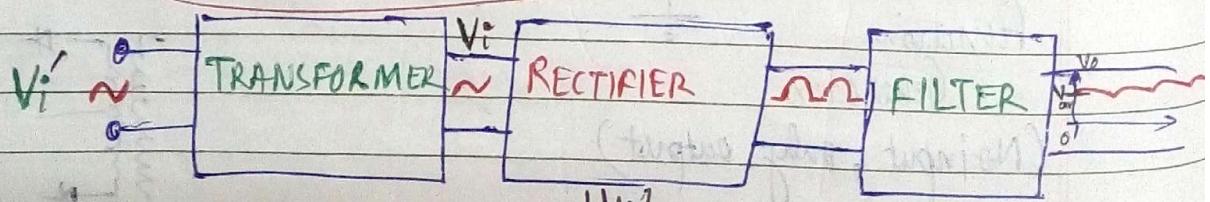

HW  
FW  
BR

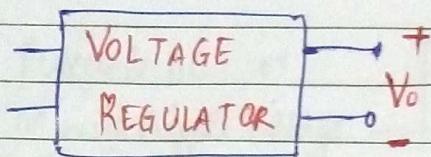

$$V_i > V_o$$





04/08/16

## VOLTAGE REGULATORS


Zener Diode  
(diff doping profile for)  
p, n

const  $V_o$  with variable  $V_i$   $\rightarrow V_i \rightarrow Z_L$

ICs

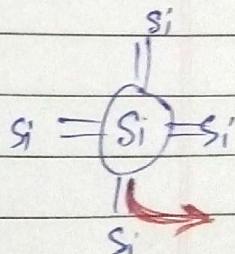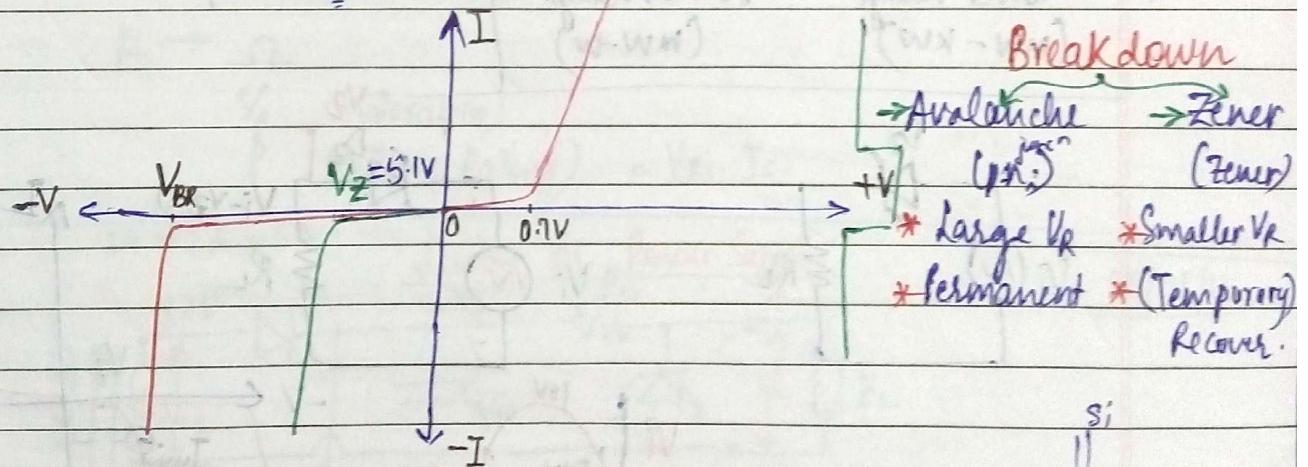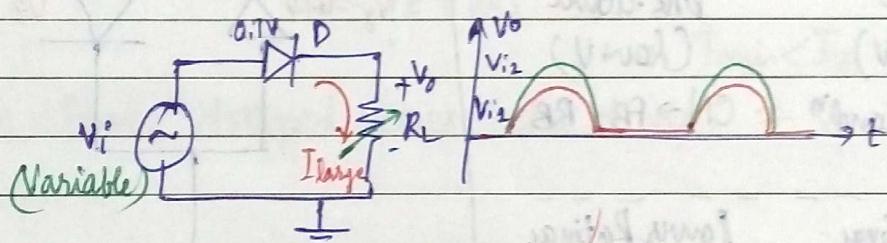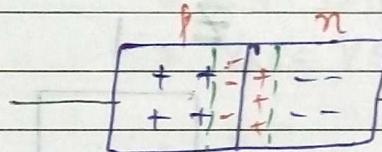

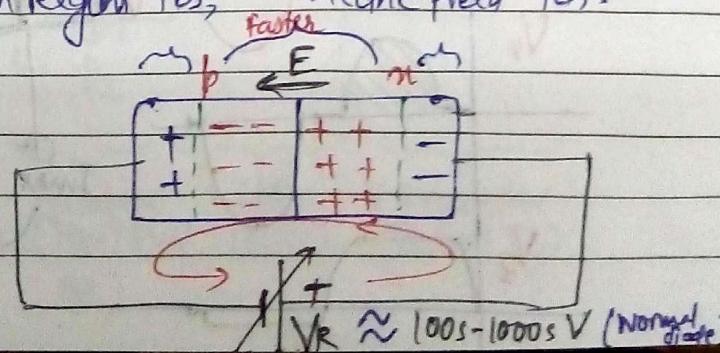Depletion Region Yes, Electric field Yes.




Impact Ionization


(Heavily accelerated beyond  
V<sub>BR</sub>)

ANUBHAJAIN  
NOTES


## Zener

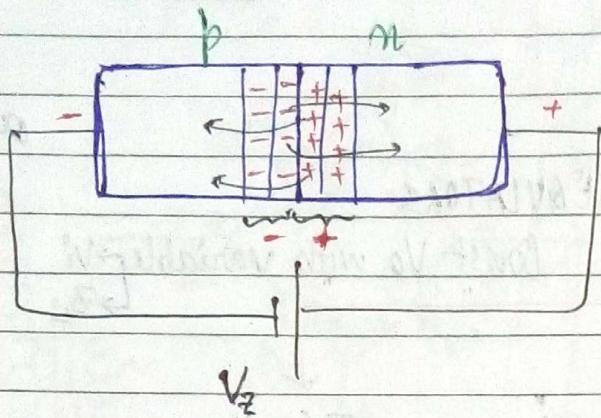

1.  $\text{PN}$

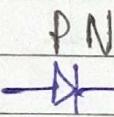

$Z$

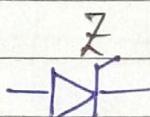

(Configuring output (b))

2. Avalanche

brk-down  
(High V)

3. ON  $\rightarrow$  FB cond<sup>n</sup>

OFF  $\rightarrow$  RB  
Power Ratings  
(mW - kW)

Zener





brk-down  
(Low V)

ON  $\rightarrow$  FB, RB


Power Ratings  
(mW - W)

$V_y = 0.7\text{V}$

$V_z = 5.1\text{V}$

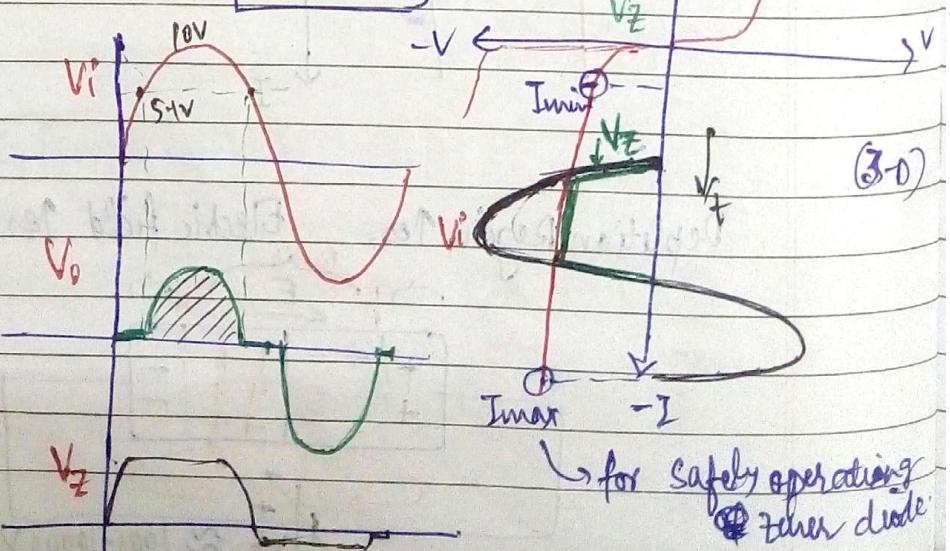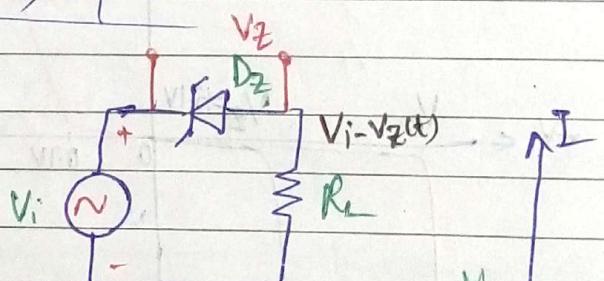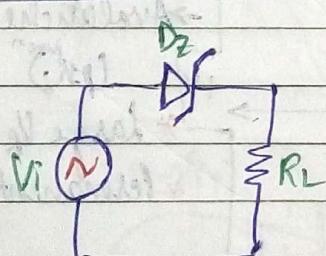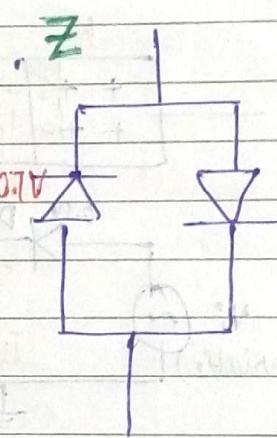

Pulsatile DC or  
DC with Ripple Voltage

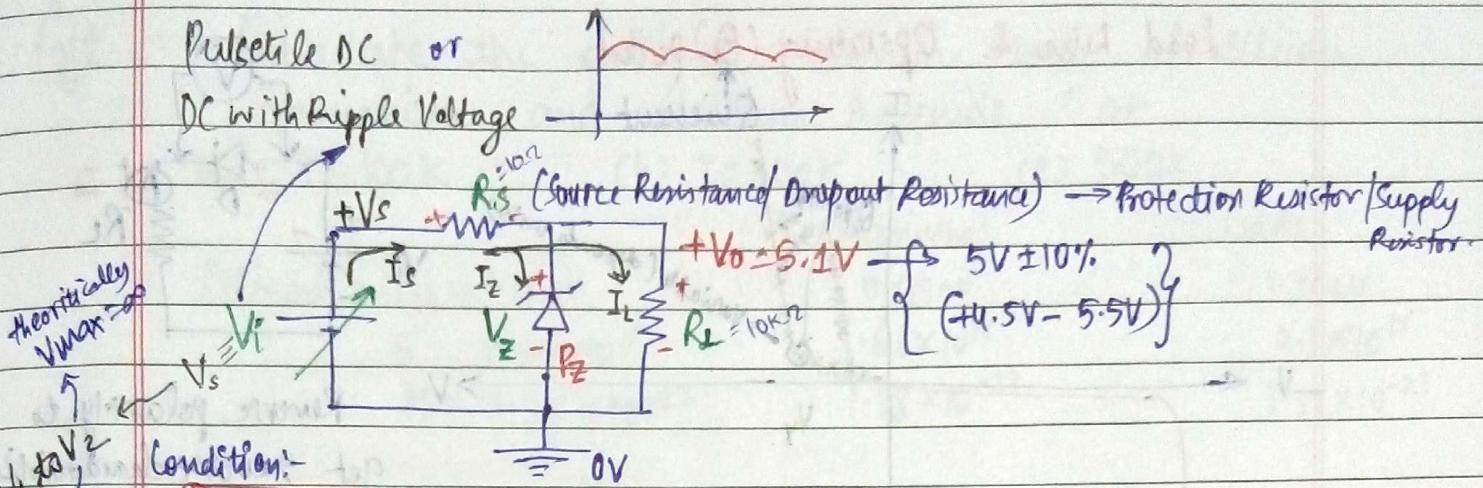

$$* I_s = I_z + I_L$$

$$* V_{RS} = V_s - V_z$$

$$I_s = \frac{V_s - V_z}{R_s}$$

$$R_s = \frac{V_s - V_z}{I_s}$$

$$* V_s = V_z + V_{RS}$$


$$* I_{min} < I_z \leq I_{max}$$

\*  $P_z = \text{Power dropped across zener diode} = V_z \cdot I_z$ . (specified by manufacturer)

$$R \rightarrow \Omega$$

% (Tolerance)
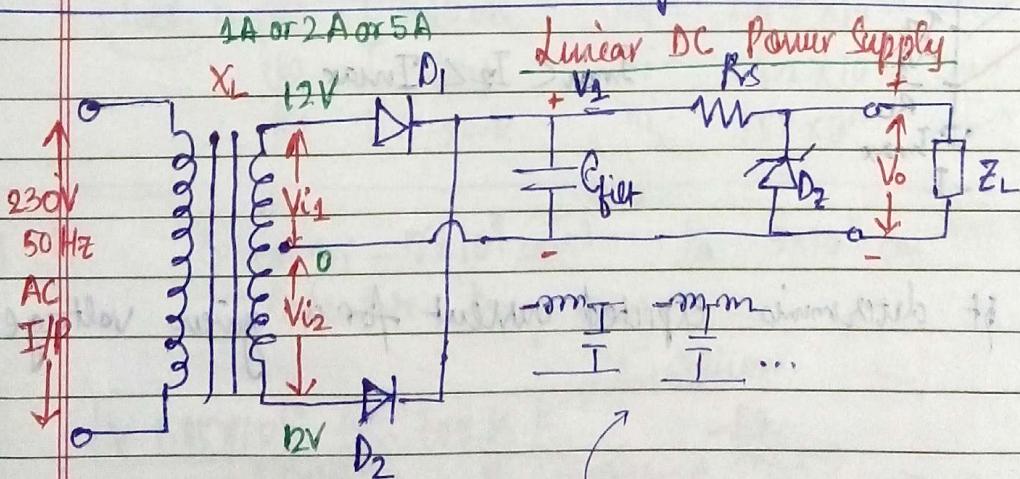
$$P \text{ (Power Rating)} = V_{RS} \cdot I_s$$




Transformer  
(Stepup/dn)  
(BR)

Rectifier  
(H/W/PW/BR)

filter  
(C/LC)

V Regulator  
(Zener/IC)


## Load Line & Operating ( $Q$ ) point

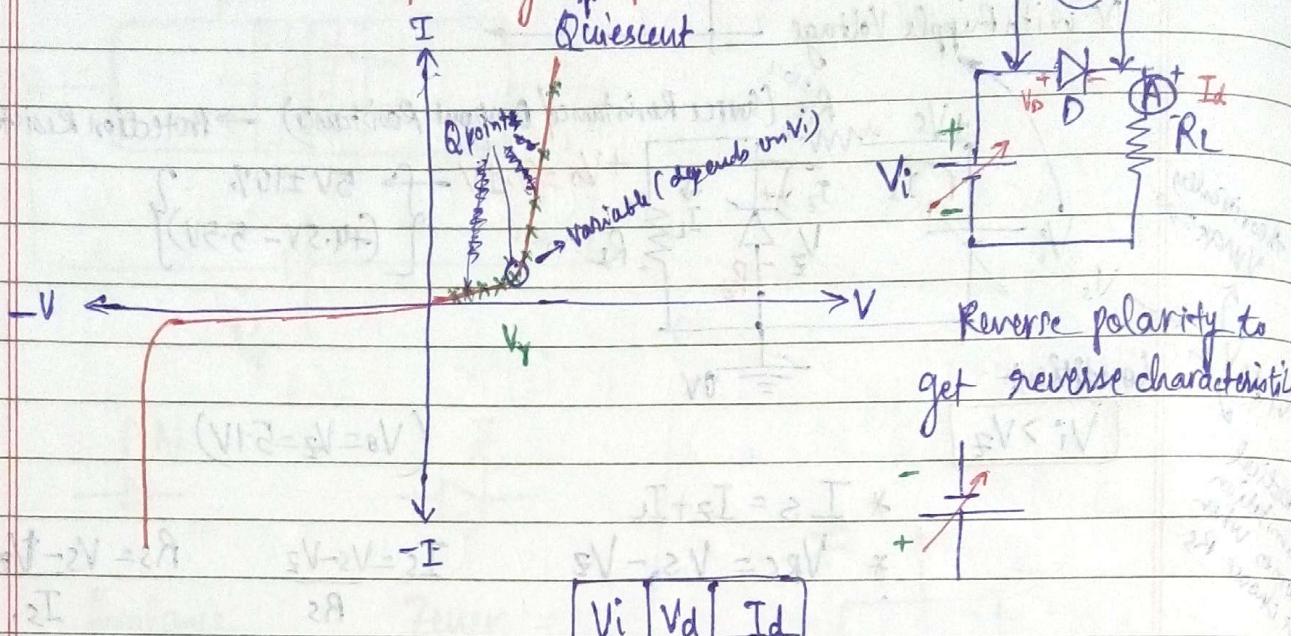

$V_i$	$V_d$	$I_d$
0	-	-
0.1	-	-

$$I_S = I_Z + I_L$$

$$I_S = I_Z + \frac{V_o}{R_L}$$

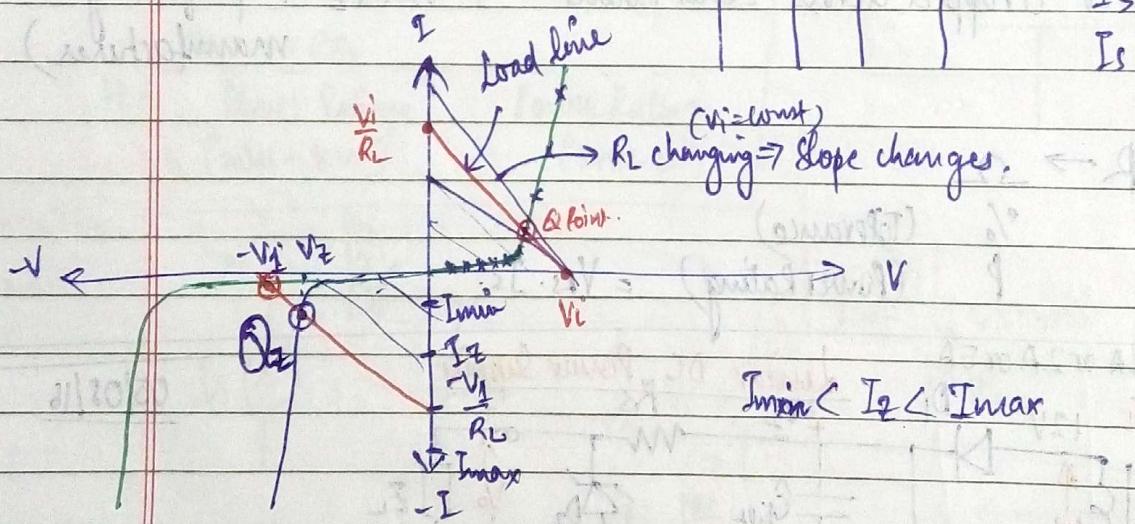

$$I_{min} < I_Z < I_{max}$$

$Q$  pt determines expected current for a given voltage.

Q1. Calculate the intrinsic carrier conc of silicon, Germanium and Gallium Arsenide at

(a)  $T=100\text{K}$  (b)  $T=300\text{K}$  (c)  $500\text{K}$ .

Silicon:  $E_g = 1.12\text{eV}$

$$B = 5.23 \times 10^{15}$$

$$K = 1.38 \times 10^{-23}$$

Germanium

$$0.67\text{eV}$$

$$1.66 \times 10^{15}$$

$$1.38 \times 10^{-23}$$

GaAs

$$1.42\text{eV}$$

$$2.1 \times 10^{14}$$

$$1.38 \times 10^{-23}$$

Ans.

$$n_i = BT^{3/2} e^{-E_g/2kT}$$

(a)

Si,

$T=100\text{K}$

$$n_i = 3.317 \times 10^{10} \text{ cm}^{-3}$$

(normal calculation)

$$n_i = 2.74 \times 10^{10} \text{ cm}^{-3}$$

TRICK

$$E_g \rightarrow \text{eV}$$

$$k \rightarrow B \cdot 6 \times 10^{-5} \equiv \frac{K}{e}$$

$$(b) T=300\text{K} n_i = 1.0177 \times 10^{10}$$

$$(c) T=500\text{K} n_i = 1.29 \times 10^{14}$$

Ge

$$(a) T=100\text{K} n_i = 20.08 \text{ cm}^{-3}$$

$$(b) T=300\text{K} n_i = 1.98 \times 10^{13} \text{ cm}^{-3}$$

$$(c) T=500\text{K} n_i = 7.67 \times 10^{15} \text{ cm}^{-3}$$

GaAs

$$(a) T=100\text{K} n_i = 293 \times 10^{19} \text{ cm}^{-3}$$

$$(b) T=300\text{K} n_i = 1.22 \times 10^{16} \text{ cm}^{-3}$$

$$(c) T=500\text{K} n_i = 1.58 \times 10^{11} \text{ cm}^{-3}$$

Q1(c)

$$\text{Given } n_i = 5 \times 10^9 \text{ cm}^{-3} \xrightarrow{293\text{K}} \text{ to } 5 \times 10^{11} \text{ cm}^{-3} \xrightarrow{300\text{K}}$$

Calculate temp range.

for Silicon.

$\nexists 1.85 \times 10^{10} \text{ at } 300\text{K}$

$$1.85 \times 10^{10} = B (300)^{3/2} e^{-E_g/2k(300)} \Rightarrow B \cdot C \frac{-E_g}{2k(300)} = 2886751.346$$

$$5 \times 10^9 = B T^{3/2} e^{-E_g/2kT}$$

Use Trial and error method.

$$\frac{n_0}{B} = T^{3/2} \cdot \exp \left( \frac{-E_g}{2k} \cdot \frac{1}{T} \right) = \text{const.} T^{3/2} \cdot \exp \left( -\frac{K_2}{T} \right)$$

$$T = 290 \text{ K}, \quad n_i = 4.57 \times 10^9 \text{ cm}^{-3}$$

$$\Rightarrow T=291\text{ K}, \quad n_i = 4.969 \times 10^9 \text{ cm}^{-3} \Rightarrow n_i \approx 5 \times 10^9 \text{ cm}^{-3}$$

$$T = 3500 \text{ K}, \quad n_i = 2.85 \times 10^{11} \text{ cm}^{-3}$$

$$m_i = 2.85 \times 10^{11} \text{ cm}^{-3}$$

$$m_i = 4.98 \times 10^{11} \text{ cm}^{-3} \Rightarrow m_i \approx 5 \times 10^{11} \text{ cm}^{-3}$$

(iii) Silicon is doped with  $5 \times 10^{16} \text{ cm}^{-3}$  Arsenic atoms. Calculate the electron and hole conc. at 300K and 350K.

$$N_d = 10^{16} \text{ cm}^{-3}, \quad \rho_i = 1 \text{ g cm}^{-3}$$

$$\mu_0 = 1.5 \times 10^{10} \text{ a.u.} (300 \text{ K})$$

$$\text{At } T=300\text{K, } n_i = 1.0177 \times 10^{10} \text{ cm}^{-3}$$

$$\Rightarrow p_i = 2071.426 \text{ cm}^{-3}$$


$$\text{at } T=350\text{ K, } n_i = 2.85 \times 10^{11} \text{ cm}^{-3}$$

$$\Rightarrow p_i = 1624500 \text{ atm}^{-3}$$

$$1.61 \times 10^6 \text{ cm}^{-3}$$

	$E_g$	$\mu_n$	$\mu_p$	$(\text{cm}^2/\text{V}\cdot\text{s})$
Si	1.12 eV	1350	480	
Ge	0.67 eV	3900	1900	
GaAs	1.42 eV	8500	400	
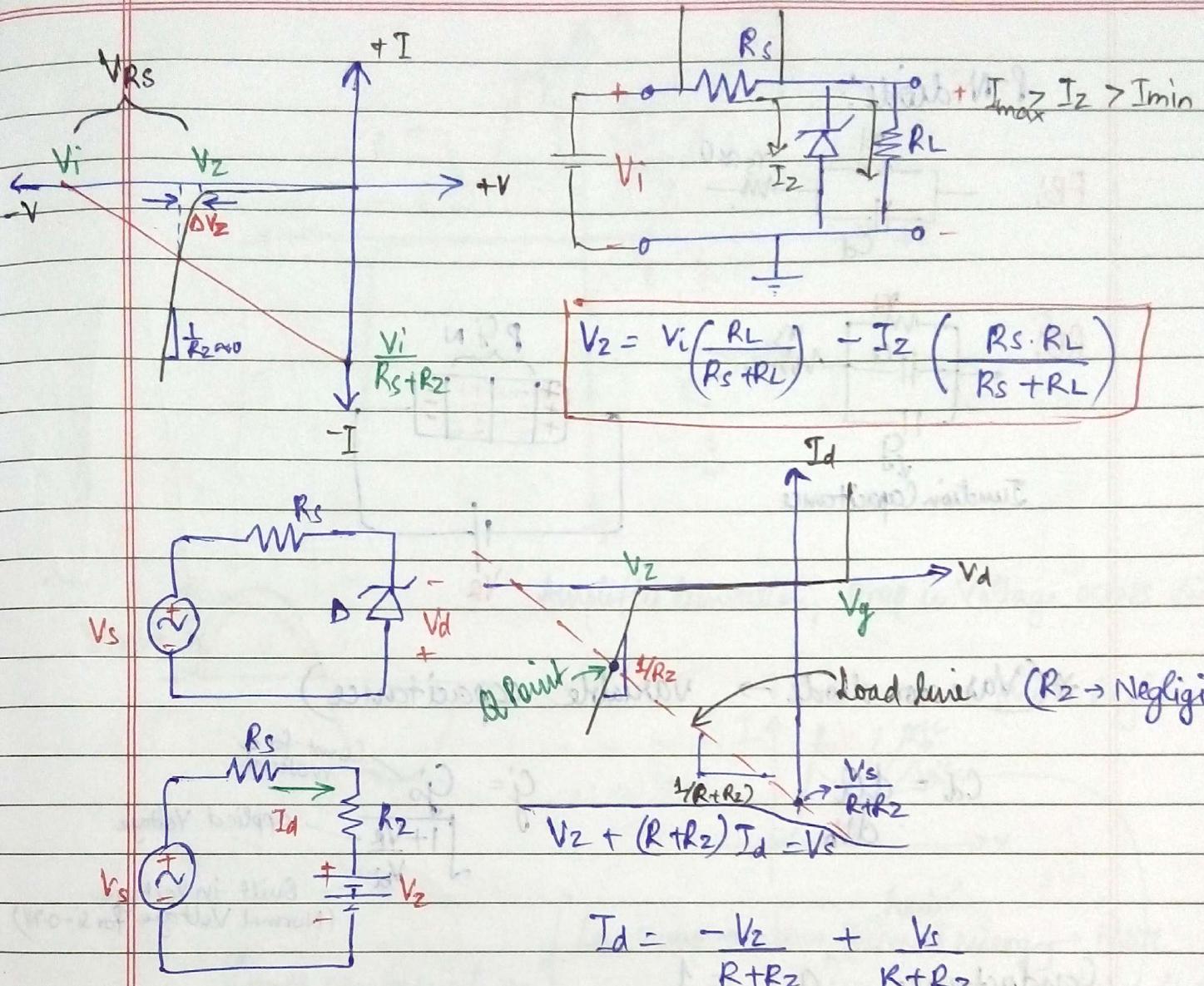
$$\frac{KJ}{e} = \frac{Dn}{fun} = \frac{Dp}{fup} \rightarrow \text{cm}^2/\text{s.}$$



Input Voltage, Regulation accuracy


Quality of Regulation :-


$$1) \text{ Line / Source of Reg} = \frac{\Delta V_o}{\Delta V_i} \times 100\% \quad (\text{should be less than } 8\%)$$

$$2) \text{ Load Reg.} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$




$R_2 > 0 \rightarrow \text{finite slope,}$   
 $\text{little change in } V_2 \text{ causes high change in } I$

Eq. Representation of Zener diode :-

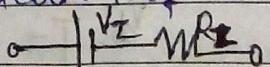\*  $R_B$  

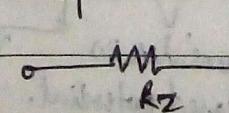\*  $F_B$  

P-N diode:

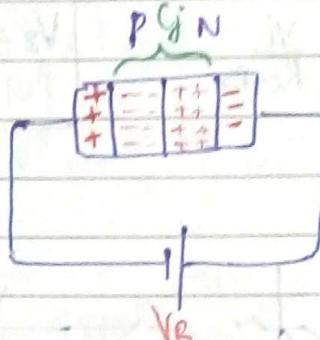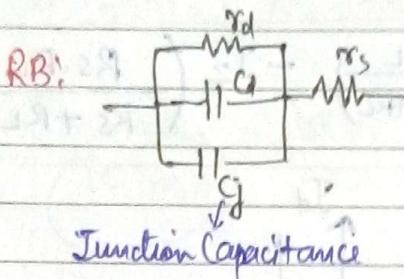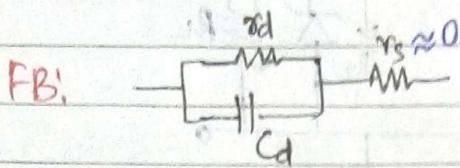

\* (Varactor diode  $\rightarrow$  variable capacitance)

$$C_d = \frac{dQ}{dV_b}$$

$$G = \frac{G_0}{\sqrt{1 + \frac{V_R}{V_{bi}}}} \quad \begin{matrix} \text{constant for a} \\ \text{material} \end{matrix}$$


applied Voltage

Built-in Voltage  
(Normal Voltage for Si - 0.7V)


Conductance,  $g_m = \frac{1}{r_d}$   
(Inverse of Resistance)


AC equivalent of Conductance  $\rightarrow$  Admittance  $y = g_m + j \omega C_d$

Admittance = Conductance + Susceptance


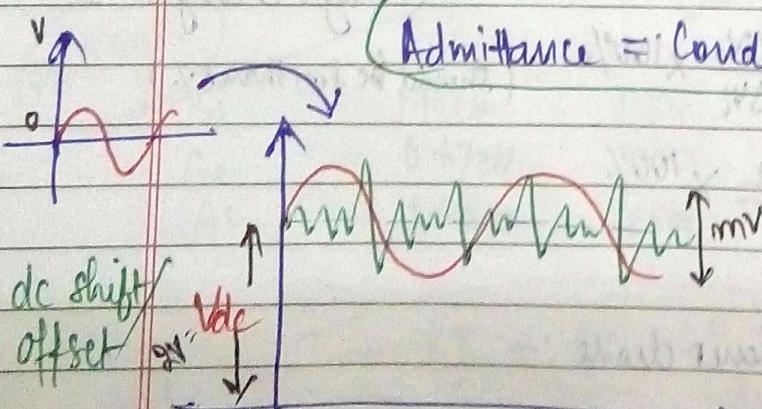


VARIABLE BIAS  
NOTES  
Amplifier

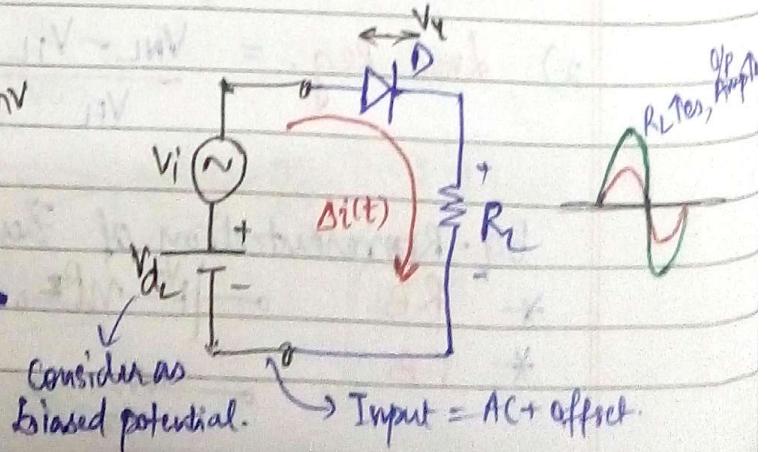

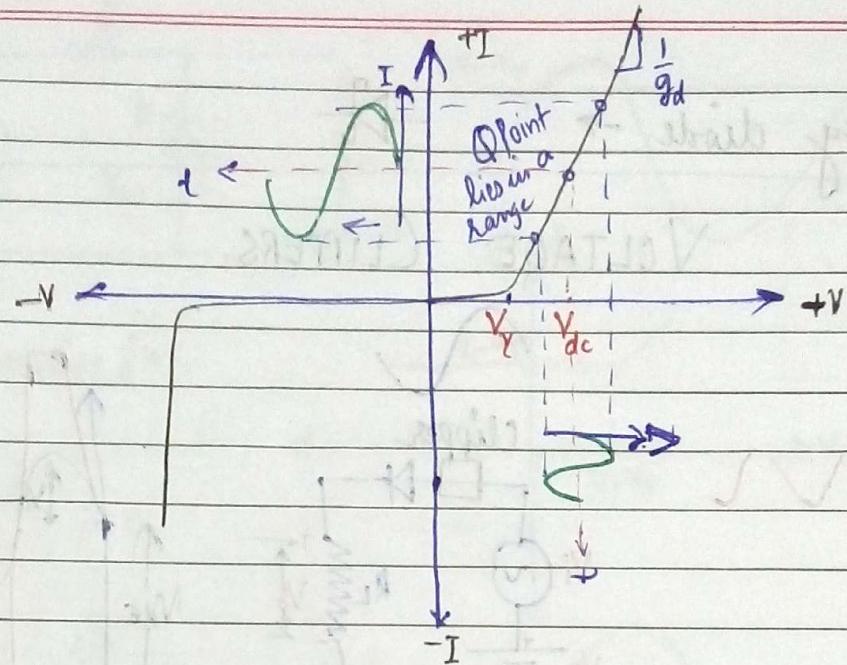

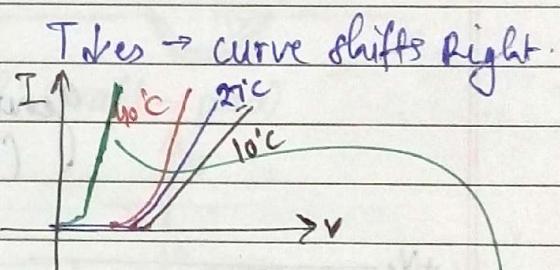
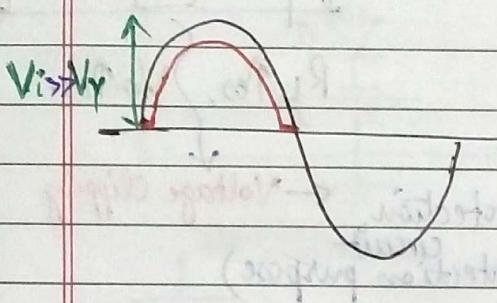
Amplifier limitation: Drop in Voltage across diode.



Diode can be used as a Temperature Sensor.

Low Temp  $\rightarrow$  <sup>heat</sup> low thermal energy  $\rightarrow$  More energy is req'd. to turn it on.

High Temp  $\equiv$  less energy req'd.


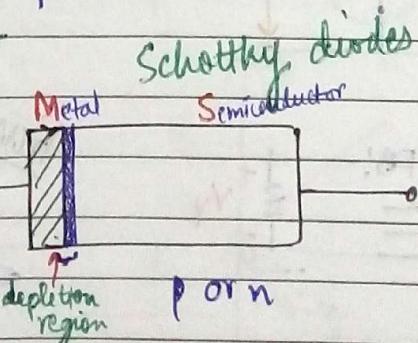
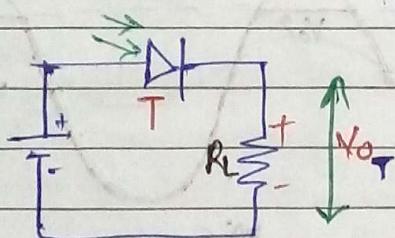


Metal-Semiconductor Junction  $\rightarrow$  nanoscopic level

Schottky diode  $\rightarrow$





## VOLTAGE CLIPPERS

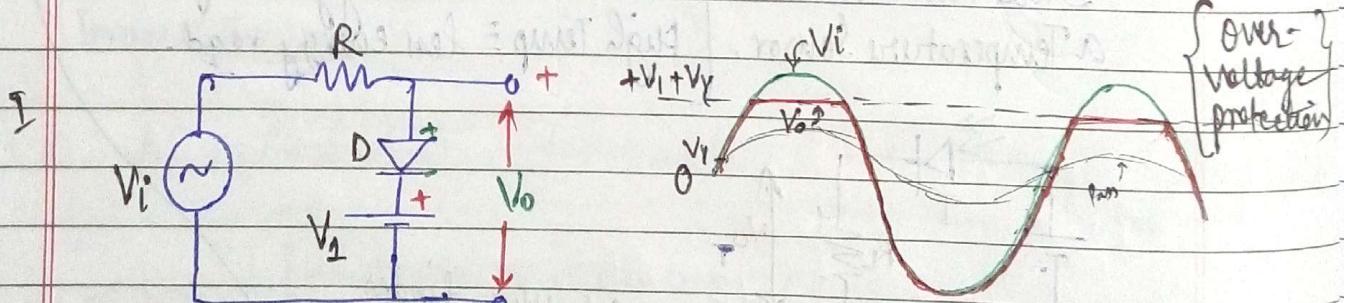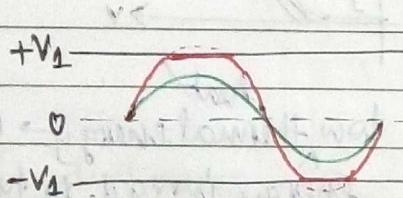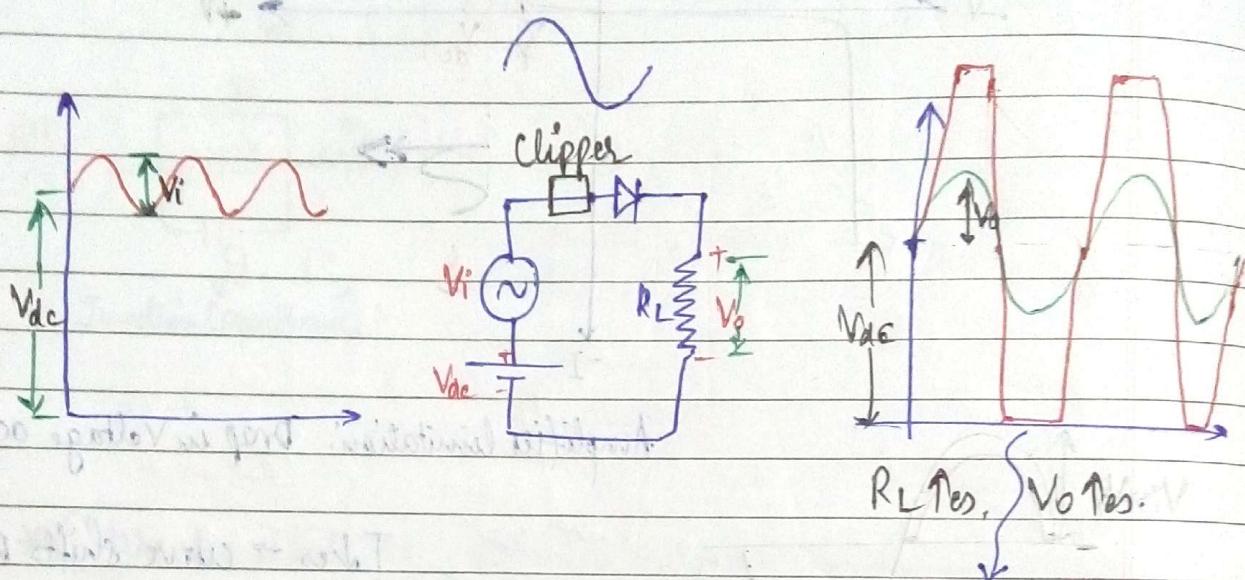


$$FB! = \frac{1}{1 + \frac{V_o}{V_1}}$$

Brackets  $\uparrow$

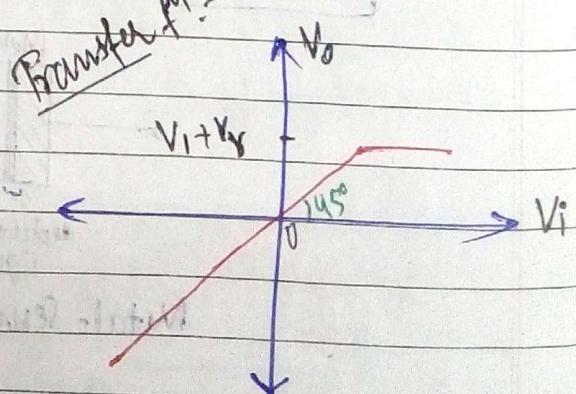


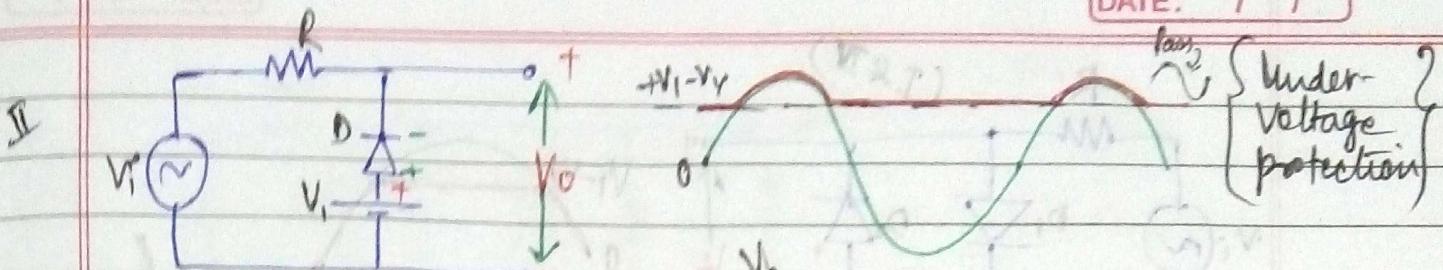


Transfer f/f :-

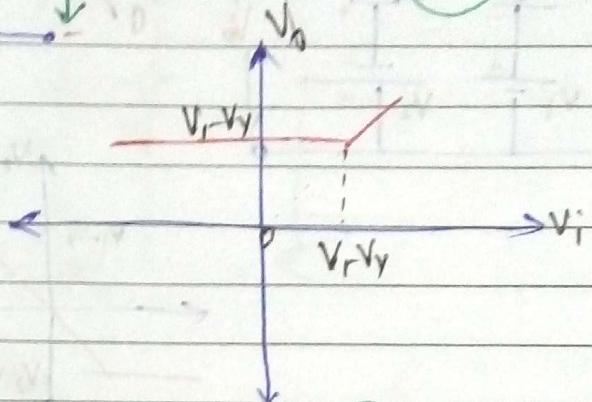


III

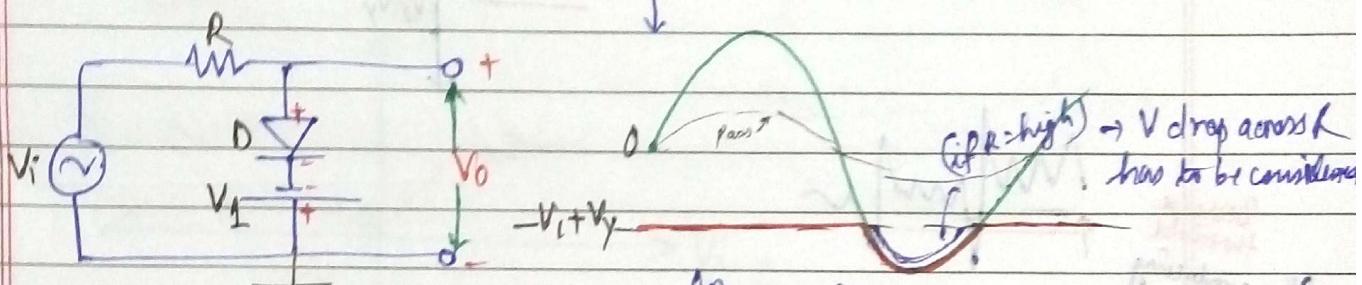


(R=small → peace)

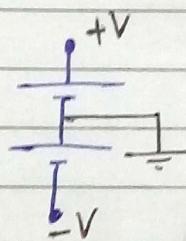


Tf :-


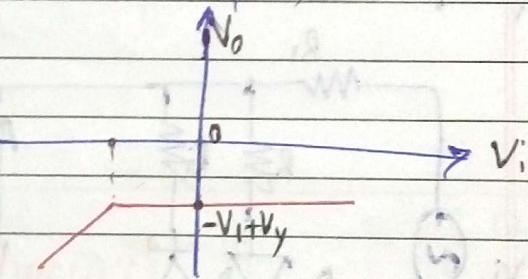


IV

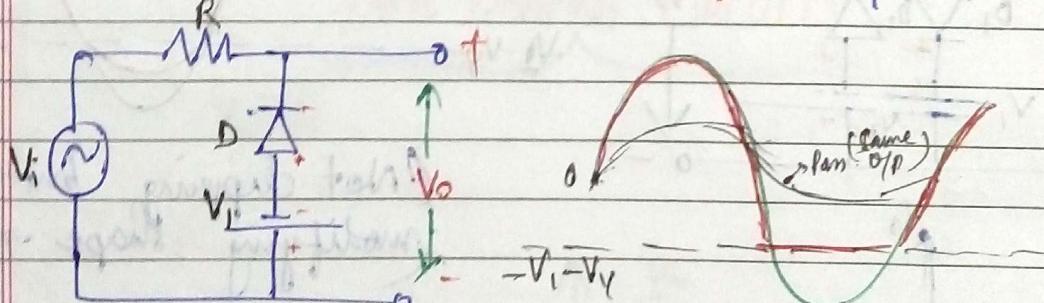


Tf. th :-

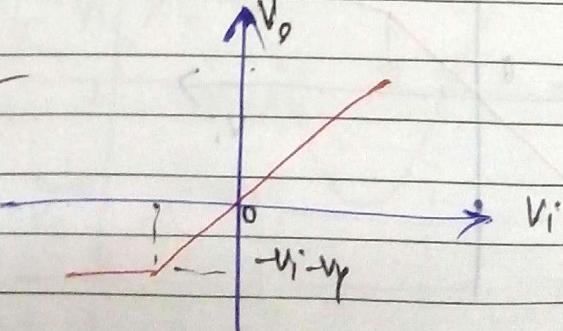


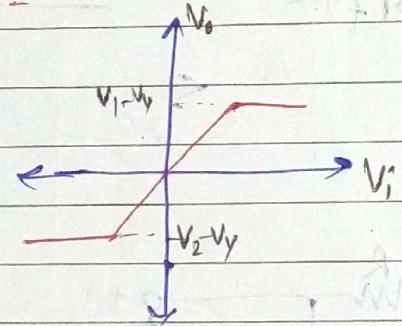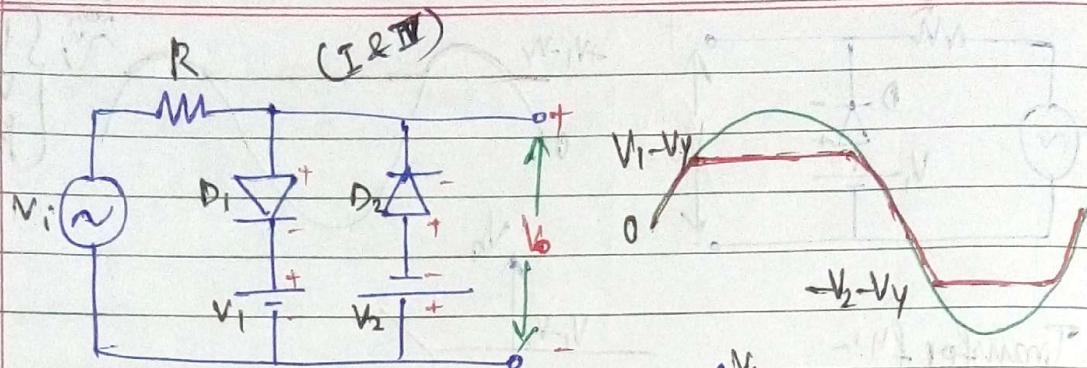

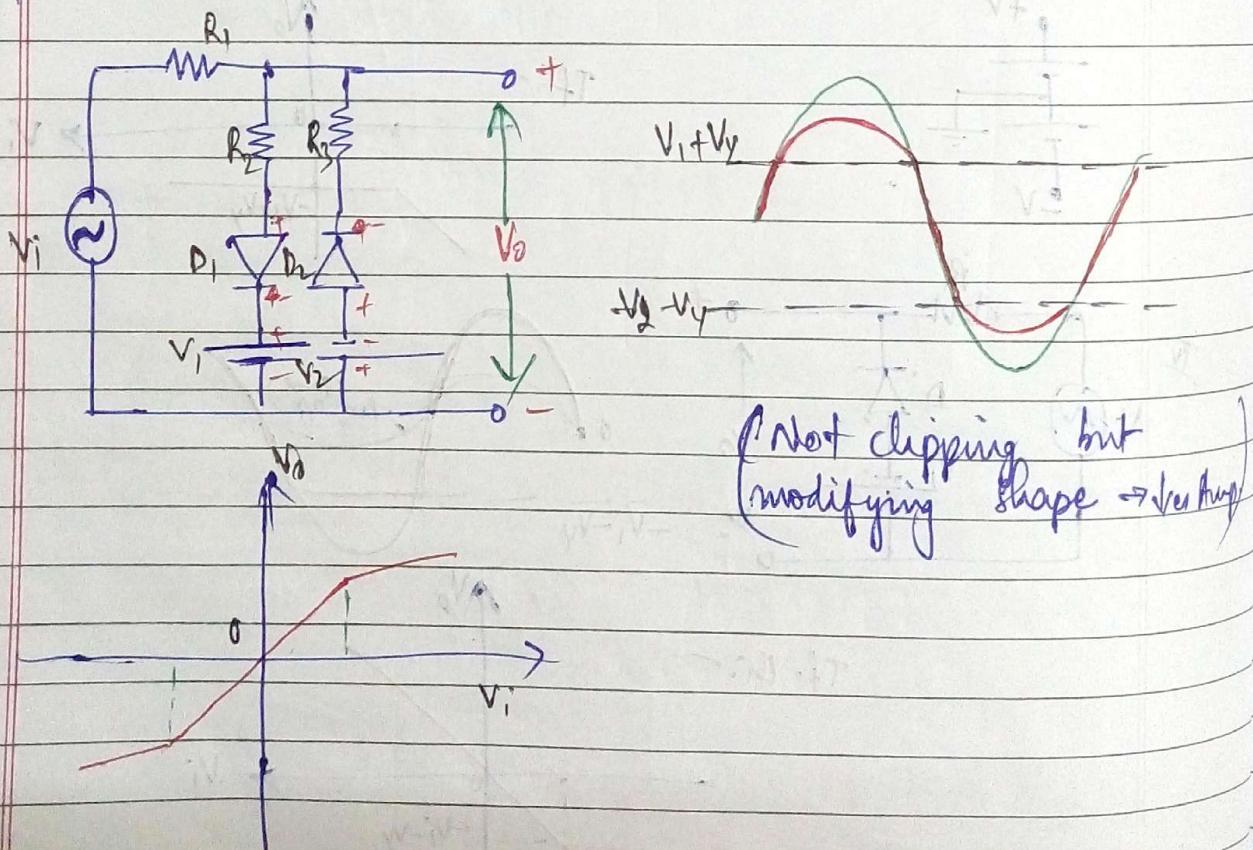Decrease threshold  
(for producing  
no sharp change)




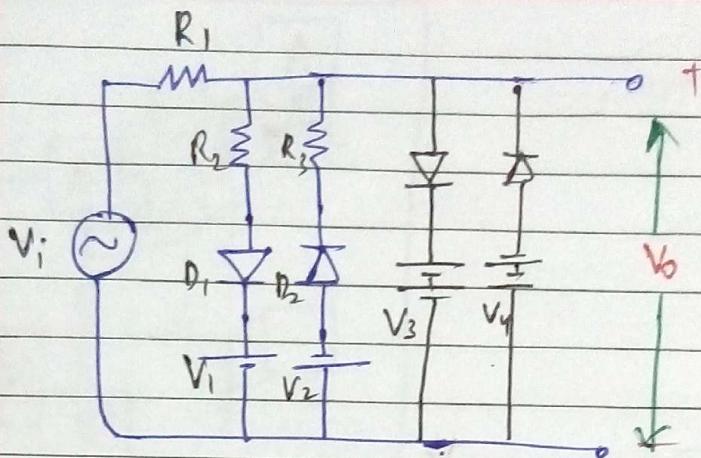Not clipping but  
(modifying shape  $\rightarrow$  Varying)



$$V_3 > V_1$$

$$V_4 > V_2$$

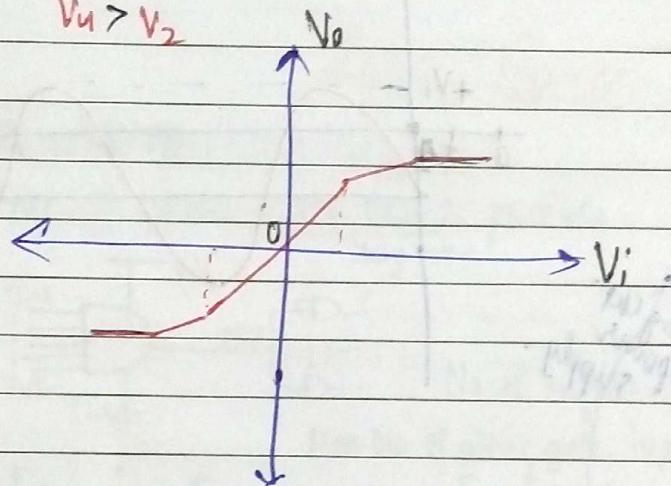

12/08/16





## WAVE SHAPING CIRCUITS

Clipper



Clamper

DC shift


CLAMPER

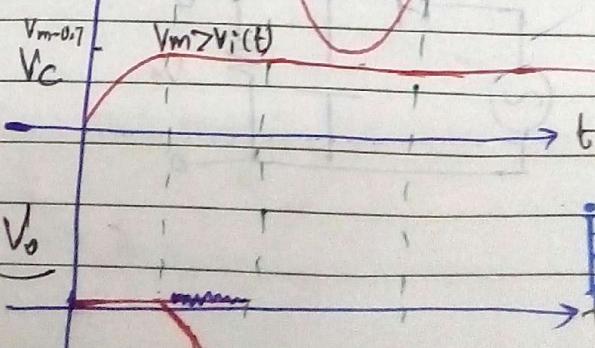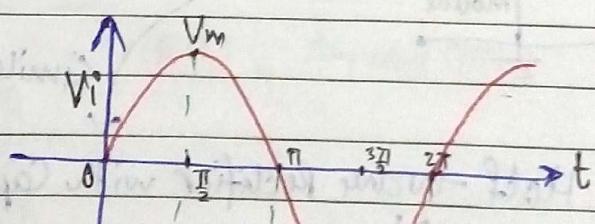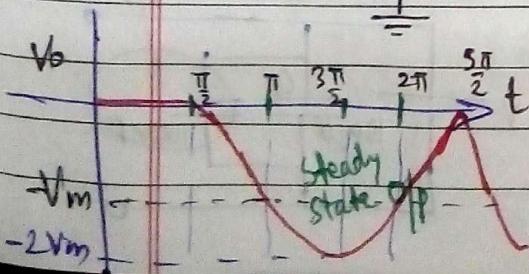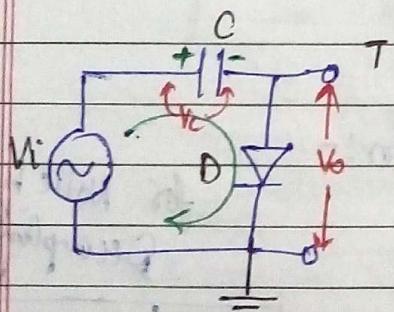

BAJANUBHAJ  
JAIN NOTES

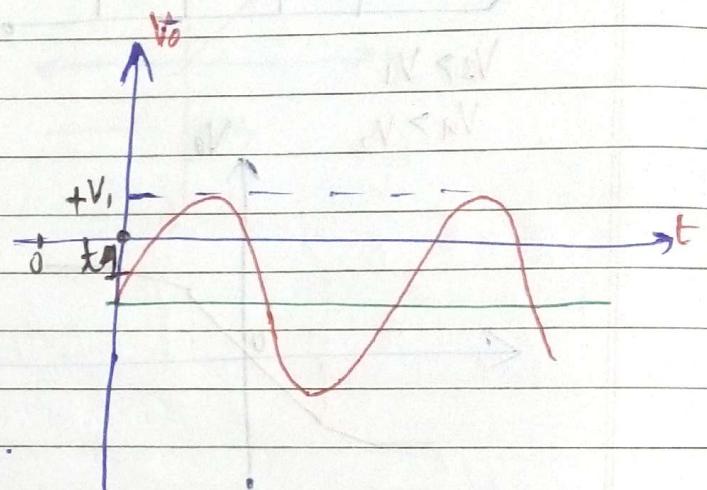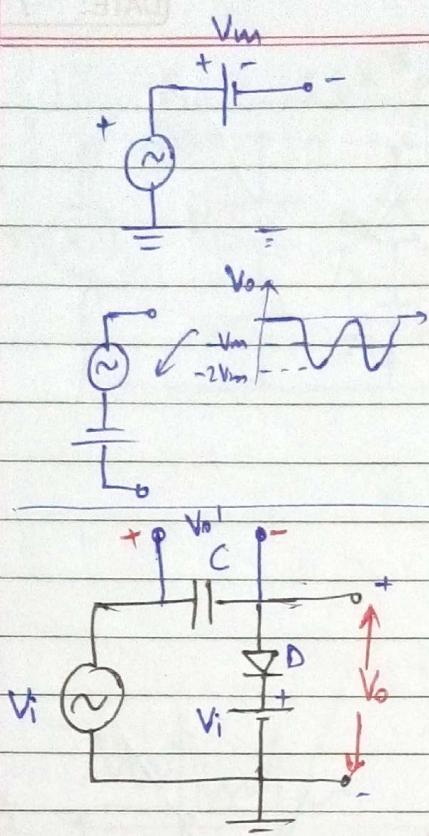


Charging C.R.  
as power supply.

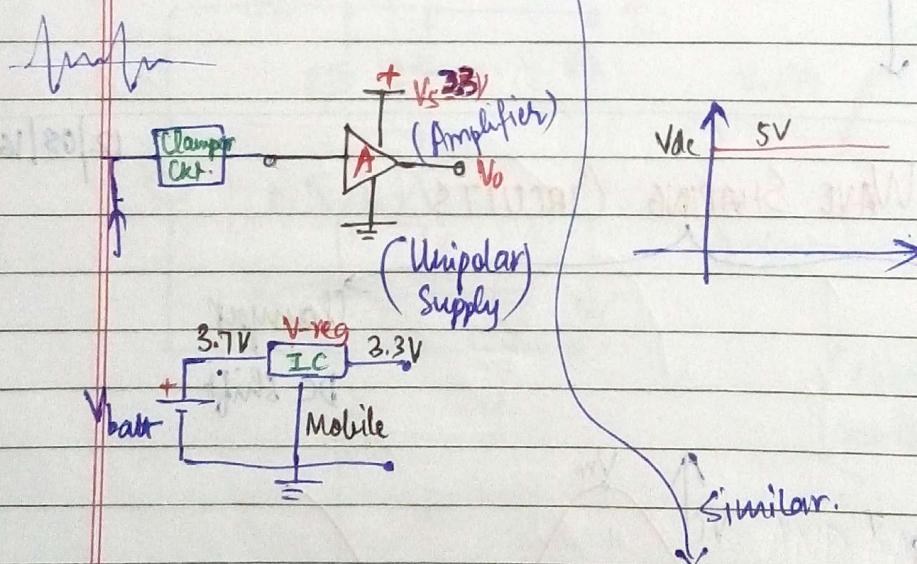


Similar.


Half-wave Rectifier with Capacitor! -

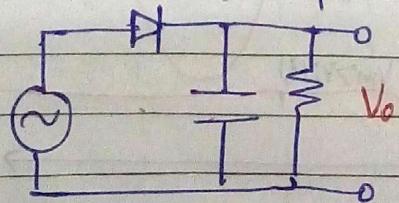

for Noise bypassing  
Decoupling

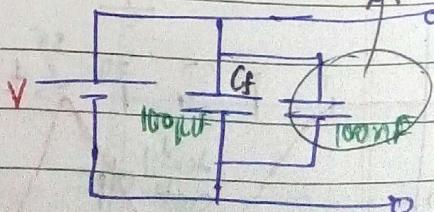


VANSHI  
ANUJ  
JAIN  
NOTES

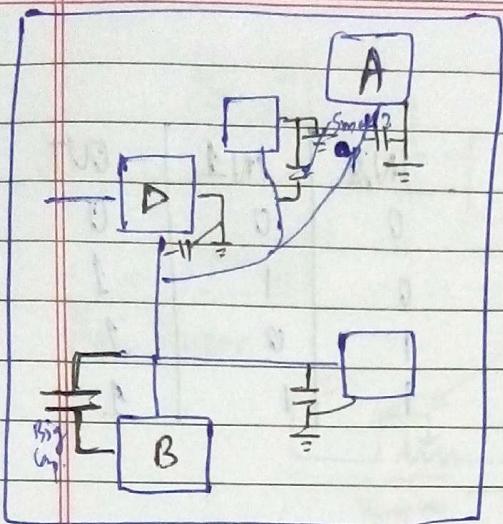
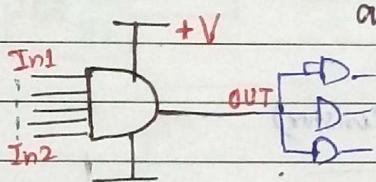
## LOGIC GATES

NOT  $\rightarrow$  1 I/p

Other  $\rightarrow$  2 or More than 2 possible.  
any no.



No. of inputs that can be connected by output  $\rightarrow$  limited

Max. No. of other gate inputs that may be connected

Fan-in = 5

Fan-out =  $\times$


Emitter  
Coupled  
Logic

\* Logic family  $\rightarrow$  TTL, DTL, ECL  
Transistor Transistor Logic, Diode TL  
(+) (+) (-)


\* Noise Margin  $\rightarrow$  1, 0

0  $\rightarrow$  0V (0-0.8V)

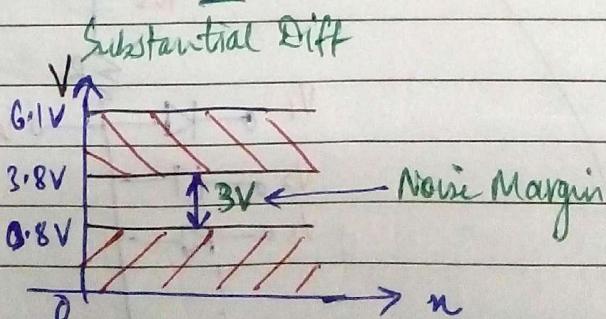1  $\rightarrow$  5V, -5V (ECL), Any value (DTL)  
(4.5-5.5)  
(3.8-6.4V)






## OR GATE

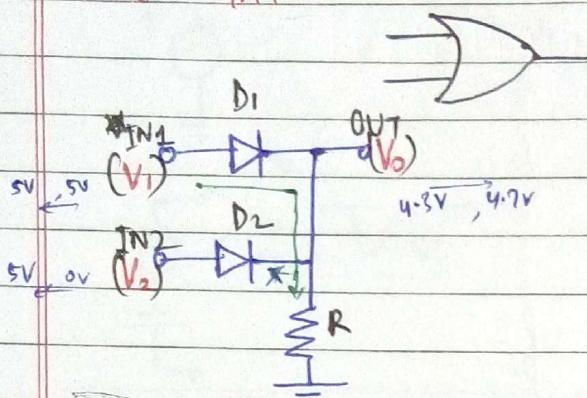



IN <sub>2</sub>	IN <sub>1</sub>	OUT
0	0	0
0	1	1
1	0	1
1	1	1

\* Iterative Design Process.

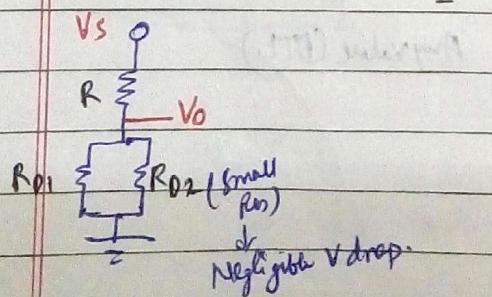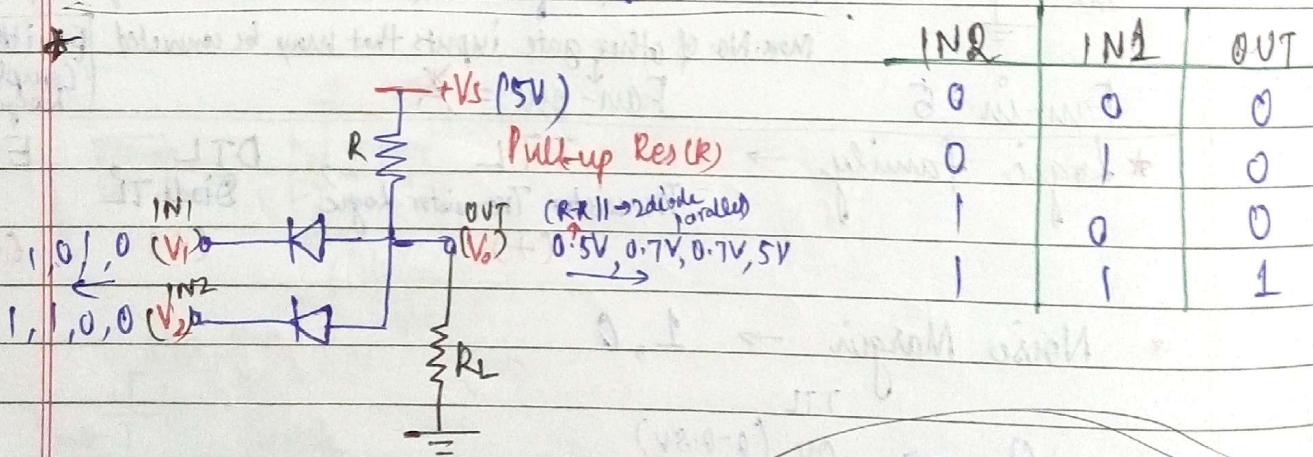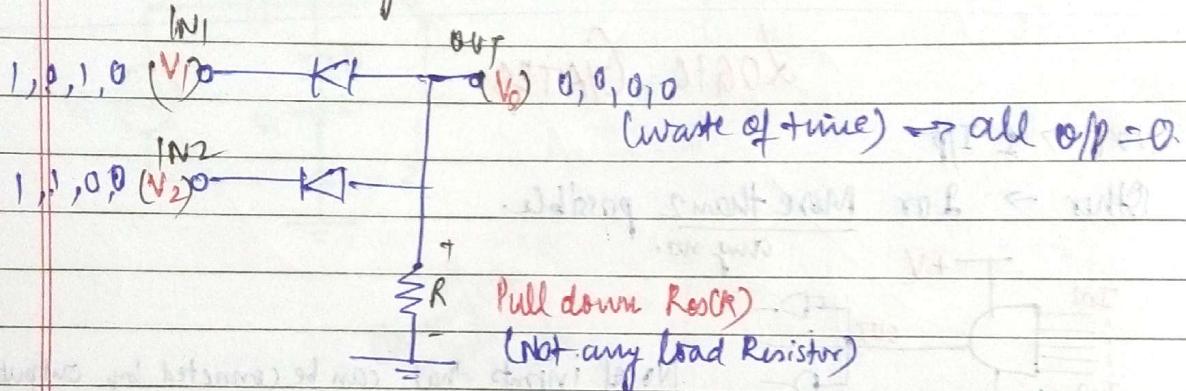

AND GATE:  $FAN-IN = n$

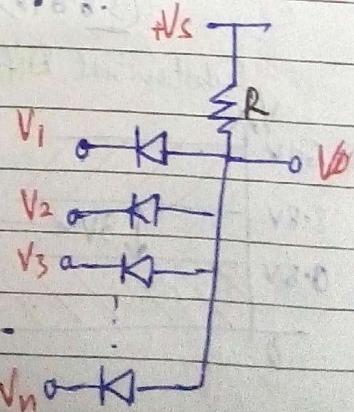


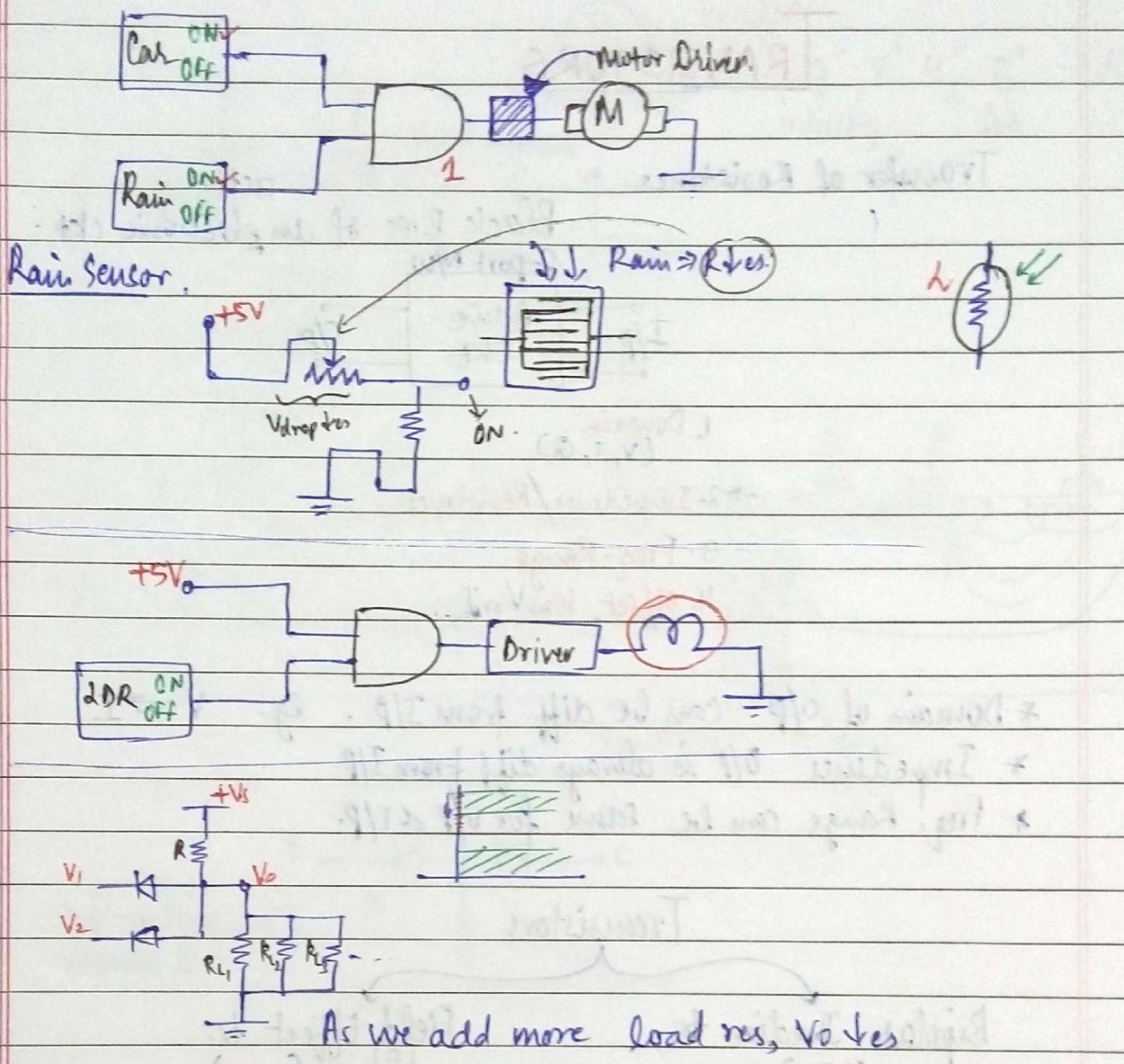

$R \rightarrow$  large  $\rightarrow$  fan-out large  
 $R \rightarrow$  small  $\rightarrow$  fan-out low.

# TRANSISTORS

## Transfer of Resistance

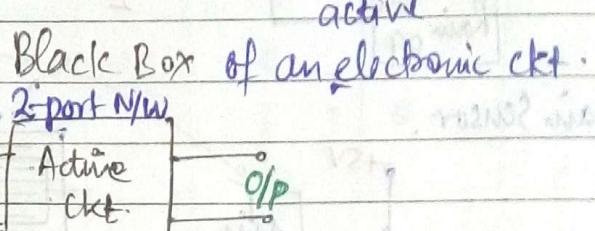

1. Domain  
( $V$ ,  $I$ ,  $G$ )

→ 2. Impedance / Resistance

3. Freq. Range

4. Offset, bias  $V$  or  $I$ ...

\* Domain of O/P can be diff from I/P. e.g.  $V \rightarrow I$

\* Impedance O/P is always diff from I/P.

\* freq. Range can be same for O/P & I/P.


## Transistors



Bipolar Junction tr.

(BJT)

Field Effect tr.  
(FET)



→ formed by extension of diode str.

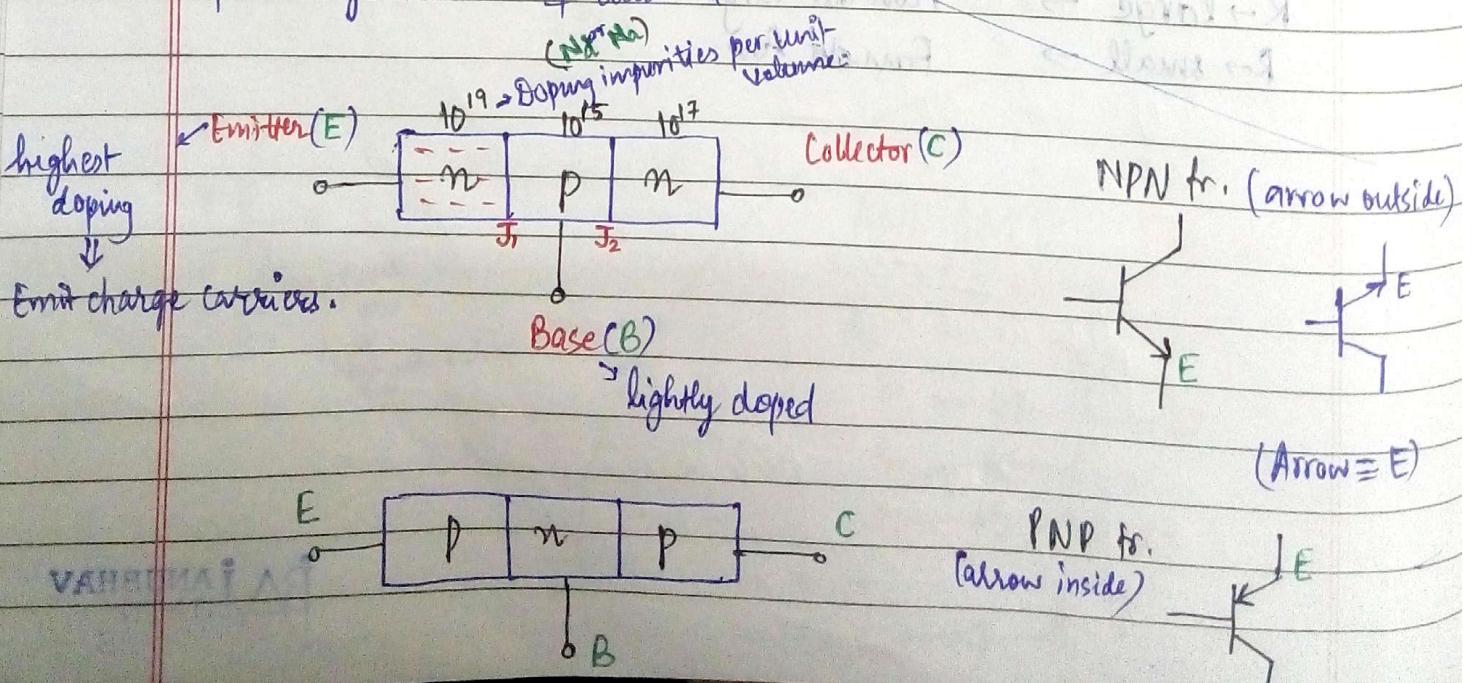

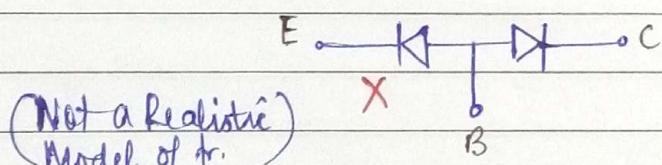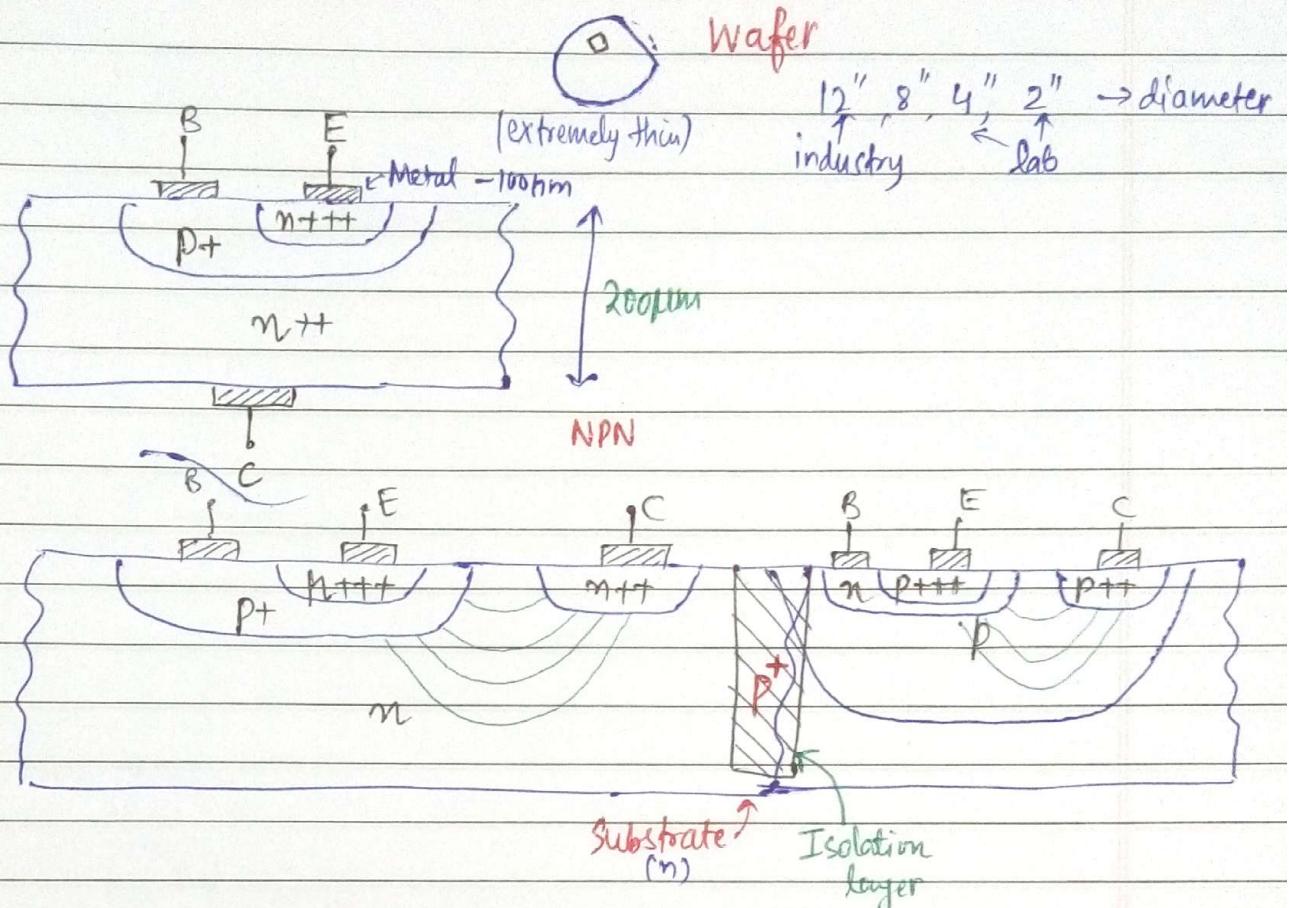

TUTORIALRectified Circuits



Q1:

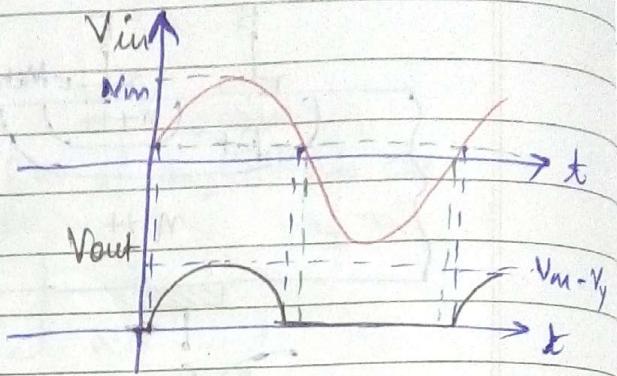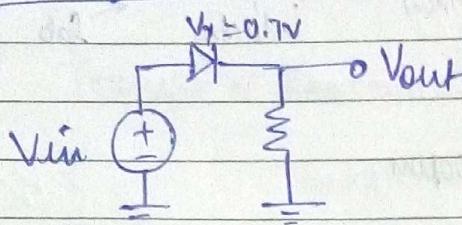

$$\text{Max. } V_{\text{out}} = V_m - V_y$$

$$V_{\text{out}} = V_m \sin(\omega t)$$

If

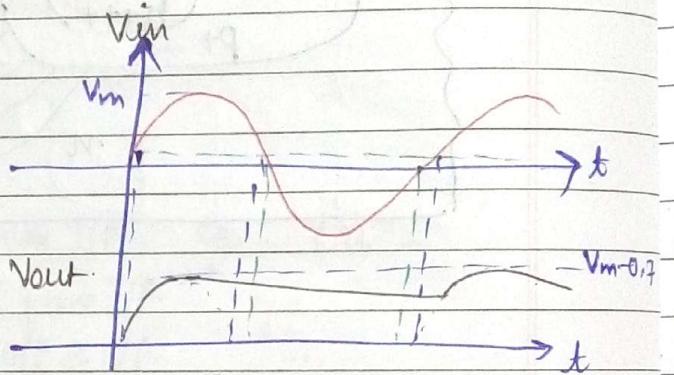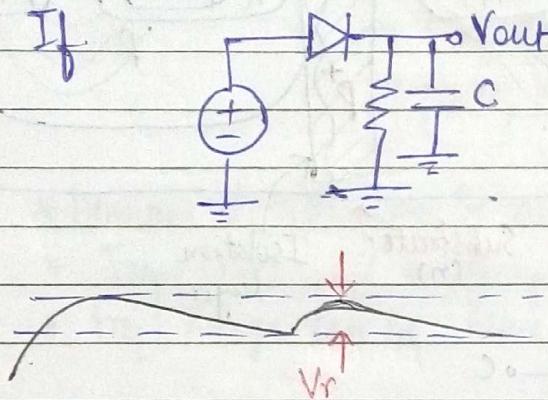


$$\text{Full wave } V_r = \frac{V_m - 0.7}{2fRC}$$


$$\text{Halfwave } V_r = \frac{V_m - 0.7}{fRC}$$

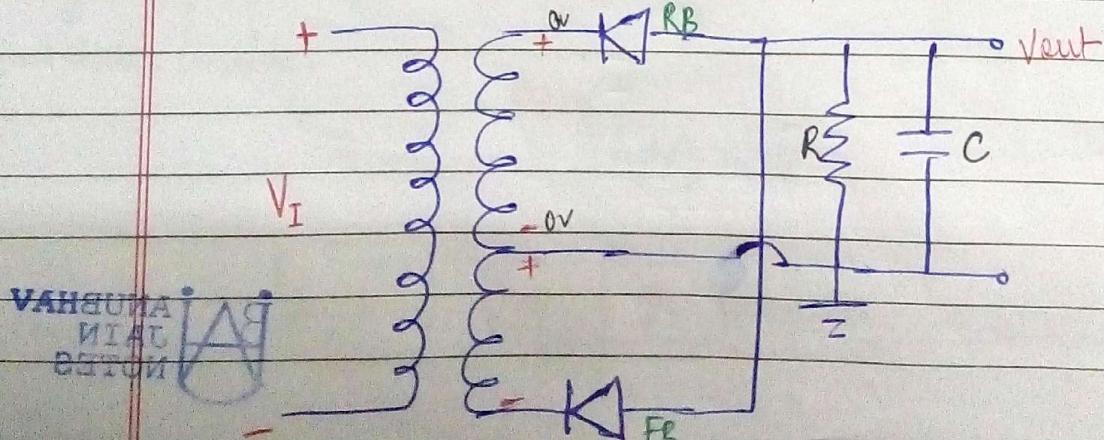Q2.

The rectifier circuit shown in Fig 1 has an input signal value of freq. 60Hz. Rms of  $I_{\text{rs}} = 8.5\text{V}$  Cut-in voltage of diodes = 0.7V,  $R = 10\text{k}\Omega$ ,  $C = 10\text{mF}$

Find max. value of  $V_o$ , What is PIV of each diode?



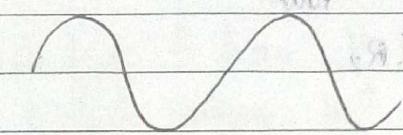$V_I$  $V_S$ 

→ half of  $V_I$ .

$$V_{D_{AVG}} = \frac{8.5 - 0.7}{2 \times 60 \times 10 \times 10^{-3}} = \frac{13}{80} = 0.1625 \text{ V}$$

$$V_{D_P} = V_{D_{AVG}} (\sqrt{2}) = 0.2298 \text{ V}$$

$$V_m = 8.5\sqrt{2} = 12.021 \text{ V}$$


$$V_m - 0.7 = 11.321 \text{ V}$$

$$V_{D_{MAX}} = -11.321 + 0.2298 \\ = -11.091 \text{ V}$$

$$V_L = 11.321$$

$$\frac{1}{2 \times 60 \times 10 \times 40 \times 10^{-3}}$$

$$= 0.2358 \approx 0.236 \text{ V}$$

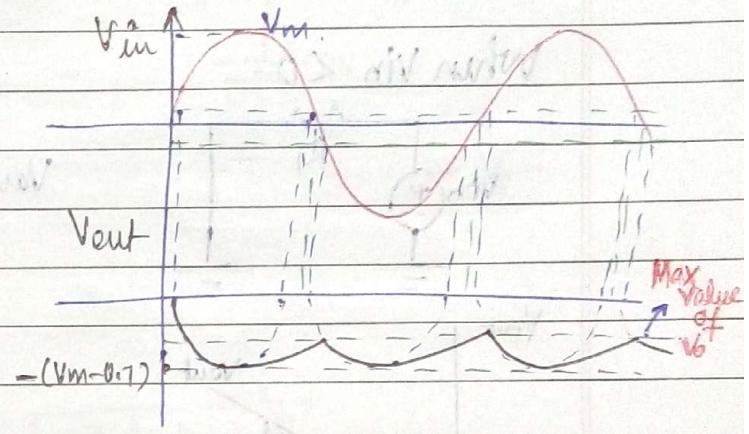

$$\therefore V_{D_{MAX}} = -11.32 + 0.236 = -11.0851 \text{ V}$$


PIV: Peak Inverse Voltage :-

Max value of  $V_I$  - Min value of  $V_{out}$  will max value of diode voltage.


$$\text{Max. PIV of diode} = 12.02 - (-11.32) \\ = 23.34 \text{ V.}$$

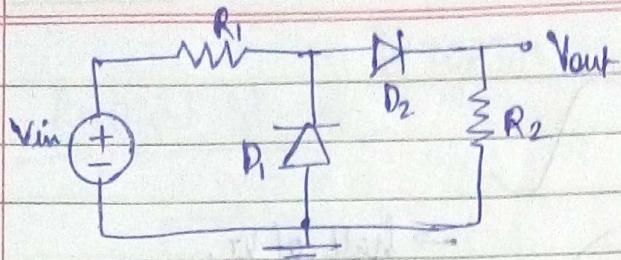Q2.

In the circuit of fig 2,  $R_1 = 500 \Omega$ ,  $R_2 = 1 \text{ k}\Omega$ . Sketch the input output characteristics for  $V_{out}$  v/s  $V_{in}$ . Also plot the current through  $R_1$ . Assume  $V_T = 0 \text{ V}$ .




When  $V_{in} > 0$

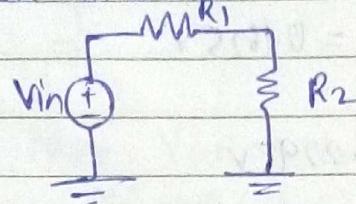


$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in} = \frac{2}{3} V_{in}$$

$$= V - \frac{R_1}{R_1 + R_2} V$$

When  $V_{in} < 0$

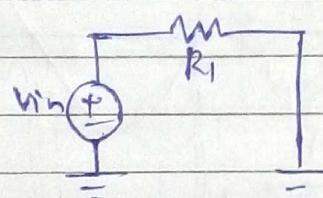


$$V_{out} = 0$$

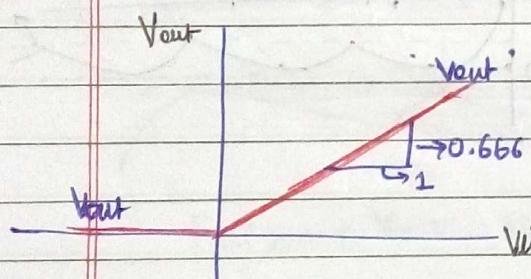

Current through  $R_1$



When  $V_{in} > 0$

$$I = \frac{V_{in}}{R_1 + R_2}$$




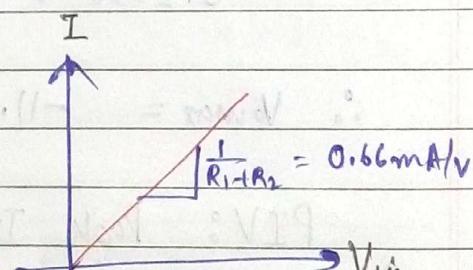




When  $V_{in} < 0$

$$I = \frac{V_{in}}{R_1}$$

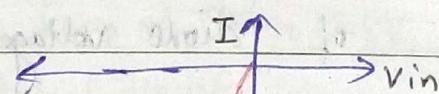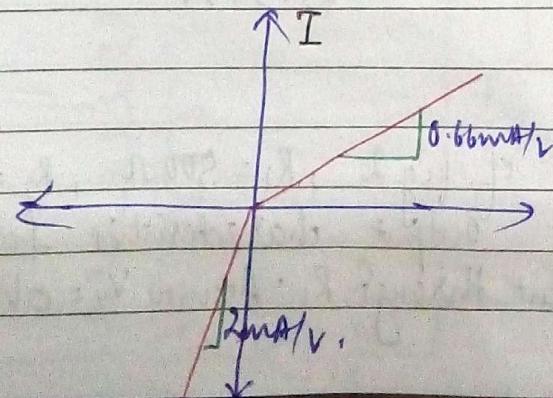


Q3.

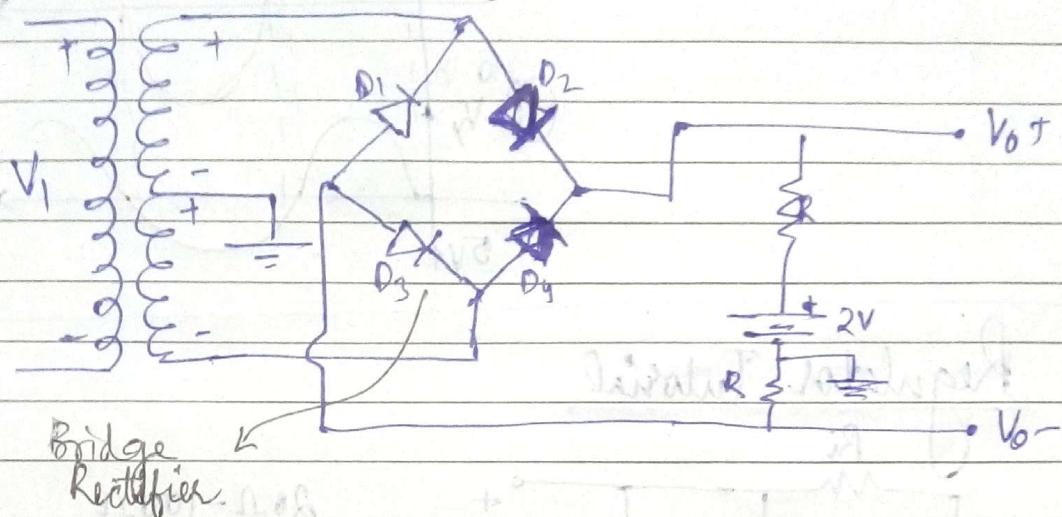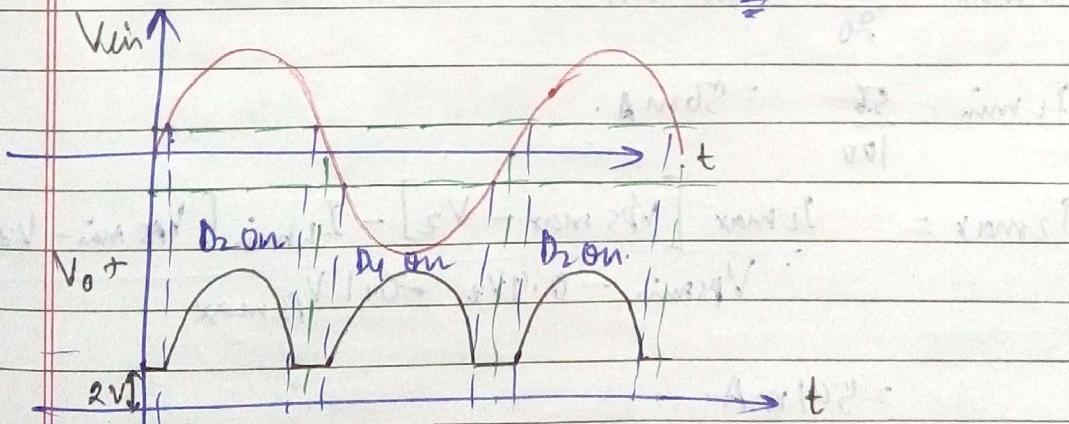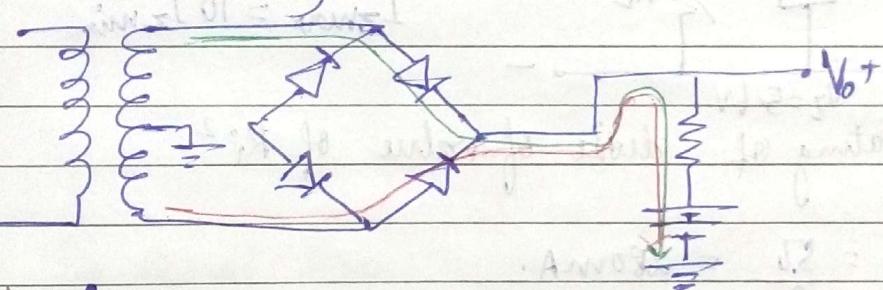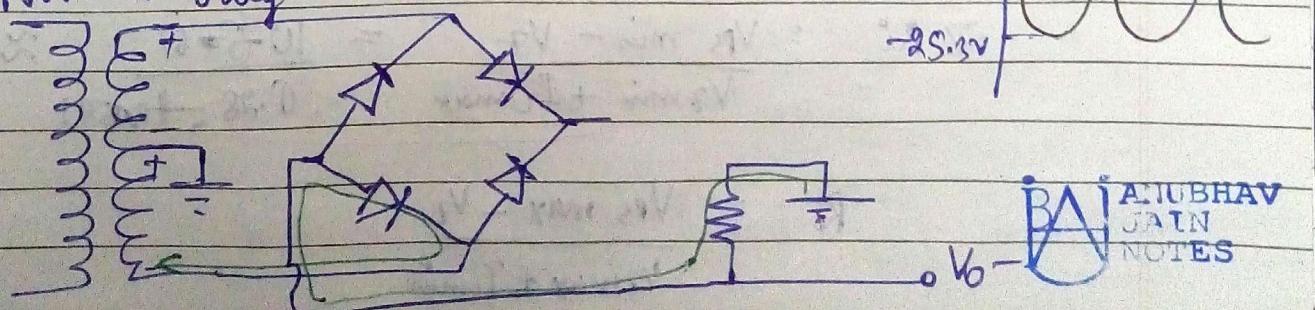The ckt. in fig B has  $V_s = 26 \sin(2\pi 60t)$ .Sketch output voltage  $V_o^+$  and  $V_o^-$  v/s time.Assume  $V_f = 0.7V$ .Consider  $V_o^+$  onlyNow  $V_o^-$  only! :-

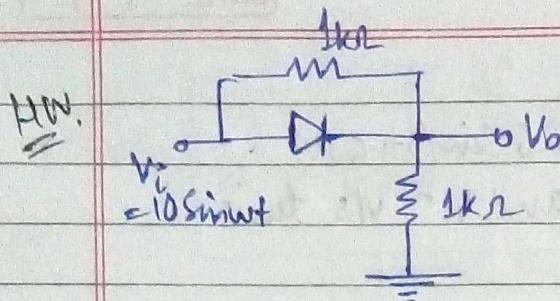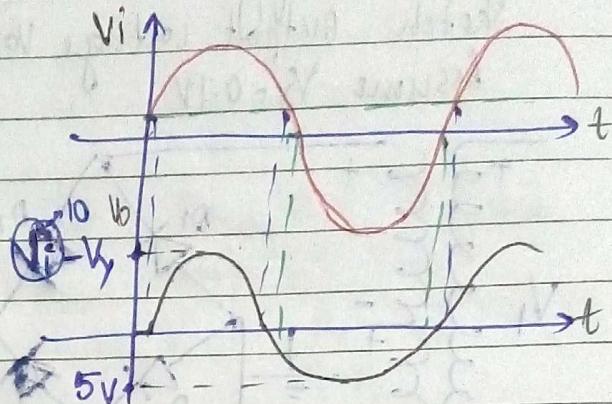float  $V_o$  v/s t.

## Regulator Tutorial

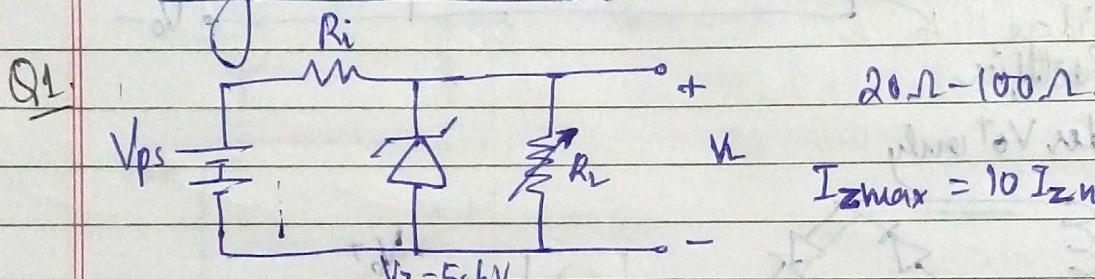Find power rating of diode of value of  $R_i^2$ .

$$I_{L\max} = \frac{5.6}{20} = 280\text{mA}$$

$$I_{L\min} = \frac{5.6}{100} = 56\text{mA}$$

$$I_{Z\max} = \frac{I_{L\max} [V_{ps\max} - V_z] - I_{L\min} [V_{ps\min} - V_z]}{V_{ps\min} - 0.9V_z} = 0.11 V_{ps\max}$$

$$= 591\text{mA}$$



$$I_{Z\max} \cdot V_z = 591\text{mA} \times 5.6\text{V} = 3.31\text{W}$$

$$\Rightarrow R_i = \frac{V_{ps\min} - V_z}{V_{z\min} + I_{Z\max}} = \frac{10 - 5.6}{5.6 + 0.11} \approx 13\Omega$$

$$R_i = \frac{V_{ps\max} - V_z}{V_{z\max} + I_{L\min}}$$


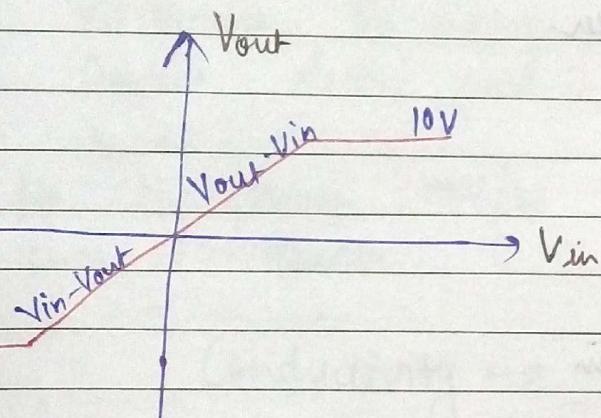
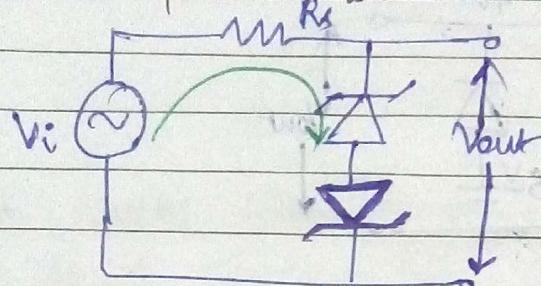
Q2.

In the circuit shown diodes are ideal and have breakdown voltage of  $V_Z = 10V$ ,  $V_{Z2} = 8V$ . If input is 15V peak sinusoidal waveform then plot the output of transfer characteristics.



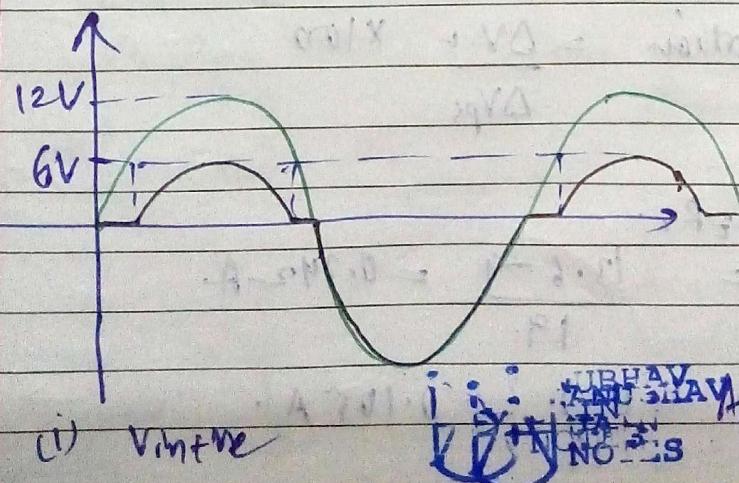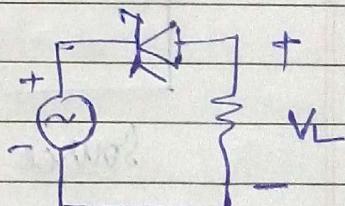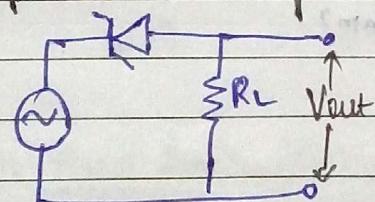Q3.

In circuit shown, zener diode is ideal and breakdown voltage is 6V, if the input voltage is 12V peak sinusoidal then plot the output waveform.




After breakdown,  $V_{out} = 6V$  (const value)  
 $V_{in} = 6V$  (const value)




Qn.

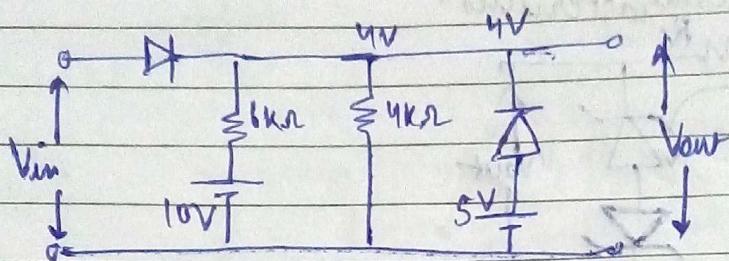
In the circuit shown, the diodes are ideal.  
Plot its char.



First assume both are open.

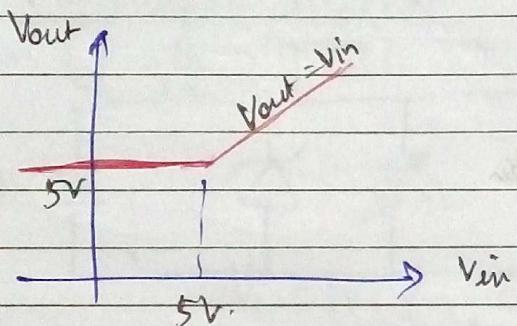

Qn.

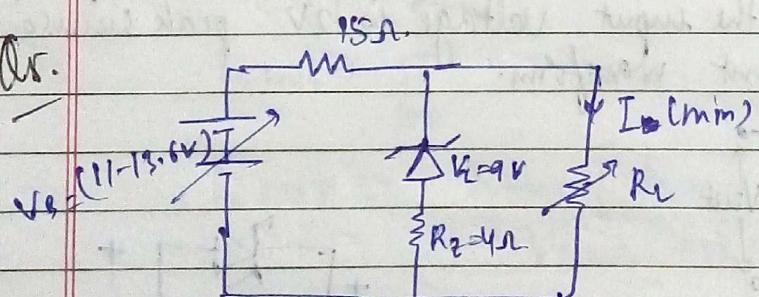

$$\text{Source Regulation} = \frac{\Delta V_L}{\Delta V_{ps}} \times 100$$

$$V_L = V_2 + I_2 R_2$$

$$I_2 (\text{max}) = \frac{13.6 - 9}{19} = 0.242 \text{ A}$$

$$I_2 (\text{min}) = \frac{V_2 - 9}{19} = 0.105 \text{ A}$$

$$V_{max}, V_{min}; \Delta V = V_{max} - V_{min}.$$

## TUTORIAL

24/08/16.

- Q2 (i) In GaAs determine the range of conductivity for a range in donor concentration of  $10^{15} \leq N_d \leq 10^{19} \text{ cm}^{-3}$
- (ii) Determine the range of direct current density if the applied electric field is  $E = 0.1 \text{ V/cm}$ .

$$\mu_p = 4000 \text{ cm}^2/\text{Vs}$$

$$\mu_n = 8500 \text{ cm}^2/\text{Vs}$$

↓  $\Sigma \text{N}_d$

(i) Conductivity  $\rightarrow \sigma = e \mu_n N_d$ .

$$\sigma_{max} = 13600$$

$$\sigma_{min} = 1.36$$


$$\Rightarrow 1.36 < \sigma < 13600$$

(ii)  $J_n = \sigma E = 0.1 \sigma$

$$\Rightarrow 0.136 < J < 1360$$

↓  $\text{A/cm}^2$

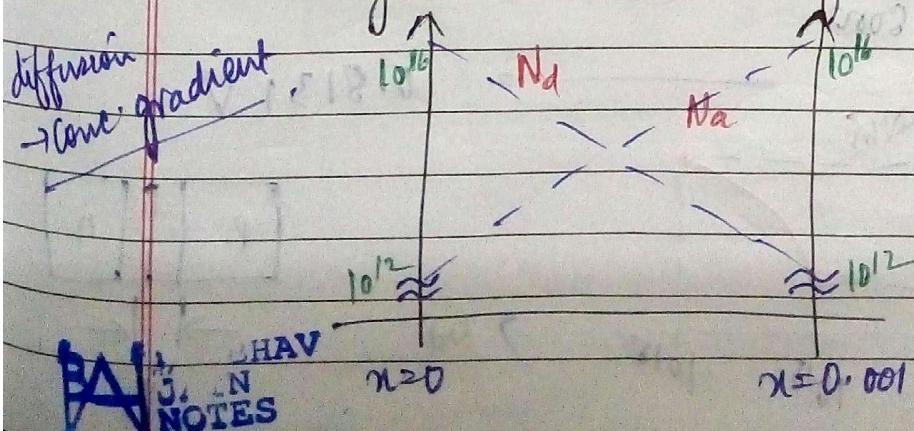- (iii) Electron and hole conc in a sample of silicon are shown in fig. Determine the total diffusion current density versus distance for  $0 \leq x \leq 0.001 \text{ cm}$



$$\mu_n = 1250 \text{ cm}^2/\text{Vs}$$

$$\mu_p = 450 \text{ cm}^2/\text{Vs}$$

$$\frac{dn}{dx} = - (10^{16} - 10^{12}) = 9.999 \times 10^{15} \text{ cm}^{-1}$$

$$\frac{dp}{dx} = - \frac{dn}{dx} = - 9.999 \times 10^{15}$$

$$\frac{KT}{e} = \frac{D_n}{\mu_n} = \frac{D_p}{\mu_p}$$

$$J_n = e D_n \frac{d N_d}{dx}$$

$$= \mu_n k T \frac{d N_d}{dx} = -51.767 \text{ A cm}^{-2} \cdot \text{A} \times 10^5 \times 10^2 \times 10^3 = 5176.7 \text{ A cm}^{-2}.$$

$$J_p = -e D_p \frac{d N_a}{dx}$$

$$= -\mu_p k T \frac{d N_a}{dx} = -18.6218137 \text{ A cm}^{-2} \cdot \text{A} \times 10^2$$

$$\text{Total diffusion current density} = -70.72 \text{ A/cm}^2. \text{ my} \rightarrow -70.7$$

Q3 (i) The donor concentration at a silicon p-n junction is

$$N_d = 10^{16} \text{ cm}^{-3}$$

plot the  $V_{bi}$  versus  $N_a$  over the

$$\text{range of } 10^{15} \leq N_a \leq 10^{18} \text{ cm}^{-3} \text{ at } 300 \text{ K.}$$

$$n_i = 1.5 \times 10^{16} \text{ cm}^{-3}$$



$$N_d = 10^{16} \text{ cm}^{-3}$$

$$V_{bi} \rightarrow \text{built in potential} = \frac{kT}{q} \ln \left( \frac{N_a N_d}{n_i^2} \right)$$

$$V_{bi} = \frac{(1.38 \times 10^{-2})(300)}{(1.6 \times 10^{-19})} \ln \left\{ \frac{N_a (10^{16})}{(1.5 \times 10^{16})^2} \right\}$$

$$V_{bi} \text{ min} = \frac{207}{8000} \text{ V} = 0.6344 \text{ V}$$
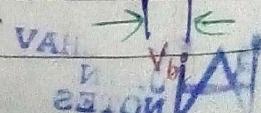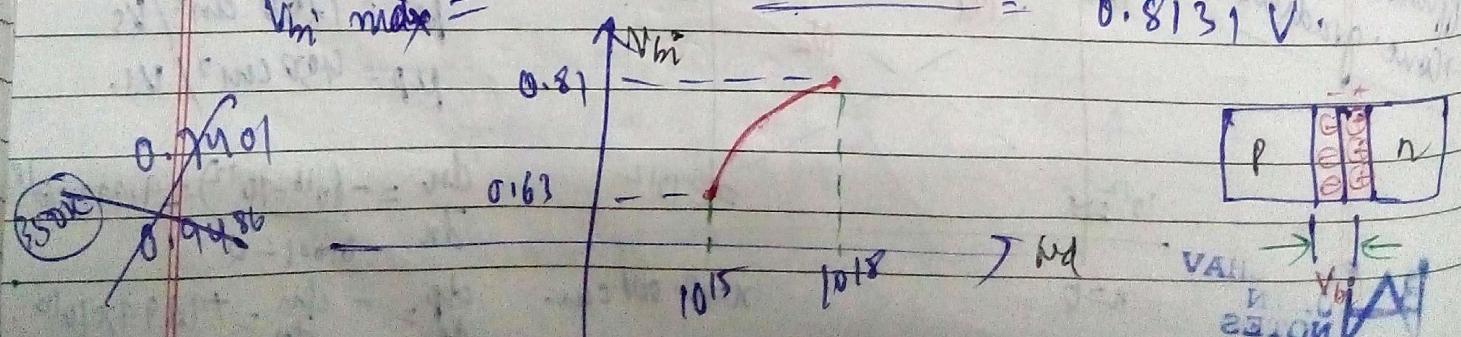
$$V_{bi} \text{ max} = \frac{0.81}{10^{18}} \text{ V} = 0.8131 \text{ V.}$$



$$C_J = C_{J0} \left(1 + \frac{V_R}{V_T}\right)^{-1/2}$$

PAGE: 1 / 1  
DATE: 1 / 1

On changing Temp,  $n_i$  also changes.

$$n_i' = \frac{1.5 \times 10^{10}}{\left(\frac{350}{300}\right)^{3/2}} = 1.588 \cdot \text{m}^3 \text{ (Note: } n_i \propto T^{3/2})$$

$$n_i' = 1.38 \times 10^{10}$$

$$M_{i\max} = \left( \frac{1.38 \times 10^{-23} \times 350}{1.6 \times 10^{-19}} \right) \ln \left( \frac{(10^{18})(10^{16})}{(2.38 \times 10^{10})^2} \right) = 0.92$$

Q4. The zero biased Junction capacitance of a silicon p-n junction is  $C_{J0} = 0.4 \text{ pF}$ . The doping conc. are  $N_A = 1.5 \times 10^{16} \text{ cm}^{-3}$  &  $N_D = 4 \times 10^{15} \text{ cm}^{-3}$ .

Determine the junction cap. at

$$(a) V_R = 1V \quad (b) V_R = 3V \quad (c) V_R = 5V$$

$$V_{bi} = \frac{kT}{e} \ln \left( \frac{N_A N_D}{n_i^2} \right) = 0.68 \text{ V.}$$

$$(a) C_J = (0.4 \text{ pF}) \left( 1 + \frac{0.1}{0.68} \right)^{-1/2} = 0.254 \text{ pF.}$$

$$(b) C_J = (0.4 \text{ pF}) \left( 1 + \frac{3}{0.68} \right)^{-1/2} = 0.172 \text{ pF.}$$

$$(c) C_J = (0.4 \text{ pF}) \left( 1 + \frac{5}{0.68} \right)^{-1/2} = 0.138 \text{ pF.}$$


Transistor.  $\rightarrow 0\text{--}\infty \Omega$  Resistance

ON  
OFF  
} Switch  
 $\downarrow$   
 $\infty \Omega$

Amplifier (somewhere in between 0 to  $\infty \Omega$ )

$\Omega$   
 $k\Omega$   
 $M\Omega$



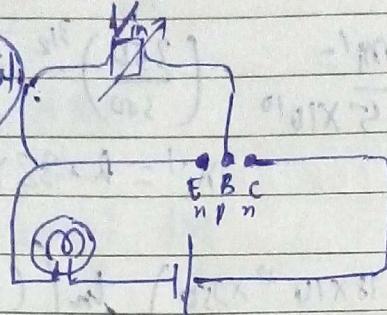
$V_{BE}$  not enough to  
overcome barrier potential.  
OFF



YouTube | LearnEngineering  
Transistor - How does it work

done  
Silicon  $\rightarrow$  no use


Silicon + Doping ✓

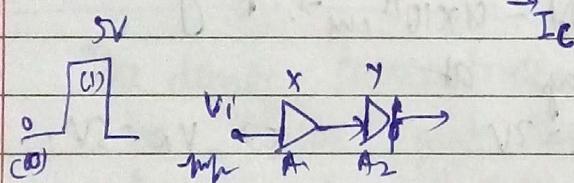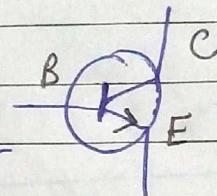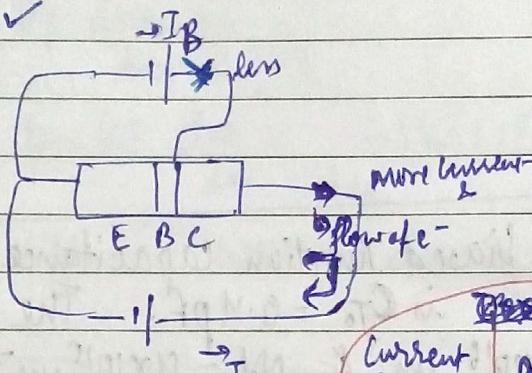


Current Gain  $\beta = \frac{I_c}{I_b} > 1$


Gain =  $A \cdot Y$ .

Transistor Circs

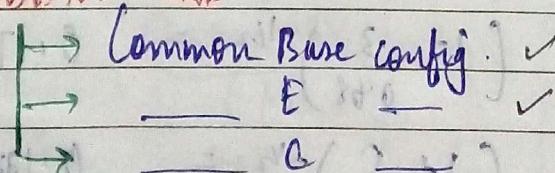

CB Config.

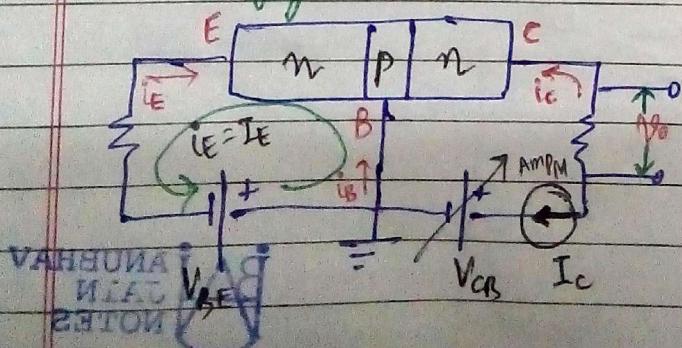

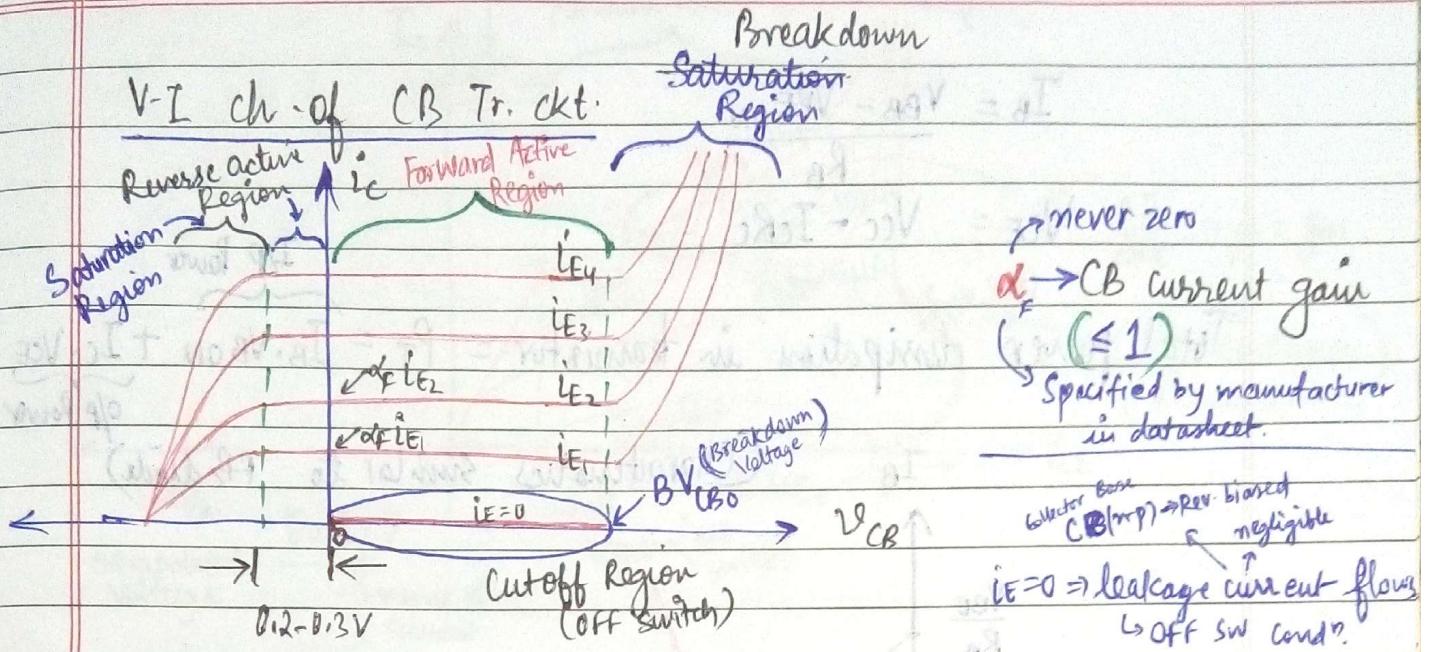

### Appl'g of CB config:-

1. Constant I Source (FW active Region)

2. OFF SW

3. Amp.

$$i_E = I_{E0} e^{\frac{V_{BE}}{V_T}} \quad 10^{-12} \text{ to } 10^{-15}$$


$$i_C = I_S e^{\frac{V_{BE}}{V_T}} \quad 26 \text{ mV}$$

$$i_C = \alpha i_E \quad I_S = \alpha I_{E0}$$

$$i_B \propto e^{\frac{V_{BE}}{V_T}}$$

### CE Config. / Amp.

26/08/16

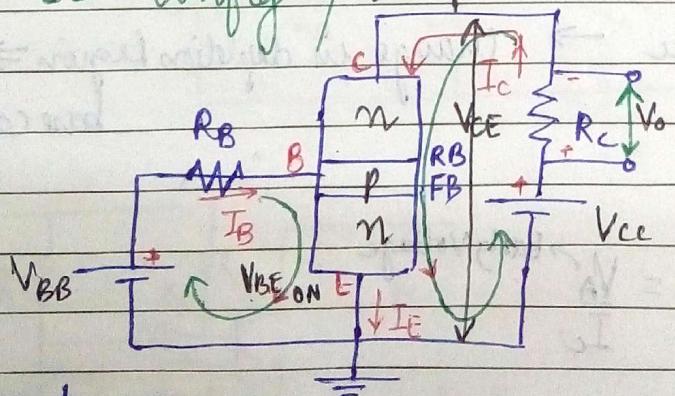

$(\alpha = \text{CB current gain})$   
 $* \beta = \text{CE current gain}$   
 $(50-200)$

$$(\alpha \leq 1 \ll \beta)$$

$$* \alpha = \frac{\beta}{1+\beta} \quad * \beta = \frac{\alpha}{1-\alpha}$$

emitter current.

$$\text{Lab} \rightarrow \beta = 100$$

$$I_E = I_C + I_B$$

$$I_C = \beta I_B$$

$$V_{CE(\text{sat})} \Rightarrow I_C > I_B$$

$$V_{CC} > V_{BB}$$

$$I_B = \frac{V_{BB} - V_{BE\ ON}}{R_B}$$



$$V_{CE} = V_{CC} - I_C R_C$$

I/P Power

O/P Power

Total power dissipation in transistor =  $P_T = I_B \cdot V_{BE\ ON} + I_C \cdot V_{CE}$

(Characteristics similar to p-n diode)

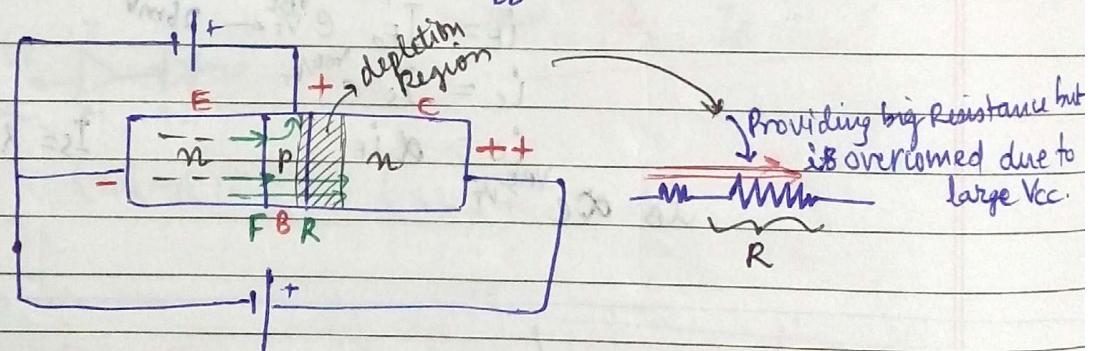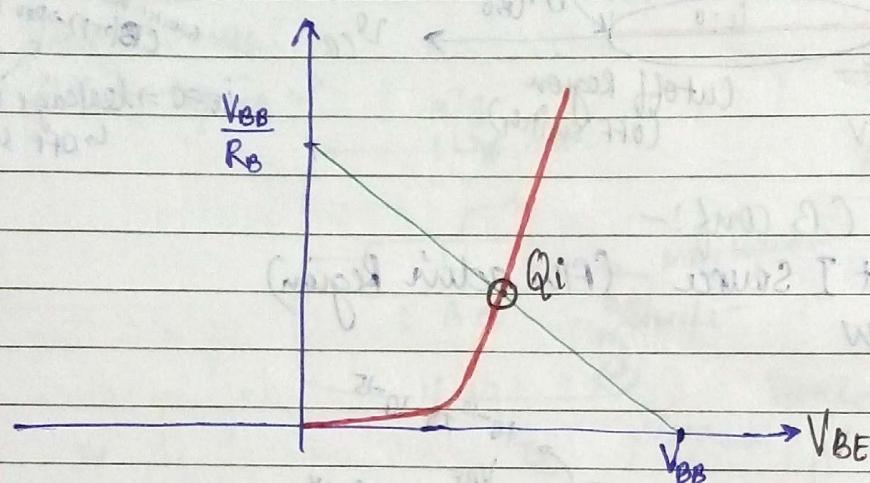


Base width modulation


Change in Vcc  $\rightarrow$  Change in depletion region  $\Rightarrow$  width of base can be modified

$$r_0 = \frac{V_A}{I_C} \rightarrow \text{Early Voltage}$$

$$BV_{CE0} = \frac{BV_{CB0}}{\sqrt{\beta}}$$



Given by manufacturer

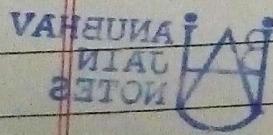


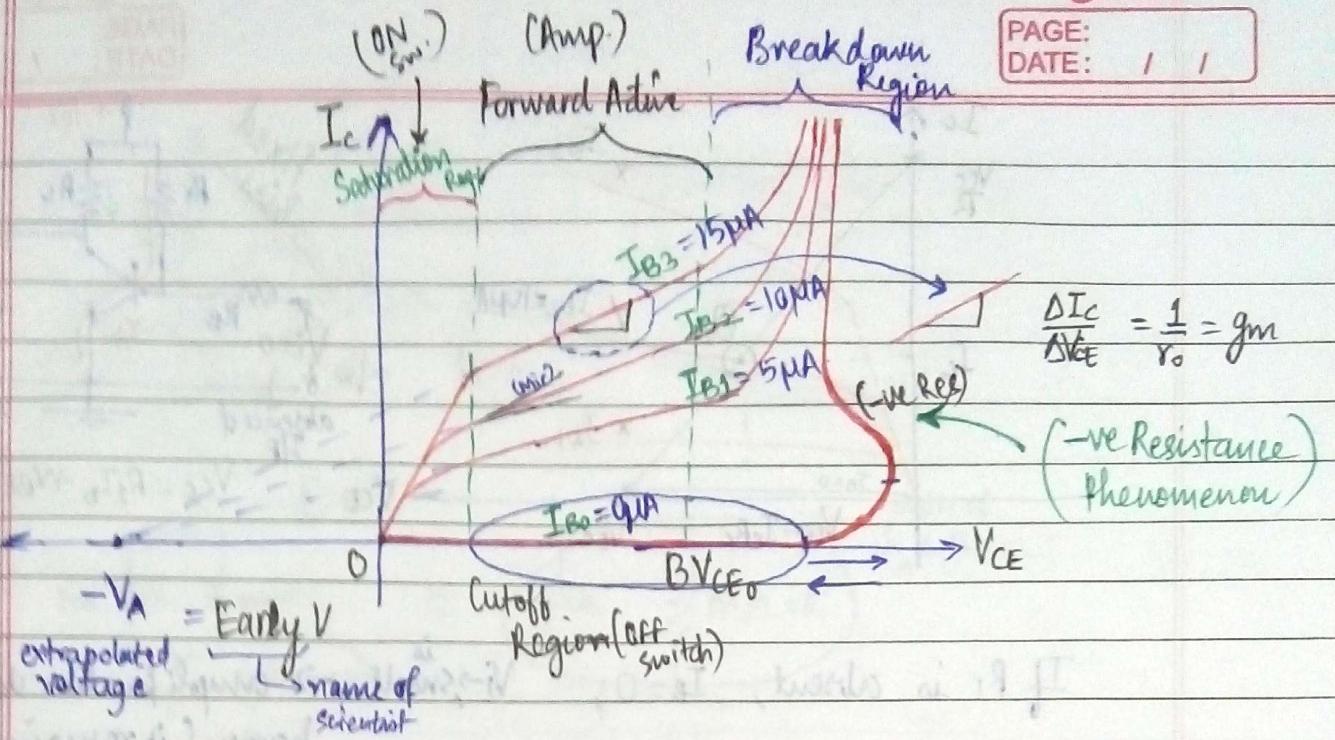

$I_c = \beta I_B$  } No longer valid after certain conditions.

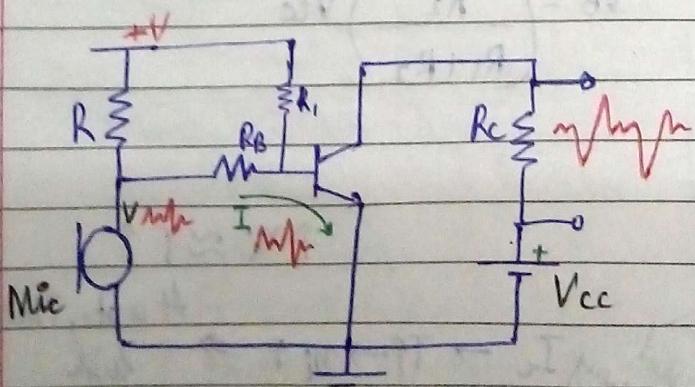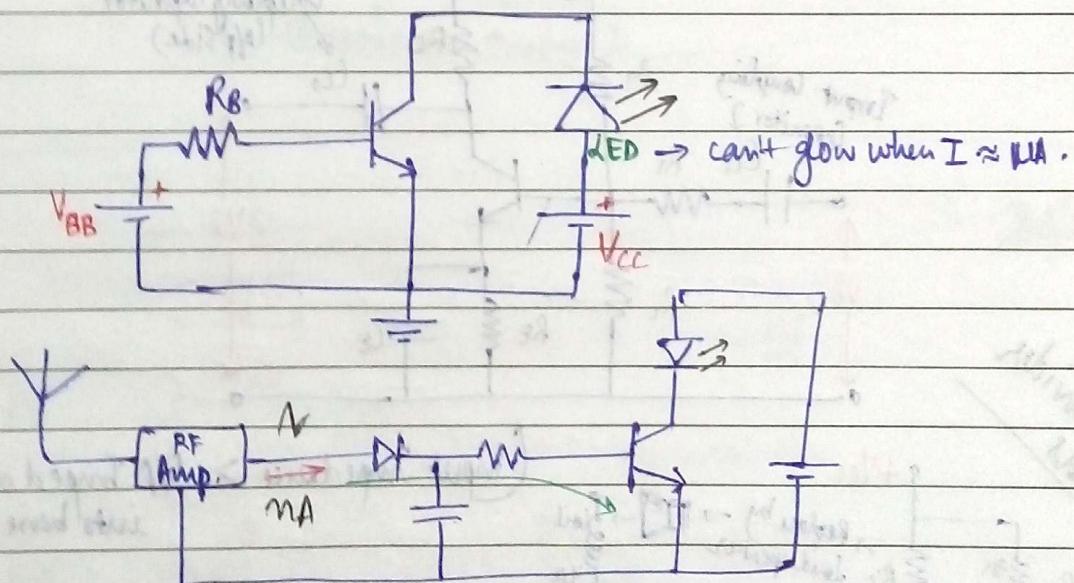
$\hookrightarrow$  after  $V_{CE} = BV_{CEO} \rightarrow$  Not valid



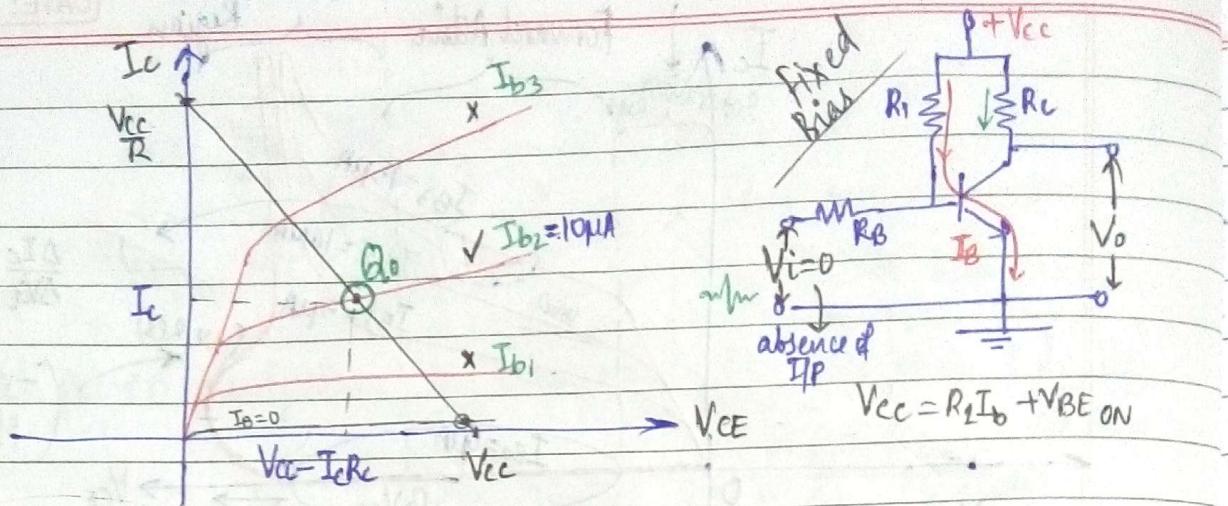


If  $R_I$  is absent,  $I_b = 0$ ,  $V_i \rightarrow$  small  $\rightarrow$  amplification does not happen (it remains close to zero)

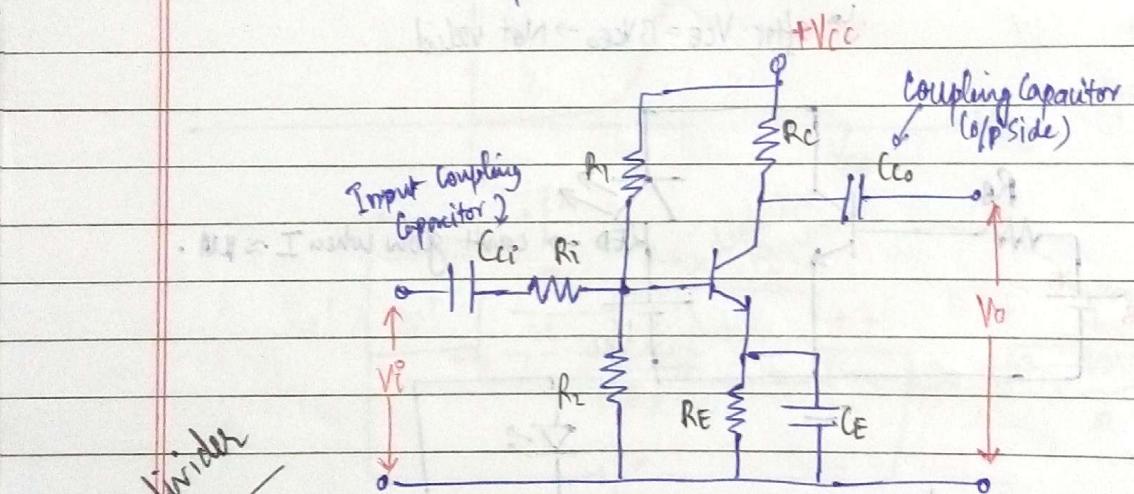For amplification, big  $I_c$  is required and for that  $R_I$  should be there &  $I_b > 0$



Resistor Bias

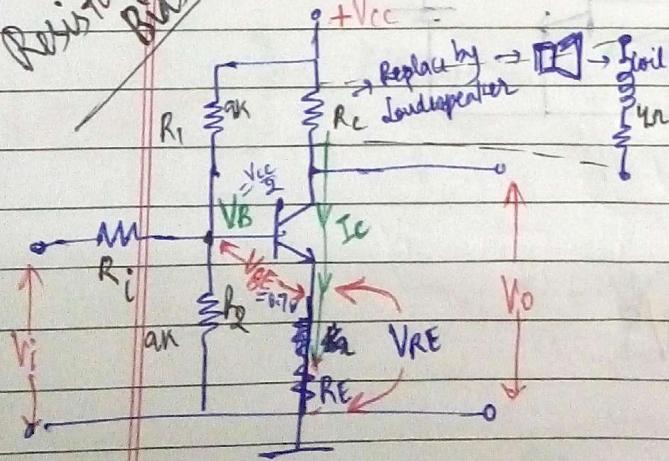(Input Impedance  $>$  O/P Impedance)  $\Rightarrow$  Current into base is small.





$$V_B = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC}$$


$\uparrow n_i \approx T \uparrow$

(RE required to prevent  
thermal runaway)

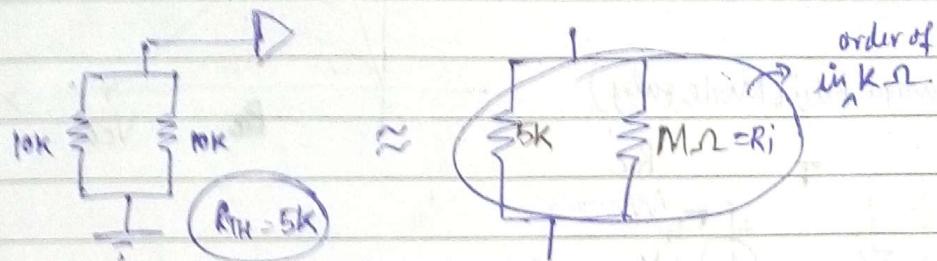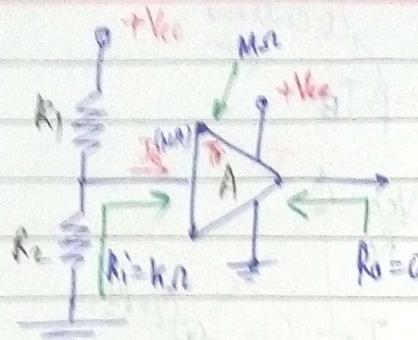
Thermal runaway  $I_c \rightarrow T \uparrow \rightarrow n_i \uparrow \Rightarrow$  high




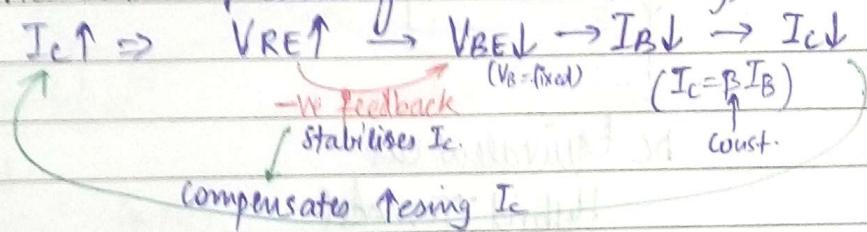Role of RE (in preventing Thermal Runaway) :-




31/08/16

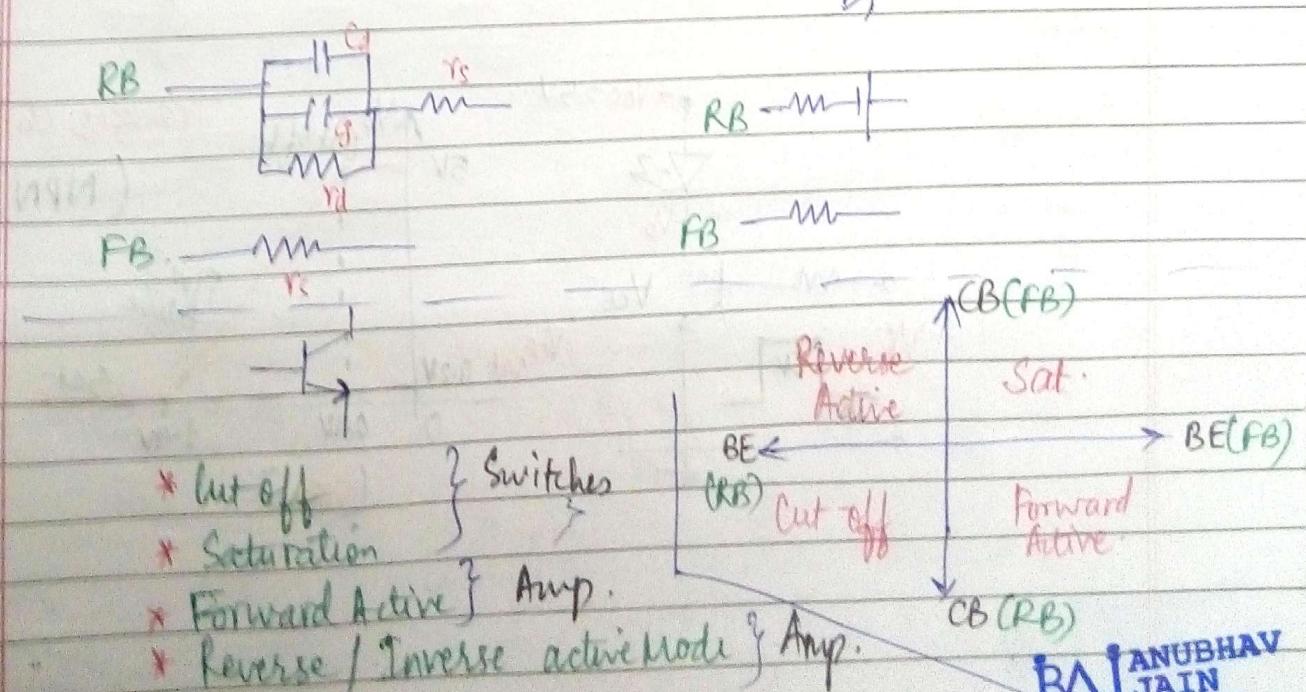

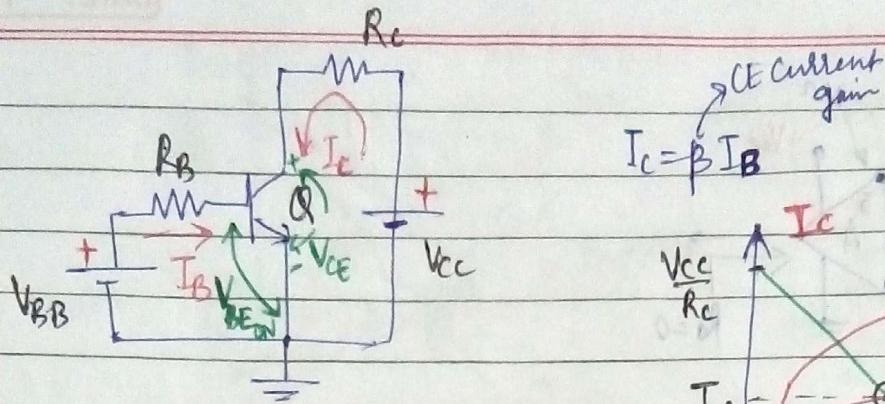

(Eq. Ckt for Forward Active Mode only)

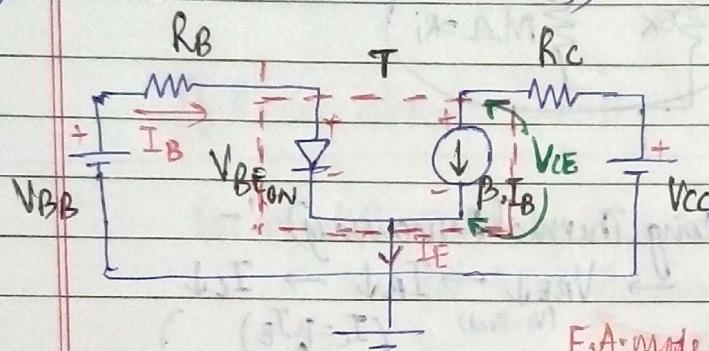



DC Equivalent Ckt

Hybrid T-model

Open Switch  $\rightarrow$   $\infty$  Off-state Resistor (Air, Moshine res.)  
very high.

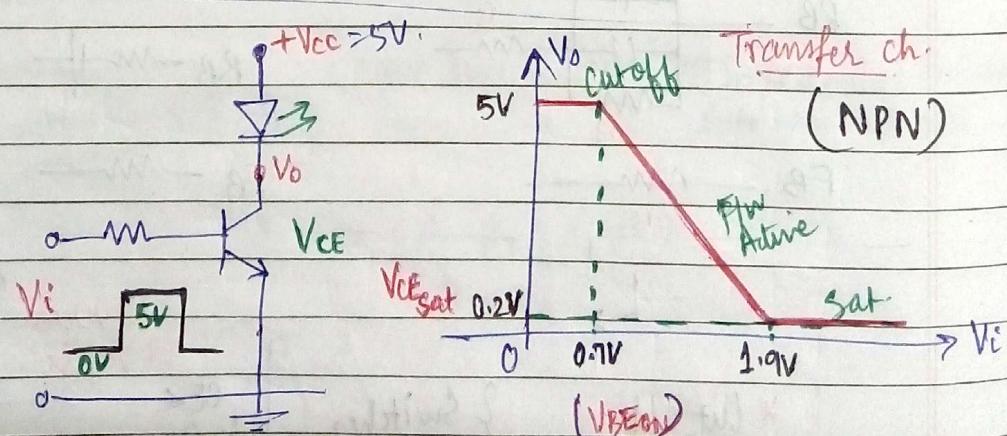
Closed Switch  $\rightarrow$   $0\ \Omega$  On-state Res.




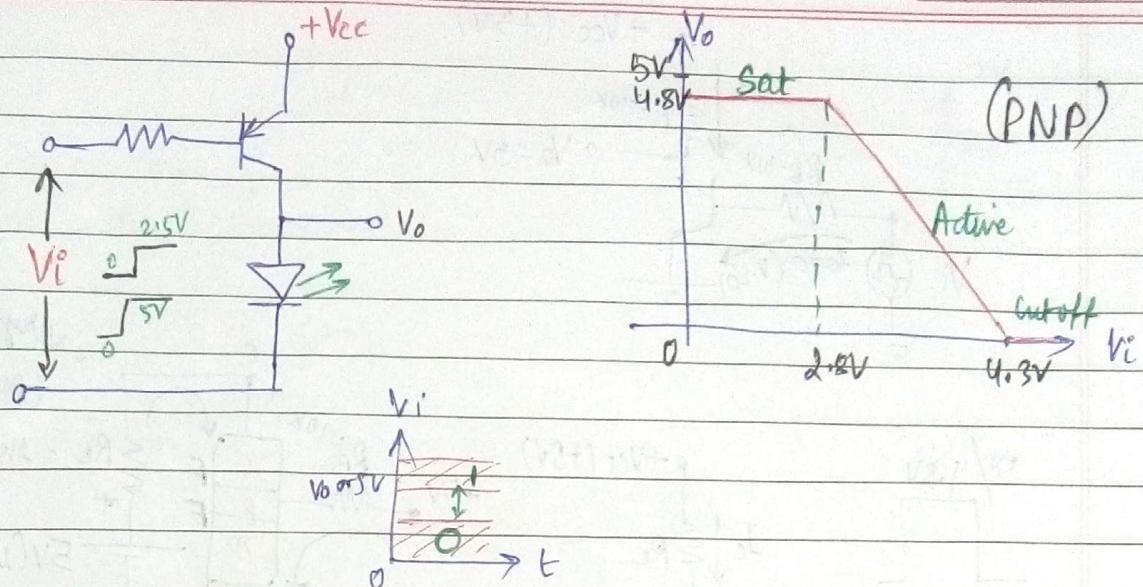



## Transistor Circuits

01/09/16.


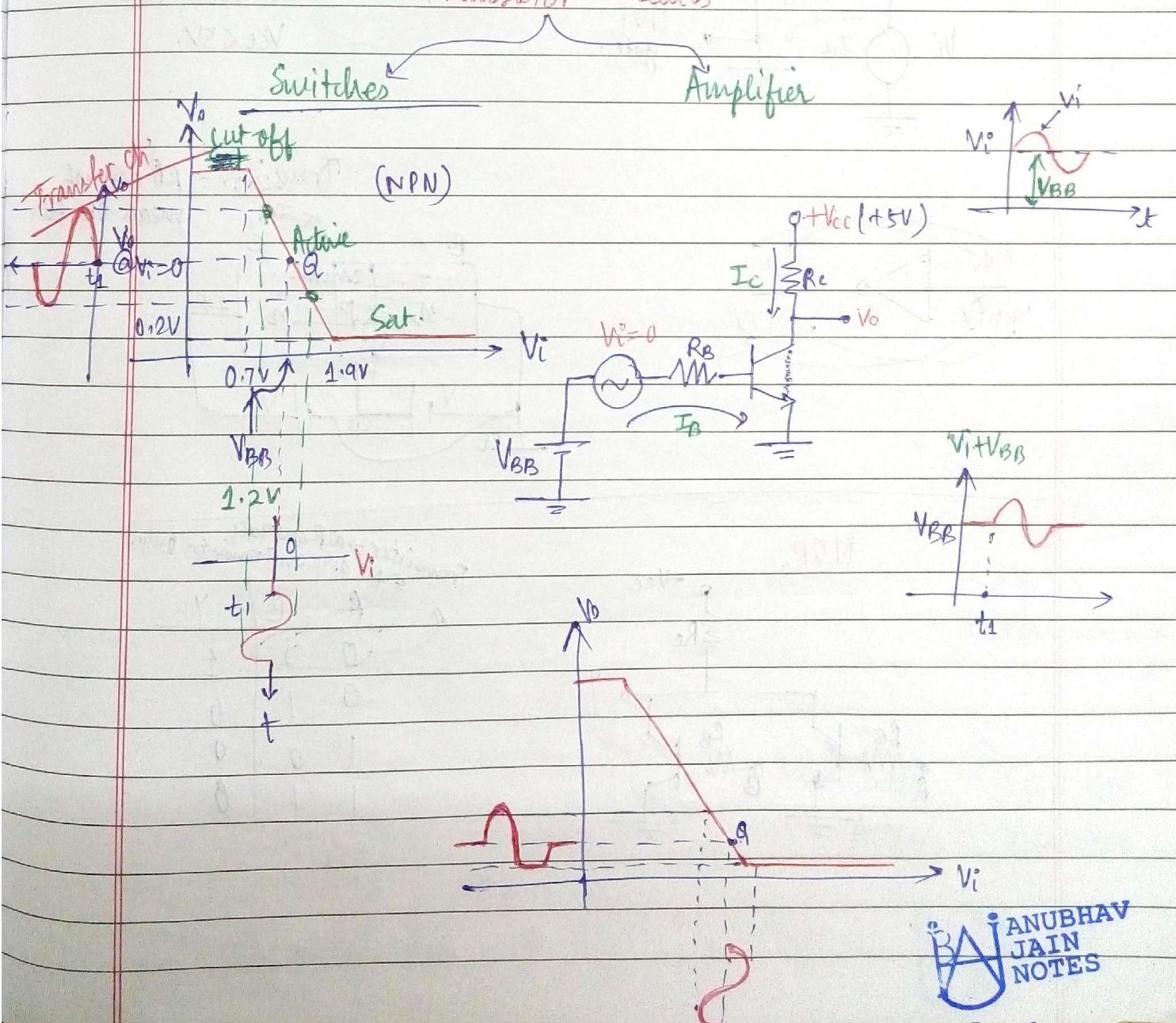


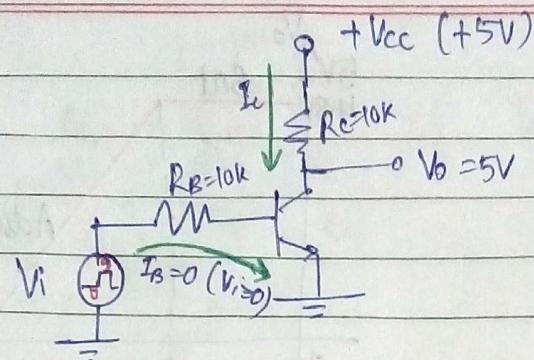


5V / 1.8V  
0V

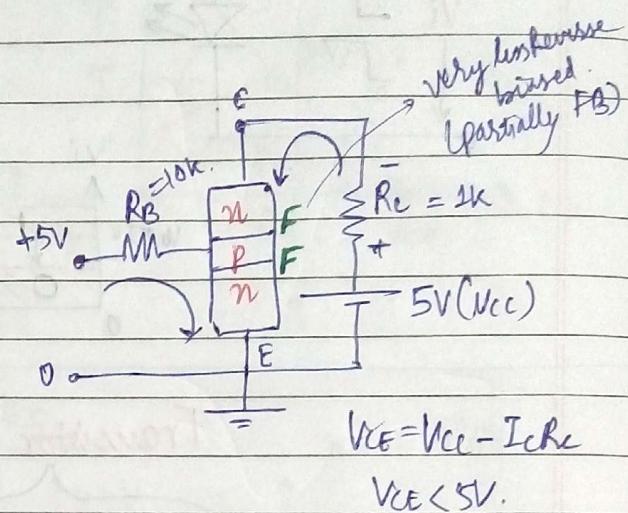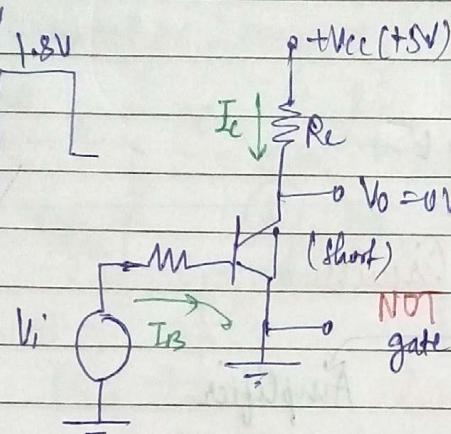

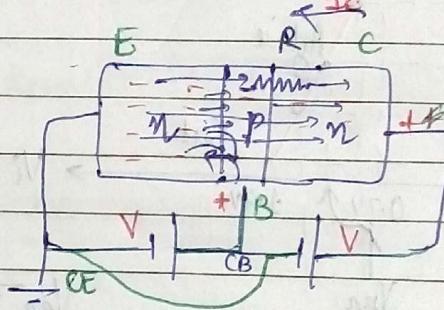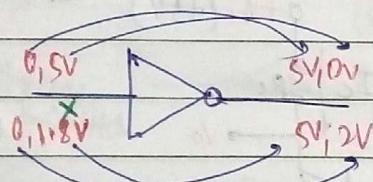Transistor  $\rightarrow$  RB does not mean OFF state.




NOR

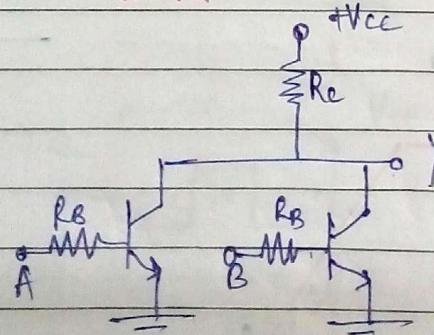

Transistor  $\rightarrow$   $\alpha$  Resistance  
All drop on Transistor fully.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


## Transistor Circuits and Models

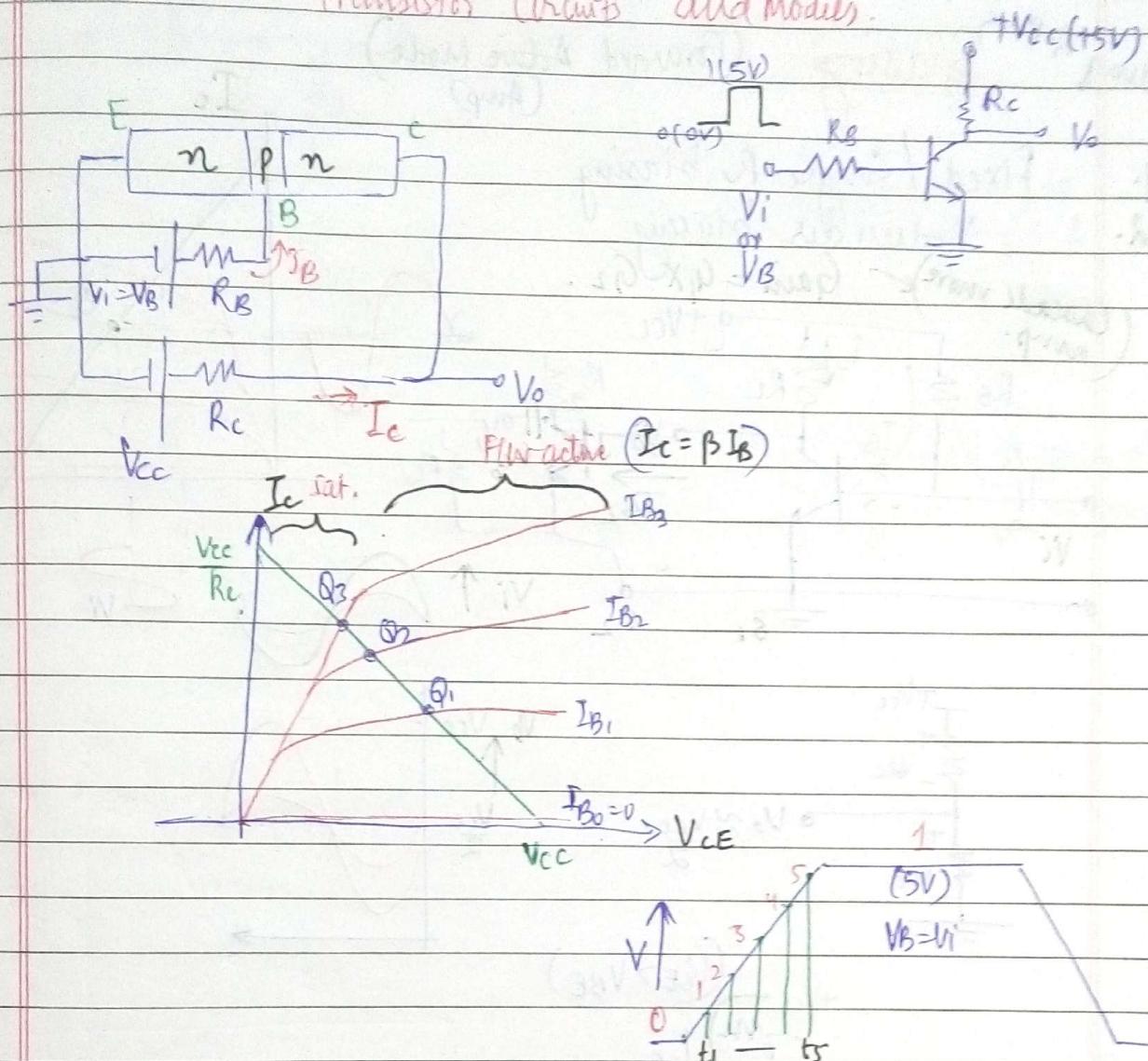

$$I_B = V_B - V_{BE}$$

$R_B$
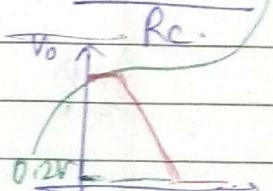
$$I_{C_{sat}} = \frac{V_{CC} - V_{CE_{sat}}}{R_C}$$



Considerations:-

1. DC to RF/high freq.
2. Leakage ( $I_{FO}$ ,  $I_{BO}$ ,  $I_{CO}$ )

3.  $V$ -range

4.  $R_i$  &  $R_o$

5.  $\beta_{dc}$  and  $\beta_{ac}$   
6. Temp Range

Sat:  $V_{CE} < V_{BE}$






Active:  $V_{CE} > V_{BE}$

setting  $Q = P_A$   $\leftarrow$  **Biassing** (Forward Active Mode) (Amp)


1. Fixed / Single R biasing

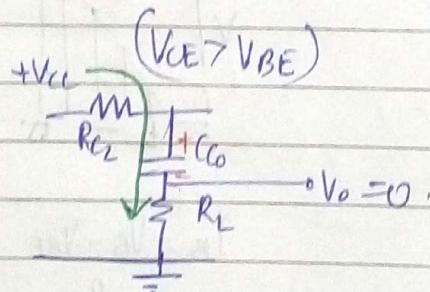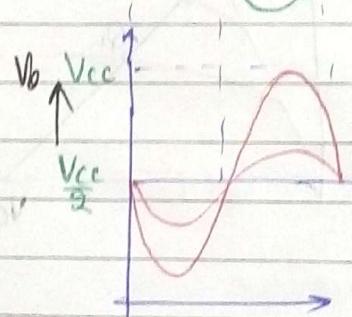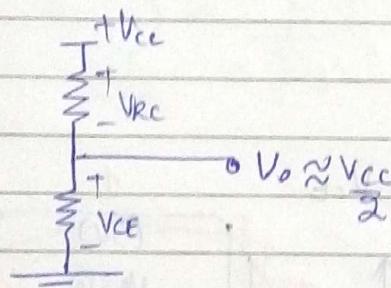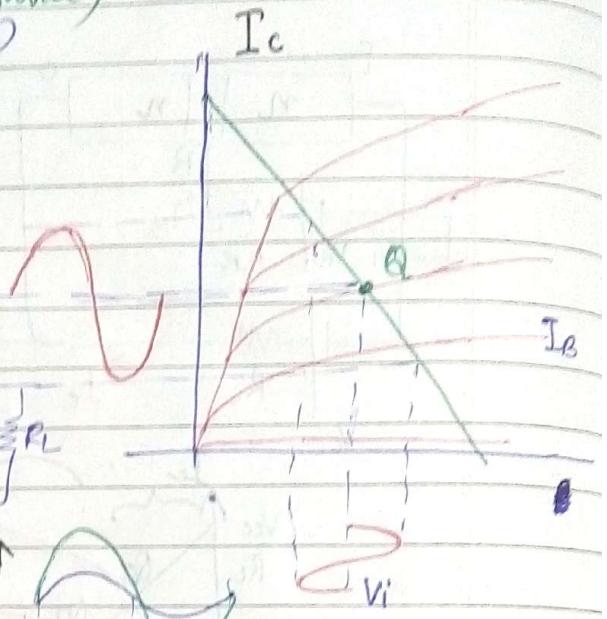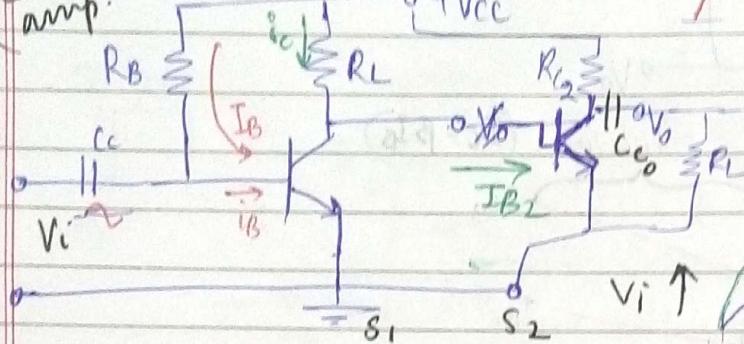2. V-divider biasing

(cascade more)  $\leftarrow$  Gain =  $G_1 \times G_2$ .  
amp.





Amp

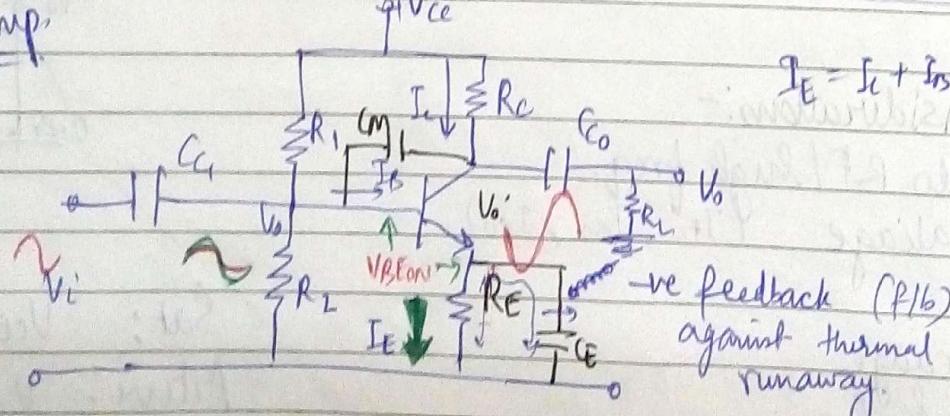

$$I_E = I_c + I_b$$

VANHUNA  
NIAT  
затон

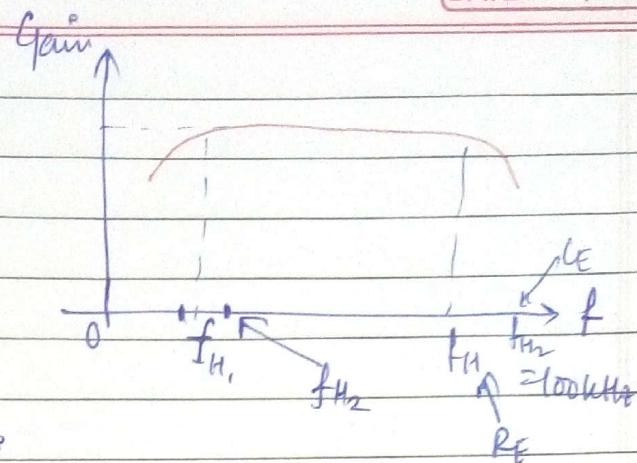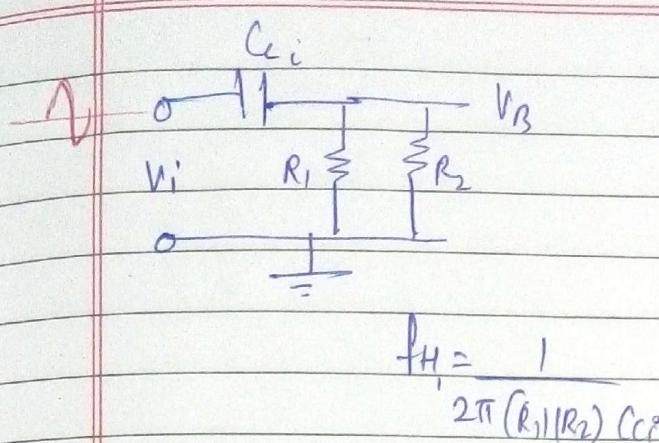$T \uparrow \quad I_c \uparrow \quad I_c \uparrow \quad V_{RE} \uparrow \quad V_{BE} \downarrow \quad I_b \downarrow \quad I_c \downarrow \Rightarrow T \downarrow$




WVA) - Features & Purpose of components.

## Tutorial

Q1. For the transistor circuit in following figure,  $\beta = 75$ .

Find the values of labeled voltages and currents.

$R_E = 10\text{ k}\Omega$ ,  $R_C = 2\text{ k}\Omega$ ,  $R_B = 20\text{ k}\Omega$ , consider  $|V_{BE}|_{ON} = 0.7\text{ V}$ .

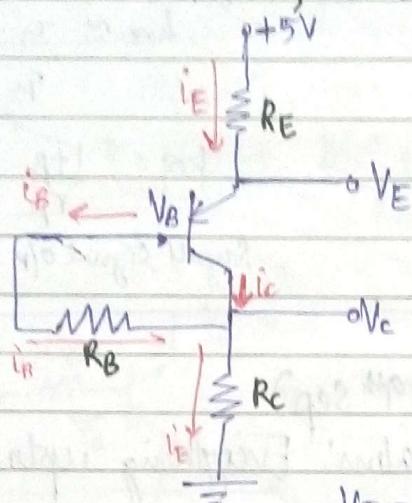

$$V_C = i_E R_C$$

$$V_B - V_C = i_B R_B$$

$$V_B = V_C + i_B R_B = i_E R_C + i_B R_B$$

$$V_E - V_B = 0.7\text{ V}$$

$$\therefore V_E = V_B + 0.7$$

$$V_E = i_E R_C + i_B R_B + 0.7$$

$$V_E = 5 - i_E R_E = i_E R_C + i_B R_B + 0.7$$

$$5 - i_E R_E = i_E R_C + i_B R_B + \frac{i_E}{\beta + 1} R_E + 0.7$$

$$i_E = i_C + i_B$$

$$\text{and } i_C = \beta i_B$$

$$\Rightarrow i_E = \beta i_B + i_B = (\beta + 1) i_B$$

$$\Rightarrow i_B = \frac{i_E}{\beta + 1}$$

$$\text{or } i_E (R_C + \frac{R_B}{\beta + 1} + R_E) = 5 - 0.7$$

$$i_E = \frac{4.3}{2\text{k} + \frac{20\text{k}}{76} + 10\text{k}}$$

$$= 0.35\text{ mA.}$$


$$i_B = \frac{i_E}{\beta + 1} = \frac{0.35 \times 10^{-3} \text{ A}}{76} = 4.614 \text{ mA.}$$

$$V_C = i_E R_C = 0.7012 \text{ V}$$

$$V_E = 5 - i_E R_E = 1.494 \text{ V}$$

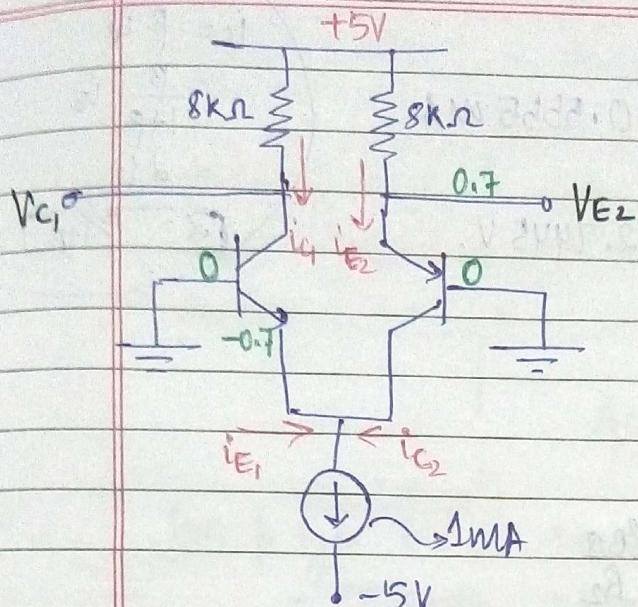Q2. For the circuit in following fig.,  $\beta = 200$  for each transistor, find  $V_{C1}$ ,  $V_{E2}$ ,  $i_{E1}$  and  $i_{C2}$ .

Assumed Transistors  $\rightarrow$  Active Mode.



$$\bullet V_{B2} = 0 \quad \bullet V_{BE} = V_{E2} = 0.7V.$$

$$i_E + i_C = 1\text{mA}$$

$$V_{E2} = 0.7V$$

$$i_{E2} = \frac{5 - 0.7}{8k} = 0.5375\text{mA}$$

$$\bullet i_{C2} = \frac{\beta}{\beta+1} i_{E2} = 0.5348\text{mA}$$

$$\bullet i_{E1} = 1\text{mA} - 0.5348\text{mA} = 0.4652\text{mA}$$

$$i_g = \frac{\beta}{\beta+1} = 0.4628\text{mA}$$

$$V_{C1} = 5 - (8k)i_{C1} = 5 - (8k)(0.4628\text{mA})$$

$$V_{C1} = 1.297V$$



$$|V_{BE}| = 0.7 \quad (\text{Always } \rightarrow \text{for Si})$$

PNP      npn


$$\leftarrow V_{BE} = 0.7 \quad V_{BE} = 0.7$$

Early voltage

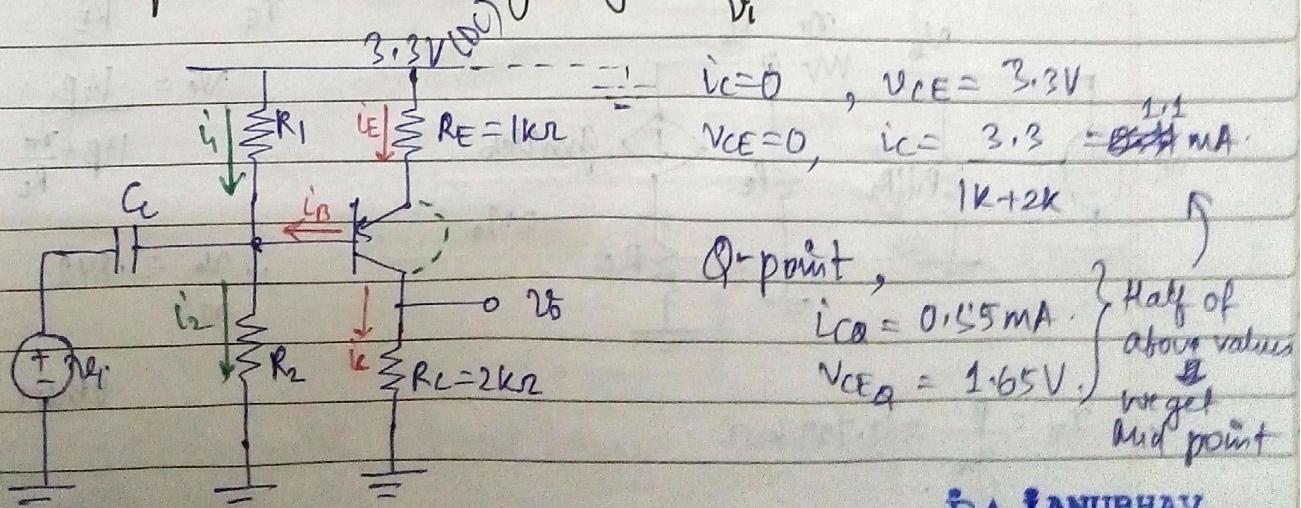Q3.

The transistor for the following ckt has  $\beta=100$ ,  $V_A = \infty$ . Find  $R_1$  and  $R_2$  such that it is bias stable and Q-point is near the centre of load line. (Plot of  $i_C$  &  $V_{CE}$ )

Also find the small signal gain  $\frac{V_o}{V_i}$



Q-point,  
 $i_{CQ} = 0.55\text{mA}$ . } Half of  
 $V_{CEQ} = 1.65V$ . } above values  
 we get  
 mid point

$$i_{EQ} = \frac{i_{CA}}{\alpha} = \frac{0.55 \text{ mA}}{10\%} = 0.5555 \text{ mA}$$

$$V_{EQ} = 3.3 - i_{EQ} \times R_E = 2.7445 \text{ V.}$$

$$V_{BEQ} = V_{EQ} - 0.9$$


$$= 2.0445 \text{ V}$$

$$i_{BQ} = \frac{i_{CA}}{\beta} = 5.5 \text{ mA.}$$

$$\frac{3.3 - V_{BEQ}}{R_1} + 5.5 \text{ mA} = \frac{V_{BEQ}}{R_2}$$

$$\Rightarrow R_2 = 150 \text{ k}\Omega, R_1 = 35.5 \text{ k}\Omega. \text{ (Assumed)}$$

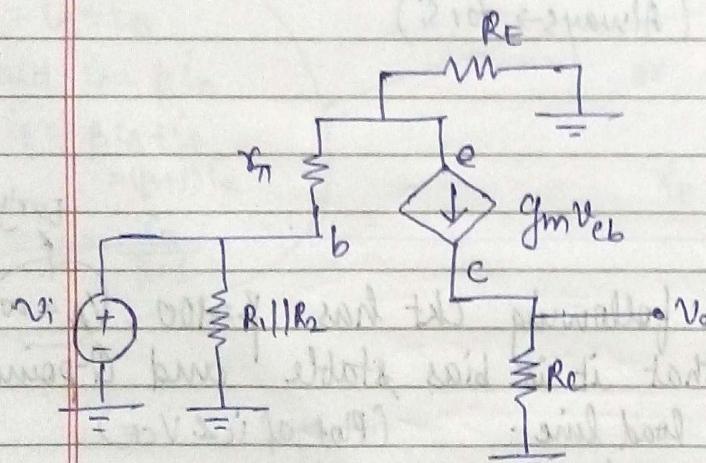→ No current in capacitor branch  $\Rightarrow i_1 + i_B = i_2$ .



$$V_{eb} = V_c - V_i$$

$$V_b = g_m V_{eb} R_c$$

$$= g_m \cancel{R_e} (V_c - V_i)$$

$$= g_m R_c V_i$$

$$(1+\beta) \frac{R_E}{R_T} + 1$$

$$\frac{V_i + V_c}{R_T} = \frac{V_c + g_m (V_c - V_i)}{R_E}$$

$$V_c = \frac{1+\beta}{1+\beta + \frac{g_m}{R_E}} V_i$$

$$1 + \beta + \frac{g_m}{R_E}$$

$$\therefore \frac{V_o}{V_i} = 1.892$$

where  $\beta = g_m R_T$

$$R_T = \frac{\beta}{g_m} = 4.729 \text{ k}\Omega$$

$$V_T = 21.15 \text{ mA/V}$$

$\rightarrow 26 \text{ mV.}$