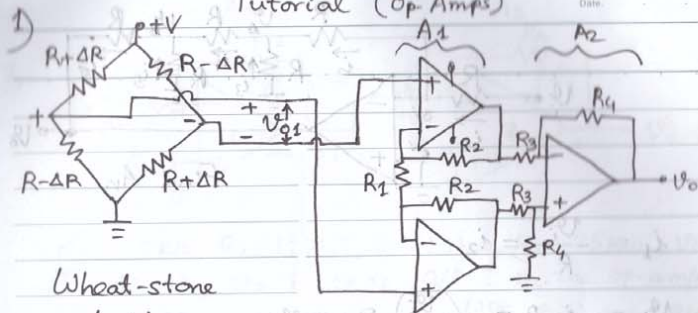


Tutorial (Op-Amps)



Wheat-stone
bridge

→ Calc. values
of R

$$R = 10k\Omega, \Delta R = 50\Omega, +V = 3.5V$$

Design an amp. for $V_0 = 5V$ when $\Delta R = 50\Omega$

$$\text{Sol}^n: V_{01} = \left[\frac{R - \Delta R}{(R - \Delta R) + (R + \Delta R)} - \frac{R + \Delta R}{(R + \Delta R) + (R - \Delta R)} \right] V$$

(V-divider eqⁿs.)

$$= \left[\frac{R - \Delta R}{2R} - \frac{R + \Delta R}{2R} \right] \cdot +V$$

$$= - \frac{\Delta R}{R} \cdot (+V) = - \frac{50}{10 \times 10^3} (3.5) = -1.75 \times 10^{-2} = 17.5 \text{ mV}$$

$$\text{Required gain} = A_d = \frac{V_0}{V_i} = \frac{5}{17.5 \text{ m}} = 285.714$$

For an instrumentation amp,

$$|A_d| = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) = 285.714$$


Assume, $R_3 = 10k\Omega$ & $R_4 = 150k\Omega$

$$\therefore \frac{R_2}{R_1} = 9.02$$

$$\text{Let, } R_2 = 100k\Omega, \therefore R_1 = 11.1k\Omega$$

(Ans)

2.

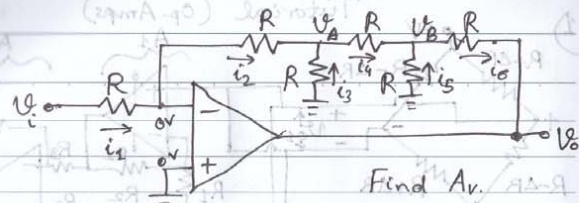

Find A_v .

$$i_1 = \frac{V_i}{R} = i_2$$

$$V_A = -i_2 \cdot R = -\left(\frac{V_i}{R}\right) \cdot R = -V_i$$

$$i_3 = i_1 - \frac{V_A}{R} = -\frac{V_i}{R}$$

$$i_4 = i_2 + i_3 = -\frac{V_A}{R} - \frac{V_A}{R} = -\frac{2V_A}{R} = +\frac{2V_i}{R}$$

$$V_B = V_A - i_4 \cdot R = -V_i - \left[\frac{2V_i}{R}\right] \cdot R = -3V_i$$


$$i_5 = -\frac{V_B}{R} = -\frac{-3V_i}{R} = \frac{3V_i}{R}$$

$$i_6 = i_4 + i_5 = \frac{2V_i}{R} + \frac{3V_i}{R} = \frac{5V_i}{R}$$

$$V_o = V_B - i_6 \cdot R = -3V_i - \left(\frac{5V_i}{R}\right) \cdot R = -8V_i$$

$$\Rightarrow \frac{V_o}{V_i} = A_v = -8 \quad (\text{Ans})$$

3.

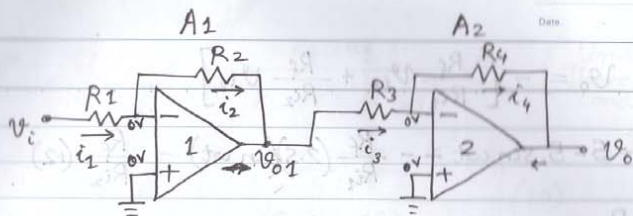

$$R_1 = 20k\Omega, R_2 = 120k\Omega, R_3 = 15k\Omega, R_4 = 75k\Omega, V_i = 0.2V$$

Find: V_{o1}, V_o, i_1 to i_4 , O/P I in the op-amps.

$$\text{Sol}^n \quad V_{o1} = -\frac{R_2}{R_1} \cdot V_i = -\frac{120k}{20k} \cdot (0.2) = -1.2V \quad (\text{Ans})$$

$$V_o = -\frac{R_4}{R_3} \cdot V_{o1} = -\frac{75k}{15k} \cdot (-1.2) = +6V \quad (\text{Ans})$$


$$i_1 = i_2 = \frac{0.2}{20k} = 10\mu A \quad (\text{Ans})$$

$$i_3 = i_4 = \frac{V_{o1}}{R_3} = \frac{-1.2}{15k} = -80\mu A \quad (\text{Ans})$$

$$\left. \begin{aligned} \text{O/P I (op-amp. 1)} &= -(10\mu + 80\mu) = -90\mu A \\ \text{O/P I (op-amp. 2)} &= +80\mu A \end{aligned} \right\} \begin{array}{l} \text{Sink I} \\ \text{Source I} \end{array} \quad (\text{Ans})$$

4. Design a summing amp: $V_i = (2.5)\sin\omega t$ (V), $V_{i2} = +2V$, $V_o = -5(1 + \sin\omega t)$ (V). Largest R is $200k\Omega$.

Solⁿ.

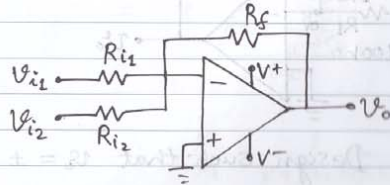

$$V_o = - \left[\frac{R_f}{R_{i1}} V_{i1} + \frac{R_f}{R_{i2}} V_{i2} \right]$$

$$\Rightarrow -5 = 5 \sin \omega t = - \frac{R_f}{R_{i1}} (2.5 \sin \omega t) - \frac{R_f}{R_{i2}} (2)$$

By separating LHS & RHS elements,

$$5 = \frac{R_f}{R_{i2}} \cdot 2$$

$$\Rightarrow \frac{R_f}{R_{i2}} = 2.5$$

Indicates $\Rightarrow R_f > R_{i2}$


$\therefore R_f = 200 \text{ k}\Omega$ (largest R in the ckts)

Now,

$$5 \sin \omega t = \frac{200 \text{ k}\Omega}{R_{i1}} \cdot (2.5 \sin \omega t)$$

$$\Rightarrow R_{i1} = \frac{200 \text{ k}\Omega \cdot (2.5)}{5} = 100 \text{ k}\Omega \text{ (Ans)}$$
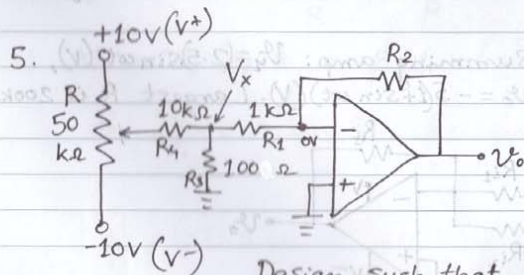
$$\text{Also, } R_{i2} = \frac{R_f}{2.5} = \frac{200 \text{ k}\Omega}{2.5} = 80 \text{ k}\Omega \text{ (Ans)}$$



Design such that $V_o = \pm 10 \text{ V}$.

Soln. $V_{x(\max)} = \frac{R_3 \parallel R_4}{R_3 \parallel (R_1 + R_4)} \cdot V^+$ (Under Thevenin's condition)

$$= \frac{(0.1)(1)}{0.1+1} \cdot (10)$$

$$= \frac{(0.1)(1+10)}{0.1+1+10}$$


$$= 0.090 \text{ V}$$

Now,

$$|V_o| = \frac{R_2}{R_1} \cdot V_{x(\max)}$$

$$\Rightarrow 10 = \frac{R_2}{1 \text{ k}} (0.090)$$
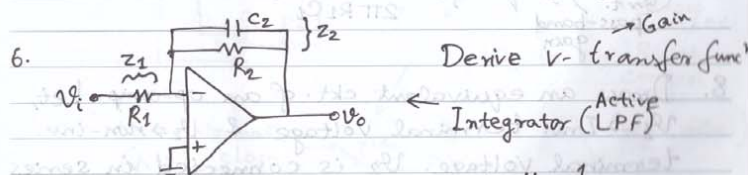
$$\Rightarrow R_2 = 111 \text{ k}\Omega \text{ (Ans)}$$




Soln. $A_v = \frac{V_o}{V_i} = - \frac{Z_2}{Z_1} = - \frac{R_2 \parallel \frac{1}{j\omega C_2}}{R_1}$

$$= - \frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}}$$

$$= - \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2} \text{ (Ans)}$$

Corner

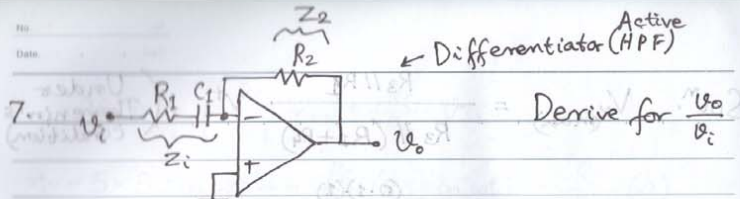(-3 db) freq. = $f_c = \frac{1}{2\pi R_2 C_2}$ w.r.t. pass-band gain



Solⁿ. Assume the op-amp is an ideal one.


$$\frac{V_o}{V_i} = - \frac{Z_2}{Z_1} = - \frac{R_2}{R_1 + \frac{1}{j\omega C_1}}$$

$$= - \frac{R_2 (j\omega C_1)}{1 + j\omega R_1 C_1}$$



$$= - \frac{R_2}{R_1} \cdot \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \quad (\text{Ans})$$

Corner
(-3 db) freq: $f_c = \frac{1}{2\pi R_1 C_1}$
pass-band gain

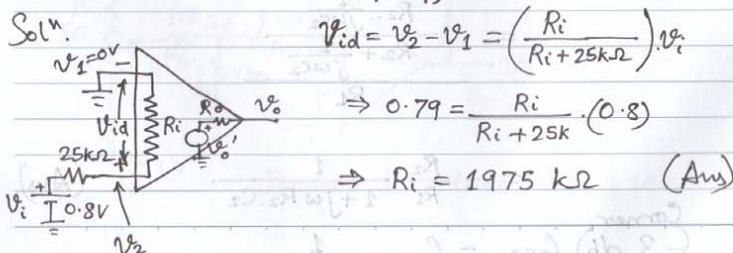8. Draw an equivalent ckt. of an op-amp. Let, $V_1 \Rightarrow$ Inv. terminal voltage & $V_2 \Rightarrow$ non-inv. terminal voltage. V_2 is connected in series with a 25k Ω resistor from a source of 0.8V & $V_1 = 0$ V. What is R_{im} such that $V_{id} = 0.79$ V?



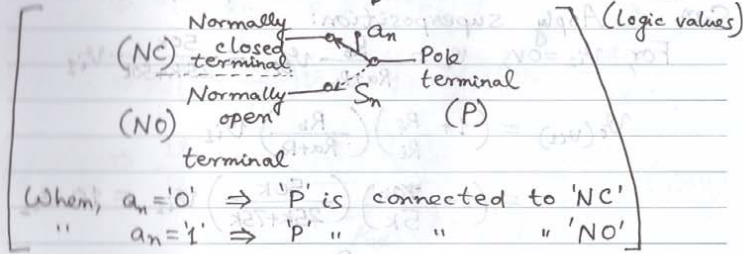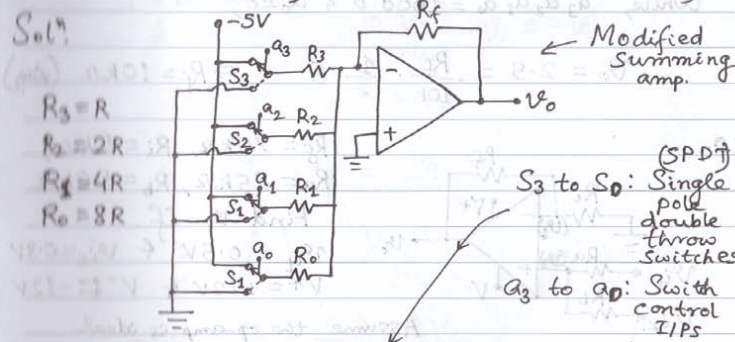9. Draw the circuit of a digital-to-analog converter by using op-amp. Write the expression for its O/P voltage as a function of digital logic. Find the feedback resistor's value such that $V_o = +2.5$ V while digital I/Ps are: $a_3 a_2 a_1 a_0 = 1000$, where, a_3 is the most significant bit, & a_0 is the least significant bit.



$$V_o = - \frac{R_f}{R_3} \cdot a_3 \cdot (-5) - \frac{R_f}{R_2} \cdot a_2 \cdot (-5) - \frac{R_f}{R_1} \cdot a_1 \cdot (-5) - \frac{R_f}{R_0} \cdot a_0 \cdot (-5)$$

$$= \frac{R_f}{R} \cdot a_3 (5) + \frac{R_f}{2R} \cdot a_2 (5) + \frac{R_f}{4R} \cdot a_1 (5) + \frac{R_f}{8R} \cdot a_0 (5)$$

No. _____
Date _____

Let, $R = 20k\Omega$


$$V_o = \frac{R_f}{20k} a_3 \cdot 5 + \frac{R_f}{40k} a_2 \cdot 5 + \frac{R_f}{80k} a_1 \cdot 5 + \frac{R_f}{160k} a_0 \cdot 5$$

$$\therefore V_o = \frac{R_f}{10k} \left[\frac{a_3}{2} + \frac{a_2}{4} + \frac{a_1}{8} + \frac{a_0}{16} \right] (5) \quad (\text{Ans})$$

While, $a_3 = 1, a_2 = 0, a_1 = 0 \text{ \& } a_0 = 0$;

$$V_o = 2.5 = \frac{R_f}{10k} \cdot \frac{1}{2} \cdot 5 \Rightarrow R_f = 10k\Omega \quad (\text{Ans})$$

10.

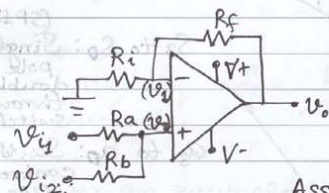

$R_f = 70k\Omega, R_i = 5k\Omega,$
 $R_a = 25k\Omega, R_b = 50k\Omega$
Find V_o if
 $V_{i1} = 0.5V$ & $V_{i2} = 0.8V$
 $V^+ = +12V$ & $V^- = -12V$

Assume the op-amp is ideal.

Solⁿ. Apply superposition:

For, $V_{i2} = 0V, V_2 = \frac{R_b}{R_a + R_b} V_{i1} = \frac{50k}{25k + 50k} \cdot V_{i1}$

$$V_o(V_{i1}) = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{R_b}{R_a + R_b}\right) V_{i1}$$

$$= \left(1 + \frac{70k}{5k}\right) \left(\frac{50k}{25k + 75k}\right) V_{i1} = 10 V_{i1}$$

For, $V_{i1} = 0V, V_2 = \frac{R_a}{R_a + R_b} V_{i2}$

$$V_o(V_{i2}) = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{R_a}{R_a + R_b}\right) V_{i2} = 5 V_{i2}$$


$$V_o = V_o(V_{i1}) + V_o(V_{i2})$$

$$= 10 V_{i1} + 5 V_{i2} \checkmark$$

$$= 10(0.5) + 5(0.8) = 9V \quad (\text{Ans})$$

11. Derive the eqⁿ of the gain of a practical non-inv. amp. using an op-amp.

Solⁿ.

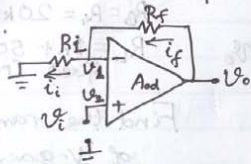

$$V_o = A_{od}(V_2 - V_1)$$

$$\Rightarrow V_o = A_{od}(V_i - V_1)$$

$$\Rightarrow \frac{V_o}{A_{od}} - V_i = -V_1$$

or, $V_1 = V_i - \frac{V_o}{A_{od}}$

Now,

$$i_i = \frac{V_1}{R_i} = i_f = \frac{V_o - V_i}{R_f}$$


$$\therefore V_1 \left(\frac{1}{R_i}\right) = \frac{V_o - V_i}{R_f}$$

$$\Rightarrow V_1 \left(\frac{1}{R_i} + \frac{1}{R_f}\right) = \frac{V_o}{R_f}$$

$$\Rightarrow V_o \left(1 + \frac{R_f}{R_i}\right) V_1 = \left(1 + \frac{R_f}{R_i}\right) \left(V_i - \frac{V_o}{A_{od}}\right)$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{\left(1 + \frac{R_f}{R_i}\right)}{1 + \frac{1}{A_{od}} \left(1 + \frac{R_f}{R_i}\right)} \quad (\text{Ans})$$

12. Consider an instrumentation amp.

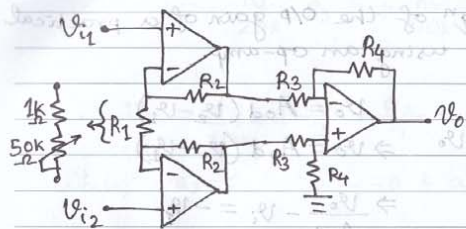

$$R_2 = 100 \text{ k}\Omega$$

$$R_3 = R_4 = 20 \text{ k}\Omega$$

$$R_1 = 1 \text{ k}\Omega + 50 \text{ k}\Omega \text{ (fixed) (pot.)}$$

Find the range of V-gain.

$$\text{Sol}^n. \quad V_o = -\frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (V_{i2} - V_{i1})$$

$$\text{Differential gain} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right)$$

Gain is inversely proportional to R_1 .

Min. $R_1 \Rightarrow$ Max. gain. $\Rightarrow R_1 = 1 \text{ k}\Omega$



$$\therefore A_d = \frac{20 \text{ k}}{20 \text{ k}} \left(1 + \frac{2(100 \text{ k})}{1 \text{ k}} \right) = 201$$

Max. $R_1 \Rightarrow$ Min. gain $\Rightarrow R_1 = 51 \text{ k}\Omega$


$$\therefore A_d = \frac{20 \text{ k}}{20 \text{ k}} \left(1 + \frac{2(100 \text{ k})}{51 \text{ k}} \right) = 4.92$$

\therefore Range of differential gain: $A_{od} = 4.92 \text{ to } 201$ (Ans)

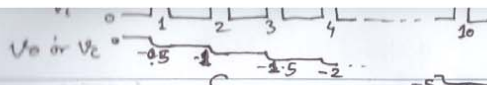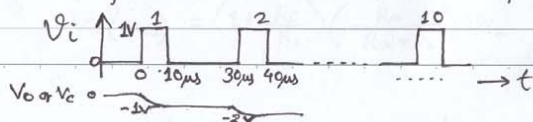13. Consider an op-amp integrator (ideal). Find R, if $C = 10 \text{ nF}$ & $V_o = -5 \text{ V}$ after 10's pulse.



Solⁿ.

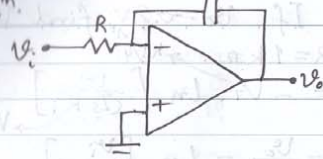

$$V_o = \frac{1}{RC} \int_0^t V_i(t) dt$$

$$\text{and } \tau = RC$$

End of 1st pulse:

$$V_o = -\frac{1}{\tau} \cdot t \Big|_0^{10 \mu\text{s}}$$

$$= \frac{-10 \times 10^{-6}}{\tau}$$

$$\text{After 10th pulse, } V_o = -5 = \frac{-10(10 \times 10^{-6})}{\tau}$$

$$\Rightarrow \tau = 20 \mu\text{s}$$

$$\Rightarrow RC = 20 \mu\text{s}$$

$$\Rightarrow R = \frac{20 \mu\text{s}}{C}$$

$$= \frac{20 \mu\text{s}}{10 \text{ nF}} = 2 \text{ k}\Omega$$

(Assume, C does not discharge while $V_i = 0$) (Ans)

14. Draw a V-follower & find closed loop gain if the open loop differential gain (A_{od}) is 10^4 & 10.

$$\text{Sol}^n. \quad V_o = A_{od} (V_i - V_o)$$

$$\Rightarrow \left(\frac{1}{A_{od}} + 1 \right) V_o = V_i$$


$$\Rightarrow \frac{V_o}{V_i} = \frac{1}{1 + \frac{1}{A_{od}}} = A_v$$

$$\text{If } A_{od} = 10^4, \quad \frac{V_o}{V_i} = 0.999$$

$$\text{If } A_{od} = 10, \quad \frac{V_o}{V_i} = 0.909$$

Precision op amp
(Ans)
Poorly designed

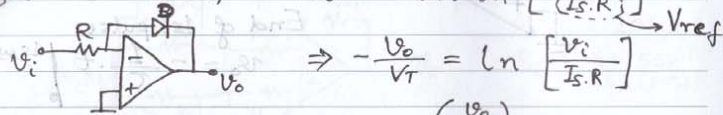15. Consider a log amp. If $V_o = -0.3V$, find V_i if $I_{s(p)} = 20fA$ & $R = 1k\Omega$.
 Solⁿ. We know, $V_o = -V_T \ln \left[\frac{V_i}{I_{s(p)} R} \right]$



$$\Rightarrow -\frac{V_o}{V_T} = \ln \left[\frac{V_i}{I_{s(p)} R} \right]$$

$$\Rightarrow I_{s(p)} R \cdot e^{\left(-\frac{V_o}{V_T}\right)} = V_i$$

$$\Rightarrow V_i = 20 \times 10^{-15} \times 1 \times 10^3 \cdot e^{\left(\frac{-0.3}{0.026}\right)}$$

$$\therefore V_i = 2.051 \mu V$$

@ $V_o = -0.3V$
 @ $27^\circ C$

Also, @ $V_o = -0.6V$

$$V_i = 20 \times 10^{-15} \times 1 \times 10^3 \cdot e^{\frac{-0.6}{0.026}}$$

$$= 0.210V$$

$$\therefore V_i = 2.051 \mu V \Rightarrow V_o = -0.3V ; A_v = \frac{V_o}{V_i} = \frac{-0.3}{2.051 \times 10^{-6}} = -146.3$$

$$V_i = 0.210V \Rightarrow V_o = -0.6V ; A_v = \frac{V_o}{V_i} = \frac{-0.6}{0.210} = -2.86$$

\therefore Log amp. acts like a data/value compressor.

16 A Wein-bridge oscillator is required to generate a 5.2 kHz sine wave. Calculate the resistor values & the capacitor values. Find the min. values of the gain setting resistors as well.

Solⁿ. $f_r = \frac{1}{2\pi RC} = 5.2 \times 10^3$

$kHz \rightarrow \mu F$
 $MHz \rightarrow pF$

Let $R_1 = R_2$ & $C_1 = C_2$

Let, $C = C_1 = C_2 = 3 nF$

$$\therefore R = R_1 = R_2 = \frac{1}{2\pi f_r C} = \frac{1}{2\pi \times 5.2 \times 10^3 \times 3 \times 10^{-9}}$$

$$= 10.2 k\Omega$$

For a sine-wave oscillation, $A_v \geq 3$ (Wein bridge only)

While considering a non-inv. op-amp amp:
 $A_v = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i} \geq 3$ (op-amp is an ideal)


Let, $R_f = 100 k\Omega$

$$\Rightarrow R_i = \frac{R_f}{A_v - 1} = \frac{100 \times 10^3}{3 - 1} = 50 k\Omega$$

$\therefore R_1 = R_2 = 10.2 k\Omega$

Assumed $\left\{ \begin{array}{l} C_1 = C_2 = 3 nF \\ R_f = 100 k\Omega \\ R_i = 50 k\Omega \end{array} \right.$ (Ans)

Calculated

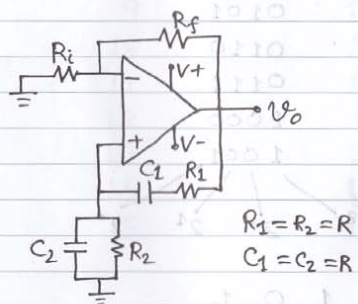

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

MOSFET Tutorial (cont.)

5 (cont.) By solving the quadratic equation,

$$V_{SG} = \frac{-0.4 \pm \sqrt{(0.4)^2 + 4(0.3)(3.986)}}{2 \cdot (0.3)}$$

$$= +3.04V \quad (\text{Considering the +ve answer only})$$

$$\text{Now, } I_D = (0.25m) [3.04 + 1]^2 = 1.04 \text{ mA} \quad (\text{Ans})$$


$$\begin{aligned} \text{Also, } V_{SD} &= (V_{SS} - V_{DD}) - I_D (R_S + R_D) \\ &= 10 - [(1.04m)(1.2k + 4k)] \\ &= 4.59V \quad (\text{Ans}) \end{aligned}$$

For confirmation about saturation mode,

$$V_{SD(sat)} = V_{SG} - V_{TP} = 3.04 - 1 = 2.04V$$

$$\therefore V_{SD} > V_{SD(sat)}$$

6.

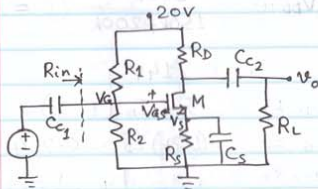

$$A_v = \frac{V_o}{V_i} = -10$$


$$R_L = 20k\Omega, R_{in} = 200k\Omega,$$

$$I_{DQ} = 1mA, V_{DSQ} = 10V,$$

$$V_{TP} = 2V, \lambda = 0$$

Find R_1, R_2, R_D, R_S .

Solⁿ. Small signal eqn. ckt. (AC)

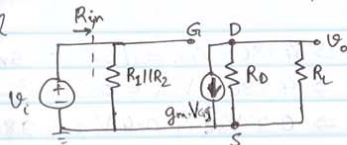

180° phase shift

$$A_v = -g_m (R_D || R_L)$$

$$V_{DSQ} = V_{DD} - I_{DQ} (R_D + R_S)$$

$$\Rightarrow 10 = 20 - (1m)(R_D + R_S) \Rightarrow R_D + R_S = 10k\Omega \quad [R_D > R_S]$$

$$\text{Let, } R_D = 8k\Omega \quad \therefore R_S = 2k\Omega \quad (\text{Ans})$$

$$\Rightarrow -10 = -g_m (8k || 20k)$$

$$\Rightarrow g_m = 1.75 \text{ mA/V} = 2\sqrt{K_n \cdot I_{DQ}} = 2\sqrt{K_n (1m)}$$

$$\Rightarrow K_n = 0.766 \text{ mA/V}^2$$

Now,

$$V_S = I_{DQ} \cdot R_S = (1m)(2k) = 2V$$

$$\text{Saturation current: } I_{DQ} = K_n (V_{GS} - V_{TP})^2$$

$$\Rightarrow 1m = 0.766 (V_{GS} - 2)^2$$

$$\Rightarrow V_{GS} = 3.14V$$

$$V_G = V_{GS} + V_S = 3.14 + 2 = 5.14V$$


$$\& V_G = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD} = \frac{1}{R_1} (200k)(20) = 5.14V$$

$$\Rightarrow R_1 = 778k\Omega \quad (\text{Ans})$$

$$\text{Also, } R_{in} = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad [\because R_{in} = R_1 || R_2]$$

$$\Rightarrow 200k = \frac{778k \cdot R_2}{778k + R_2} \Rightarrow R_2 = 269k\Omega \quad (\text{Ans})$$

7.

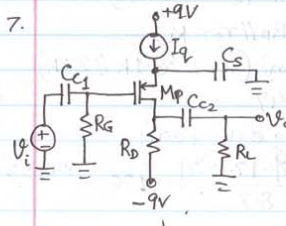


$$R_G = 500k\Omega, V_{TP} = -1.5V,$$

$$K_p = 2mA/V^2, \lambda = 0.01V^{-1},$$

$$R_L = 20k\Omega, R_D \leq 0.1 R_L$$

- Find I_Q for q-pt at the center of the saturation reg.
- Open ckt ($R_L = \infty$) & closed load ckt gain

Soln. a.

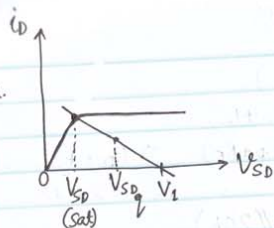

$$V_1 = 9 + V_{SG}$$

$$V_{SD(sat)} = V_{SG} + V_{TP}$$

$$V_{SDQ} = \frac{V_1 - V_{SD(sat)}}{2} + V_{SD(sat)}$$

$$\Rightarrow V_{SDQ} = \frac{(9 + V_{SG}) - (V_{SG} + V_{TP})}{2} + (V_{SG} + V_{TP})$$

$$= \frac{9 + 1.5}{2} + V_{SG} - 1.5$$

$$= 3.75 + V_{SG}$$

$$= 9 + V_{SG} - I_{DQ} \cdot R_D$$

$$4 \quad I_{DQ} = K_p (V_{SG} + V_{TP})^2$$

$$R_D = 0.1(R_L) = (0.1)(20k) = 2k\Omega$$

$$\therefore 3.75 = 9 - I_{DQ}(2k) \Rightarrow I_{DQ} = 2.625 \text{ mA} \quad (\text{Ans})$$

$$b \quad g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2m)(2.625m)} = 4.58 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(2.625m)} = 38.1k\Omega$$

Gain without R_L (or $R_L = \infty$)

$$A_v = -g_m (R_D \parallel r_o)$$

$$= -(4.58m)(2k \parallel 38.1k) = -8.70 \quad (\text{Ans})$$

Gain with R_L (or $R_L = 20k\Omega$)

$$A_v = -g_m (R_D \parallel r_o \parallel R_L)$$


$$= -(4.58m)(2k \parallel 38.1k \parallel 20k)$$

$$= -7.947 \quad (\text{Ans})$$

\therefore Percentage change in gain:

$$100 \times \frac{A_{v, \text{No load}} - A_{v, \text{load}}}{A_{v, \text{No load}}} = \frac{8.7 - 7.947}{8.7} \times 100 = 8.655\% \quad (\text{Ans})$$

8.

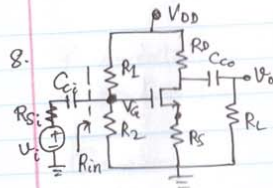

$$V_{TN} = 2V, K_n = 1 \text{ mA/V}^2, \lambda = 0, \\ V_{DD} = 12V, R_S = 2k\Omega, R_D = 3k\Omega, \\ R_1 = 300k\Omega, R_2 = 200k\Omega, R_S = 2k\Omega, \\ R_L = 3k\Omega. \text{ Find } I_{DQ}, V_{DSQ}, A_v.$$

$$\text{Soln. } V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{200k}{200k + 300k} \cdot 12 = 4.8V$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2 \quad (\text{sat. mode})$$

$$\Rightarrow 4.8 - V_{GS} = (1m)(V_{GS} - 2)^2 (2k)$$

$$\Rightarrow 2V_{GS}^2 - 7V_{GS} + 3.2 = 0$$

$$\Rightarrow V_{GS} = \frac{7 \pm \sqrt{7^2 - 4(2)(3.2)}}{2 \cdot 2} \Rightarrow 2.96V = V_{GS}$$

$$\text{Now, } I_{DQ} = (1m)(2.96 - 2)^2 = 0.920 \text{ mA} \quad (\text{Ans})$$

$$\text{Also, } V_{DSQ} = V_{DD} - I_D (R_D + R_S)$$

$$= 12 - (0.92m)[3k + 2k] = 7.4V \quad (\text{Ans})$$

$$V_o = \frac{-g_m V_G (R_D \parallel R_L)}{1 + g_m R_S}; \quad V_G = \frac{R_1 \parallel R_2}{(R_1 \parallel R_2) + R_S} \cdot V_i$$

$$\therefore A_v = \frac{-g_m (R_D \parallel R_L) [0.9836]}{1 + g_m R_S}$$

$$= \frac{300k \parallel 200k}{(300k \parallel 200k) + 2k} \cdot V_i$$

$$= (0.9836) V_i$$

Factor for R_S V-drop

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(1m)(0.92m)} = 1.92 \text{ mA/V}$$

$$\therefore A_v = \frac{(-1.92m)(3k \parallel 2k) [0.9836]}{1 + (1.92m)(2k)} = -0.585 \quad (\text{Ans})$$

$\Rightarrow A_v < 1$ (attenuation)