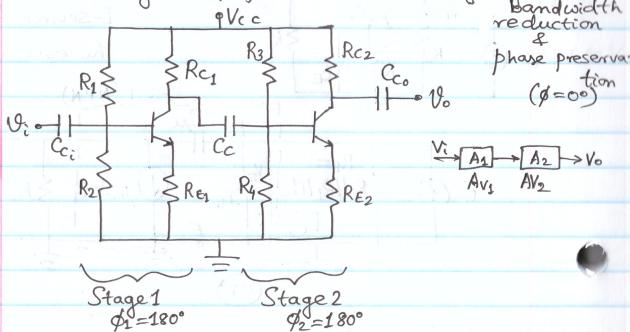


$$f_{3\text{db}} = \frac{1}{2\pi (R_B/(r_m)(C_{\pi} + C_M))}$$

(LPF like)





16. Two - stage amplifier: Obtains a larger gain w/o



$$\text{Gain: } Av = |Av_1| \cdot |Av_2|$$

$$\phi = \phi_1 + \phi_2$$

17. Equivalent 2-port networks:

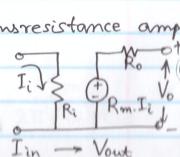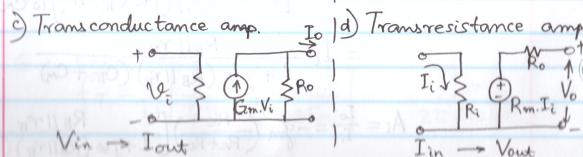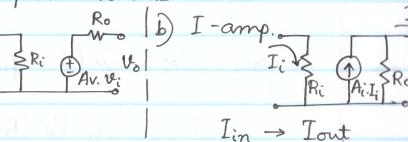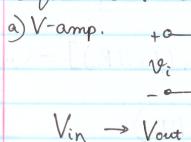

## Tutorial (BJTs)

1. Calculate  $\beta$ ,  $\alpha$  &  $I_c$  if  $I_B = 10.2\mu\text{A}$  &  $I_E = 0.9\text{mA}$

Sol<sup>m</sup>:  $I_E = (1+\beta) I_B$   
 $\Rightarrow \beta = \frac{I_E}{I_B} - 1 = \frac{0.9 \times 10^{-3}}{10.2 \times 10^{-6}} - 1 = 87.23$   $\checkmark$  (Ans)

Now,  $\alpha = \frac{\beta}{1+\beta} = \frac{87.23}{87.23+1} = 0.988$   $\checkmark$  (Ans)

And,  $I_c = \alpha \cdot I_E = (0.988)(0.9 \times 10^{-3}) = 0.889 \text{ mA}$  (Ans)

2. Find  $r_o$  if  $V_A = 190\text{V}$  &  $I_c = 2.2\text{mA}$

Sol<sup>m</sup>:  $r_o = \frac{V_A}{I_c} = \frac{190}{2.2 \times 10^{-3}} = 86.363 \text{ k}\Omega$  (Ans)

3. Find  $I_c$  at  $V_{CE} = 12\text{V}$ . Given,  $I_{c0} = 1.3\text{mA}$  @  $V_{CE0} = 0.7\text{V}$ ,  $V_A = 200\text{V}$ . Assume  $V_{BE(on)}$  is constant.

Sol<sup>m</sup>: We know,  $I_c = [I_{c0} \cdot (e^{\frac{V_{BE}}{V_T}})] \left(1 + \frac{V_{CE}}{V_A}\right) = I_{c0} \cdot (1 + \frac{V_{CE}}{V_A})$


$$\Rightarrow 1.3 \times 10^{-3} = I_{c0} \cdot \left(1 + \frac{1.5}{200}\right)$$

$$\Rightarrow I_{c0} = 1.29 \times 10^{-3} \text{ A}$$

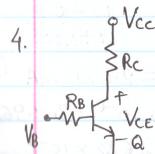i. At  $V_{CE} = 12\text{V}$ ,

$$I_c = 1.29 \times 10^{-3} \left(1 + \frac{12}{200}\right)$$

$$= 1.367 \text{ mA} @ V_{CE} = 12\text{V}$$
 (Ans)




Let,  $V_{CC} = 5\text{V}$ ,  $V_B = 2.2\text{V}$ ,  $R_C = 4.2\text{k}\Omega$ ,  $R_B = 220\text{k}\Omega$ ,  $\beta = 150$ ,  $V_{BE(on)} = 0.7\text{V}$ . Calculate  $I_B$ ,  $I_c$ ,  $V_{CE}$  &  $P_{transistor}$ .

$$\text{Soln. } I_B = \frac{V_B - V_{BE(on)}}{R_B} = \frac{2.2 - 0.7}{220 \times 10^3} = 6.818 \mu\text{A} \quad (\text{Ans})$$

$$I_C = \beta \cdot I_B = 6.818 \times 10^{-6} \times 150 = 1.022 \text{ mA} \quad (\text{Ans})$$

$$V_{CE} = V_{CC} - I_C \cdot R_C = 5 - [(1.022 \times 10^{-3})(4.2 \times 10^3)] \\ = 0.707 \text{ V, Forward active mode} \quad (\text{Ans})$$
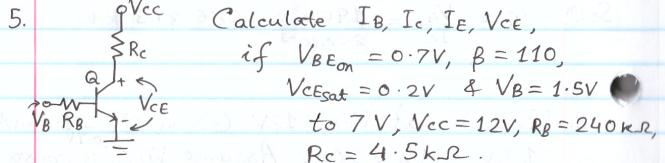
$$P_{\text{transistor}} = I_B \cdot V_{BE(on)} + I_C \cdot V_{CE} \\ = (6.818 \times 10^{-3})(0.7) + (1.022 \times 10^{-3})(0.707) \\ = 5.495 \text{ mW} \quad (\text{Ans})$$



$$\text{Soln. } I_B = \frac{V_B - V_{BE(on)}}{R_B} = \frac{1.5 - 0.7}{240 \times 10^3} = 3.333 \mu\text{A} \quad (\text{Ans})$$

$$\frac{I_B}{@V_B=7\text{V}} = \frac{7 - 0.7}{240 \times 10^3} = 26.25 \mu\text{A} \quad (\text{Ans})$$

$$I_{C,1.5V} = \beta \cdot I_B = 110 \times 3.333 \times 10^{-6} = 366.63 \mu\text{A} \quad (\text{Ans})$$


$$V_{CE} = V_{CC} - I_C \cdot R_C \Rightarrow V_{CE} > 0.2 \text{ V}$$

(likely)  
 $I_{C,7V} \Rightarrow$  Transistor is in saturation mode.

$$\therefore I_{C,7V} = \frac{V_{CC} - V_{CE(sat)}}{R_C} = \frac{12 - 0.2}{4.5 \times 10^3} \\ = 2.622 \mu\text{A} \quad (\text{Ans})$$

$$I_{E,1.5V} = (1+\beta) I_B = (1+110) 3.333 \times 10^{-6} = 369.963 \mu\text{A} \quad (\text{Ans})$$
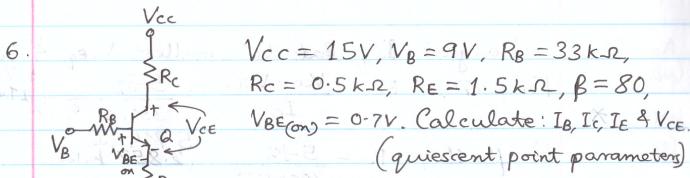
$$I_{E,7V} = I_B + I_C = 26.25 \times 10^{-6} + 2.622 \times 10^{-3} \\ = 2.648 \text{ mA} \quad (\text{Ans})$$




$$\text{Soln. } I_B = \frac{V_B - V_{BE(on)}}{R_B + (1+\beta) R_E} = \frac{9 - 0.7}{33 \times 10^3 + (1+80) \times 1.5 \times 10^3} \\ = 53.721 \mu\text{A} \quad (\text{Ans})$$

$$I_C = \beta \cdot I_B = 80 \times 53.721 \times 10^{-6} \\ = 4.297 \text{ mA} \quad (\text{Ans})$$

$$I_E = (1+\beta) I_B = (1+80) \times 53.721 \times 10^{-6} \\ = 4.351 \text{ mA} \quad (\text{Ans})$$
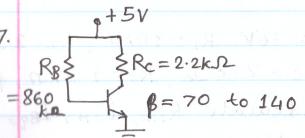
$$V_{CE} = V_{CC} - I_C \cdot R_C - I_E \cdot R_E \\ = 15 - (4.297 \times 10^{-3})(0.5 \times 10^3) - (4.351 \times 10^{-3})(1.5 \times 10^3) \\ = 6.325 \text{ V} \quad (\text{Ans})$$



Find a new  $R_C$  such that the q-pt will be in the range  $V_{CEq} = 1$  to  $3 \text{ V}$ . What is the actual range of  $V_{CEq}$  for the new  $R_C$ ?

$$\text{Soln. } I_{Bq} = \frac{V_{CC} - V_{BE(on)}}{R_B} = \frac{5 - 0.7}{860 \times 10^3} = 5 \mu\text{A}$$

$$\text{For } \beta = 70, I_{Cq} = \beta \cdot I_{Bq} = 70 \times 5 \times 10^{-6} = 350 \mu\text{A}$$

$$\text{For } \beta = 140, I_{Cq} = 140 \times 5 \times 10^{-6} = 700 \mu\text{A}$$

Largest  $I_{CQ}$  leads to smallest  $V_{CEQ}$  & vice-versa  
 For  $\beta = 70$ ,  $R_C = \frac{V_{CC} - V_{CEQ}}{I_{CQ}} = \frac{5-3}{350 \times 10^{-6}} = 5.714 \text{ k}\Omega$  (Ans)

For  $\beta = 140$ ,  $R_C = \frac{5-1}{700 \times 10^{-6}} = 1 \text{ k}\Omega$  (Ans)


Nominal  $I_{CQ_{nom.}} = \frac{350 \times 10^{-6} + 700 \times 10^{-6}}{2} = 525 \mu\text{A}$

Nominal  $V_{CEQ_{nom.}} = \frac{1+3}{2} = 2 \text{ V}$


Nominal  $R_C_{nom.} = \frac{V_{CC} - V_{CEQ_{nom.}}}{I_{CQ}} = \frac{5-2}{525 \times 10^{-6}} = 5.714 \text{ k}\Omega$

For  $I_{CQ} = 350 \mu\text{A}$ ,  $V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C$   
 $(@ \beta = 70)$   
 $= 5 - [350 \times 10^{-6}] (5.714 \times 10^3) = 3 \text{ V}$  (Ans)

For,  $I_{CQ} = 700 \mu\text{A}$ ,  $V_{CEQ} = 5 - [700 \times 10^{-6}] (5.714 \times 10^3) = 1 \text{ V}$  (Ans)

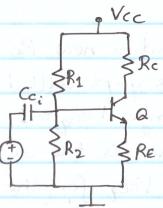8.   
 $V_{CC} = 6 \text{ V}$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 2.5 \text{ k}\Omega$ ,  
 $R_E = 220 \text{ }\Omega$ ,  $R_C = 1.2 \text{ k}\Omega$ ,  $\beta = 160$ .

Calculate  $R_{TH}$ ,  $V_{TH}$ ,  $I_{BQ}$ ,  $I_{CQ}$ , &  $V_{CEQ}$ .

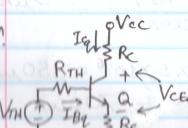
Soln.   
 $R_{TH} = R_1 // R_2 = \frac{10 \text{ k} \times 2.5 \text{ k}}{10 \text{ k} + 2.5 \text{ k}} = 2 \text{ k}\Omega$  (Ans)  
 $V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_{CC} = \frac{2.5 \text{ k}}{10 \text{ k} + 2.5 \text{ k}} \times 6 = 1.2 \text{ V}$  (Ans)

Assume,  $V_{BEon} = 0.7 \text{ V}$

$$I_{BQ} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta) R_E} = \frac{1.2 - 0.7}{2 \times 10^3 + (1+160) 220} = 13.361 \mu\text{A}$$
 (Ans)

$$I_{CQ} = \beta \cdot I_{BQ} = 160 \times 13.361 \times 10^{-6} = 2.137 \text{ mA}$$
 (Ans)  
 $I_{EB} = (1+\beta) I_{BQ} = 2.151 \text{ mA}$   
 $I_{CQ} \cdot R_E + (2.151 \times 10^{-3}) (220)$

$$V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C = 6 - [2.137 \times 10^{-3} (1.2 \times 10^3)] = 2.960 \text{ V}$$
 (Ans)

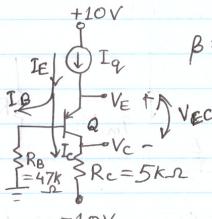9.   
 $\beta = 60$ ,  $I_E = 1.2 \text{ mA}$ . Find  $V_c$  &  $V_E$  &  $V_{EC}$

$$\text{Soln. } I_E = 1.2 \text{ mA}; I_C = \left( \frac{\beta}{1+\beta} \right) I_E = \frac{50}{1+50} \times 1.2 \times 10^{-3} = 1.176 \text{ mA}$$


$$V_C = I_C \cdot R_C + V_{EE} = (1.176 \times 10^{-3}) (5 \times 10^3) - 10 = -3.12 \text{ V}$$
 (Ans)

$$I_B = \frac{I_C}{\beta} = \frac{1.176 \times 10^{-3}}{60} = 19.6 \mu\text{A}$$

$$V_E = I_B \cdot R_B + V_{BEon} = (19.6 \times 10^{-6}) (47 \times 10^3) + 0.7 = 1.621 \text{ V}$$
 (Ans)

$$V_{EC} = V_E - V_C = 1.621 - (-3.12) = 4.74 \text{ V}$$
 (Ans)


10.

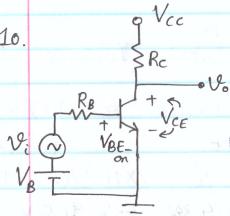

$$V_{CC} = 6V, V_B = 2V, R_B = 640k\Omega, R_C = 12k\Omega, V_{BEon} = 0.7V, \beta = 90$$

Draw the small signal hybrid- $\pi$  model. Find  $g$ -pt values,  $g_m, r_\pi$ . Calculate small-signal  $V$ -gain.

Sol": Small signal hybrid- $\pi$  model:

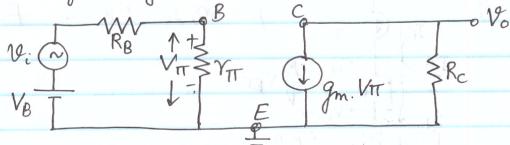

$$I_{BQ} = \frac{V_B - V_{BEon}}{R_B} = \frac{2 - 0.7}{640 \times 10^3} = 2.031 \mu A \quad (\text{Ans})$$

$$I_{CQ} = \beta \cdot I_{BQ} = 90 \times 2.031 \times 10^{-6} = 182.812 \mu A \quad (\text{Ans})$$

$$V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C = 6 - [182.812 \times 10^{-6} \times 12 \times 10^3] \quad (\text{Ans})$$

$$I_{EQ} = I_{BQ} + I_{CQ} = \frac{3.806 \times 10^{-6}}{2.031 \mu A + 182.812 \times 10^{-6}} = 184.843 \mu A \quad (\text{Ans})$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{182.812 \times 10^{-6}}{0.026} = 7.031 \text{ mA/V} \quad (\text{Ans})$$

$$\text{Assume } V_T = 26 \text{ mV}$$


$$r_\pi = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{90 \times 0.026}{182.812 \times 10^{-6}} = 12.800 \text{ k}\Omega \quad (\text{Ans})$$

$$\frac{V_o}{V_i} = A_V = -g_m \cdot R_C \left( \frac{r_\pi}{r_\pi + R_B} \right) \quad [\because A_V = g_m \cdot V_T \cdot R_C]$$

$$= -(7.031 \times 10^{-3}) \times (12.8 \times 10^3) \times \left( \frac{12.8 \times 10^3}{12.8 \times 10^3 + 640 \times 10^3} \right)$$

$$= -1.654 \leftarrow \text{No unit}$$

11.

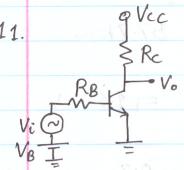

$$V_{CC} = 7V, V_B = 1V, V_A = 200V, \beta = 120, R_C = 15k\Omega, V_{BEon} = 0.7V, R_B = 120k\Omega$$

Calculate  $g_m, r_\pi, r_o$  &  $A_v$ .

must be shown in hybrid- $\pi$

$$\text{Sol": } g_m = \frac{I_{CQ}}{V_T} = \frac{\beta \cdot I_{BQ}}{V_T} = \frac{\beta \cdot (V_B - V_{BEon})}{R_B} = \frac{120 \times \left( \frac{1 - 0.7}{120 \times 10^3} \right)}{0.026} = 11.538 \text{ mA/V} \quad (\text{Ans})$$

$$r_\pi = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{120 \times 0.026}{120 \times \left( \frac{1 - 0.7}{120 \times 10^3} \right)} = 10.4 \text{ k}\Omega \quad (\text{Ans})$$


$$r_o = \frac{V_A}{I_{CQ}} = \frac{200 \times 10^3}{0.3} = 666.666 \text{ k}\Omega \quad (\text{Ans})$$

$$A_v = \frac{V_o}{V_i} = -g_m \left( \frac{r_\pi}{r_\pi + R_B} \right) (r_o // R_C)$$

$$= -(11.538 \times 10^{-3}) \left( \frac{10.4 \text{ k}\Omega}{10.4 \text{ k}\Omega + 120 \text{ k}\Omega} \right) (666.666 \text{ k}\Omega // 15 \text{ k}\Omega)$$



$$= -13.499 \quad (\text{Ans})$$

12.

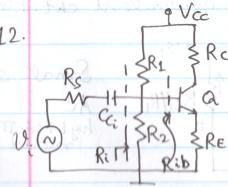

$$V_{CC} = 5V, R_C = 5.6k\Omega, R_E = 0.6k\Omega, \beta = 120, R_1 = 250k\Omega, R_2 = 75k\Omega, V_A = 0, R_S = 0.5k\Omega \text{ & } V_{BEon} = 0.7V$$

Find:  $R_{ib}$  &  $R_{re}$ .

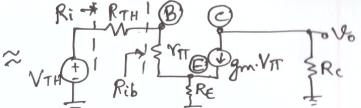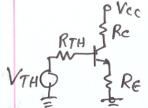

$$\text{Sol'n: } R_{TH} = R_1 // R_2 = \frac{250k \times 75k}{250k + 75k} = 57.7 \text{ k}\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{cc} = \frac{75k}{75k + 250k} \cdot 5 = 1.154 \text{ V}$$

$$I_{Bq} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)RE} = \frac{1.154 - 0.7}{57.7 - (120+1)(0.6k)} = 3.48 \mu\text{A}$$

$$I_{cq} = \beta \cdot I_{Bq} = 120 \times 3.48 \times 10^{-6} = 0.418 \text{ mA}$$

$$g_m = \frac{I_{cq}}{V_T} = \frac{0.418 \times 10^{-3}}{0.026} = 16.08 \text{ mA/V}$$


$$r_{\pi} = \frac{\beta \cdot V_T}{I_{cq}} = \frac{120 \times 0.026}{0.418 \times 10^{-3}} = 7.46 \text{ k}\Omega$$

$$X V_o = -g_m \cdot V_T \cdot R_C$$

$$R_{ib} = r_{\pi} + (1+\beta)RE = 7.46 \text{ k}\Omega + (1+120)(0.6 \times 10^3) = 80.1 \text{ k}\Omega \quad (\text{Ans})$$



$$R_i = R_1 // R_2 + R_{ib} = 57.7 \text{ k} + 80.1 \text{ k} = 137.8 \text{ k}\Omega \quad (\text{Ans})$$

13.

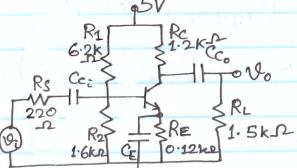

$\beta = 200, r_o = \infty$   
Find small signal hybrid-TT parameters after drawing an equivalent ckt. Find Av

Sol'n.

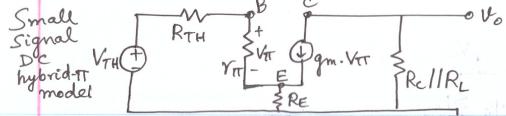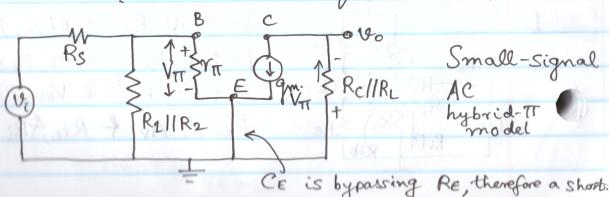

Assume,

$$V_{TR} = V_{BEon} = 0.7 \text{ V}$$

$$R_{TH} = R_1 // R_2 = \frac{6.2k \cdot 1.6k}{6.2k + 1.6k} = 1.271 \text{ k}\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_{cc} = \frac{1.6k}{6.2k + 1.6k} \cdot 5 = 1.025 \text{ V}$$

$$I_{Bq} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)RE} = \frac{1.025 - 0.7}{1.271k + (1+200)0.12k} = 12.799 \mu\text{A}$$

$$I_{cq} = \beta \cdot I_{Bq} = 200 \times 12.799 \times 10^{-6} = 2.559 \text{ mA} \quad (\text{Ans})$$

$$I_{cq} = (1+\beta)I_{Bq} = 2.572 \text{ mA}$$

$$V_{CEq} = V_{cc} - I_{cq} \cdot R_C - I_{cq} \cdot R_E \\ = 5 - (2.559 \text{ m})(1.2k) - (2.572 \text{ m})(0.12k) \\ = 1.620 \text{ V} \quad (\text{Ans})$$


$$r_{\pi} = \frac{\beta \cdot V_T}{I_{cq}} = \frac{200 \times 0.026}{2.559 \times 10^{-3}} = 2.032 \text{ k}\Omega \quad (\text{Ans})$$

$$g_m = \frac{I_{cq}}{V_T} = \frac{2.559 \times 10^{-3}}{0.026} = 98.423 \text{ mA/V} \quad (\text{Ans})$$

$$Av = -g_m \cdot \left[ \frac{R_1 // R_2 // r_{\pi}}{(R_1 // R_2 // r_{\pi}) + R_S} \right] (R_C // R_L)$$

$$= -98.423 \text{ m} \cdot \left[ \frac{6.2k // 1.6k // 2.032k}{(6.2k // 1.6k // 2.032k) + 220} \right] (1.2k // 1.5k)$$

= -

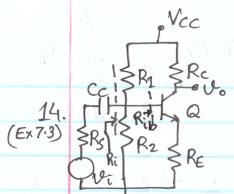

14. (Ex 7.3)  
 $R_S = 0.1 \text{ k}\Omega, R_1 = 20\text{k}, R_2 = 2.2\text{k}, R_E = 0.1\text{k}, R_C = 2\text{k}, C_C = 47\mu\text{F}, V_{CC} = 10\text{V}, V_{BEon} = 0.7\text{V}, \beta = 200, V_A = \infty.$

Find  $\tau_S$  &  $f_c$  &  $A_v$  mid-band.

Sol<sup>n</sup>.

$$\tau_S = (R_i + R_S) \cdot C_C$$

$$f_c = \frac{1}{2\pi\tau_S}$$

$$R_{TH} = R_1 // R_2 = \frac{20\text{k} \cdot 2.2\text{k}}{20\text{k} + 2.2\text{k}} = 1.98\text{k}\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_{CC} = \frac{2.2\text{k}}{20\text{k} + 2.2\text{k}} \cdot 10 = 0.990\text{V}$$

$$I_{Bq} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)R_E} = \frac{0.990 - 0.7}{1.98\text{k} + (1+200) \cdot 0.1\text{k}} = 13.2\mu\text{A}$$

$$I_{Cq} = \beta \cdot I_{Bq} = 200 \cdot 13.2\mu\text{A} = 2.636\text{mA}$$

$$\gamma_\pi = \frac{\beta \cdot V_T}{I_{Cq}} = \frac{200 \times 0.026}{2.636\text{mA}} = 1.97\text{k}\Omega$$

$$g_m = \frac{I_{Cq}}{V_T} = \frac{2.636\text{mA}}{0.026} = 101.4\text{mA/V}$$

$$R_{C_b} = \gamma_\pi + (1+\beta) \cdot R_E = 1.97\text{k} + (1+200) \cdot 0.1\text{k} = 22.1\text{k}\Omega$$

$$R_B = R_1 // R_2 = 1.98\text{k}\Omega$$

$$R_i = R_B // R_{ib} = \frac{1.98\text{k} \cdot 22.1\text{k}}{1.98\text{k} + 22.1\text{k}} = 1.817\text{k}\Omega$$

$$\therefore \tau_S = (R_i + R_S) \cdot C_C = (1.817\text{k} + 0.1\text{k}) \cdot 47\mu\text{F} = 90.099\text{ms}$$

(Ans)

$$f_c = \frac{1}{2\pi\tau_S} = \frac{1}{2\pi \times 90.099\text{ms}} = 1.77\text{Hz}$$


(High pass) (Ans)

$$A_v \text{ mid-band} = \frac{-\beta \cdot R_C}{r_\pi + (1+\beta)R_E} \cdot \frac{R_i}{R_i + R_S}$$


$$= \frac{-(200)(2\text{k})}{1.97\text{k} + (1+200) \cdot 0.1\text{k}} \cdot \frac{1.817\text{k}}{1.817\text{k} + 0.1\text{k}}$$


$$= -17.2$$

DC hybrid- $\pi$  model: Small-signal

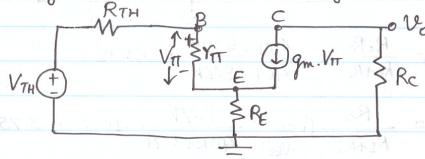


AC hybrid- $\pi$  model: Small Signal

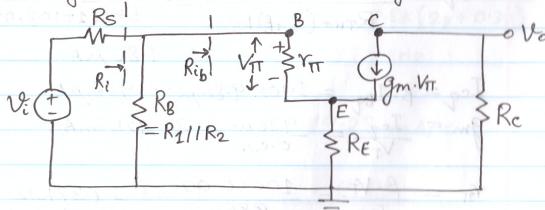

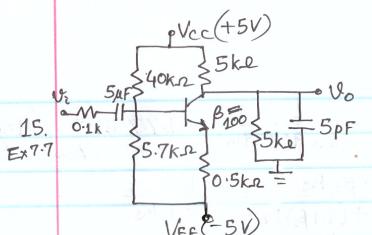

$$V_o = V_i \cdot \frac{R_s + C_c}{R_1 || R_2}$$

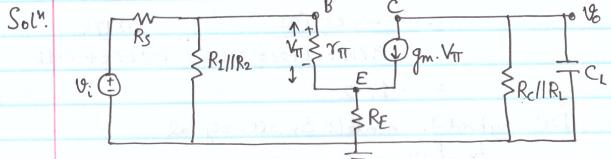Find:  $I_c$ , hybrid- $\pi$  model parameters  $f_{BW}$  & corner frequencies.



$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{40k \cdot 5.7k}{40k + 5.7k} = 5k\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} [V_{CC} - \frac{-V_{EE}}{-V_{EE}}] = \frac{5.7k}{40k + 5.7k} \cdot 10 = -3.752V$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)} - V_{EE}}{R_{TH} + (1+\beta)R_E} = \frac{-3.752 - 0.7 + 5}{5k + (1+100) \cdot 0.5k} = 9.86\mu A$$


$$I_{CQ} = \beta \cdot I_{BQ} = 100 \cdot 9.86\mu = 986\mu A \quad (\text{Ans})$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{986\mu}{0.026} = 37.925 \text{ mA/V} \quad (\text{Ans})$$

$$r_\pi = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{100 \cdot 0.026}{986\mu} = 2.637k\Omega \quad (\text{Ans})$$

$$T_L = (R_c || R_L) C_L = \frac{5k \cdot 5k}{5k + 5k} \cdot 5\text{ pF} = 12.5 \text{ ns}$$
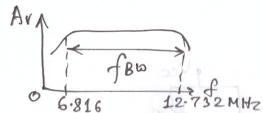
$$R_i = r_\pi + (1+\beta)R_E = 2.637k + (1+100)0.5k = 53.137k\Omega$$



$$T_S = (R_i || R_{TH} + R_s) C_c = \frac{(53.137k \cdot 5k)}{(53.137k + 5k)} + 0.1k \cdot 5\text{ pF}$$

$$= 23.349 \text{ ms}$$

$$\therefore f_L = \frac{1}{2\pi T_S} = \frac{1}{2\pi \times 23.349 \text{ ms}} = 6.816 \text{ Hz} \quad (\text{Ans})$$

$$\therefore f_H = \frac{1}{2\pi T_L} = \frac{1}{2\pi \times 12.5 \text{ ms}} = 12.732 \text{ MHz} \quad (\text{Ans})$$

$$f_{\text{bandwidth}} = f_H - f_L \approx 12.732 \text{ MHz} \quad (\text{Ans})$$

16. Ex 7.9


A BJT has  $\beta_0 = 150$ ,  $C_{\pi} = 2 \text{ pF}$ ,  $C_{\mu} = 0.3 \text{ pF}$ ,  $I_{CQ} = 0.5 \text{ mA}$ , find  $f_B$  (bandwidth) &  $f_T$  (gain-bandwidth product).

$$r_\pi = \frac{\beta_0 \cdot V_T}{I_{CQ}} = \frac{150 \times 0.026}{0.5 \text{ mA}} = 7.8 \text{ k}\Omega$$


$$f_B = \frac{1}{2\pi r_\pi (C_{\pi} + C_{\mu})} = \frac{1}{2\pi \times 7.8 \text{ k} (2 \text{ pF} + 0.3 \text{ pF})} = 8.87 \text{ MHz} \quad (\text{Ans})$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.5 \text{ mA}}{0.026} = 19.23 \text{ mA/V}$$

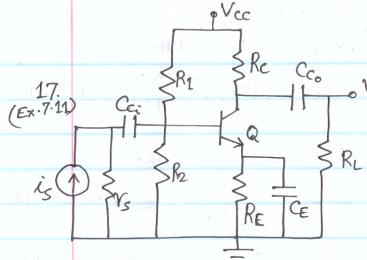
$$f_T = \frac{g_m}{2\pi (C_{\pi} + C_{\mu})} = \frac{19.23 \text{ mA/V}}{2\pi (2 \text{ pF} + 0.3 \text{ pF})} = 1.330 \text{ GHz} \quad (\text{Ans})$$



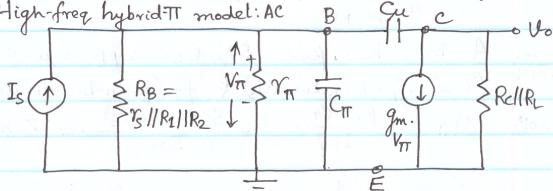Sol<sup>n</sup>. High-freq hybrid- $\pi$  model: AC



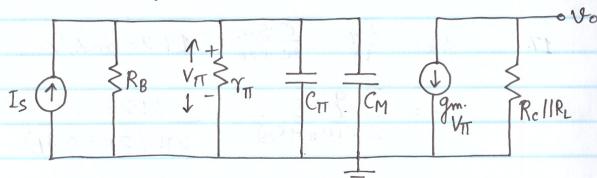(Note:  $R_E$  &  $C_E$  are shorted/ignored at high freq)  
Modified hybrid- $\pi$  model with  $C_M$  (Miller cap.) AC



$$R_{TH} = R_1 // R_2 = 200k // 220k = 104.8\text{ k}\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{220k}{200k + 220k} \cdot 5 = 2.619V$$

$$I_{BQ} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)R_E}$$

Draw the high-freq hybrid- $\pi$  ckt.

$$R_1 = 200k\Omega, R_2 = 220k\Omega,$$


$$R_C = 2.2k\Omega, R_E = 1k\Omega,$$

$$r_s = 100k\Omega, R_L = 4.7k\Omega,$$

$$V_{CC} = 5V, \beta_0 = 100, V_{BEon} = 0.7V,$$

$$V_A = \infty, C_B = 2pF, C_{\pi} = 10pF.$$

Find:  $C_M$  &  $f_{3db}$ .

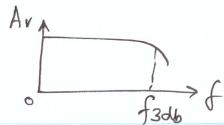

$$I_{CQ} = \beta \cdot I_{BQ} =$$

$$g_m = \frac{I_{CQ}}{V_T} =$$

$$\gamma_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}} =$$

$$C_M = C_B [1 + g_m (R_C // R_L)]$$

$$R_B = r_s // R_1 // R_2 =$$



$$f_{3db} = \frac{1}{2\pi(R_B // \gamma_{\pi})(C_{\pi} + C_M)}$$

$$\begin{matrix} \nearrow \\ \text{Ckt. BW} \\ \text{at high freq.} \end{matrix} =$$

(Ans)

(Ans)

TYU6.7  
(pg. 412)

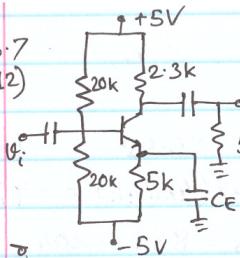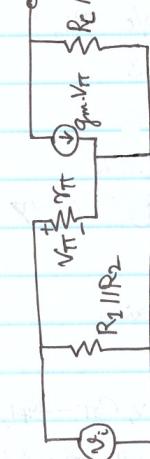

$$\beta = 125, V_{BE(on)} = 0.7V, V_A = 200V, \text{Find } R_o$$

$$R_{TH} = R_1 // R_2 = 10k\Omega$$

$$I_{BQ} = \frac{0 - 0.7 - (-5)}{10 + (125 \times 5)} = 6.72 \mu A$$

$$I_{CQ} = 125 \times 6.72 \mu A = 0.84 mA$$

$$r_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{125 \times 26 mV}{0.84 \mu A} = 3.87 k\Omega$$


$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.84 m}{0.026} = 32.3 mA/V$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.84 m} = 238 k\Omega$$

$$V_o = -q_m \cdot V_T (r_o // R_c // R_L) \quad \text{if } V_T = V_i$$

$$\therefore A_v = \frac{V_o}{V_i} = -q_m (r_o // R_c // R_L) = -(32.3)(238 k // 2.3 k // 5 k) \\ = -50.5 \quad (\text{Ans})$$
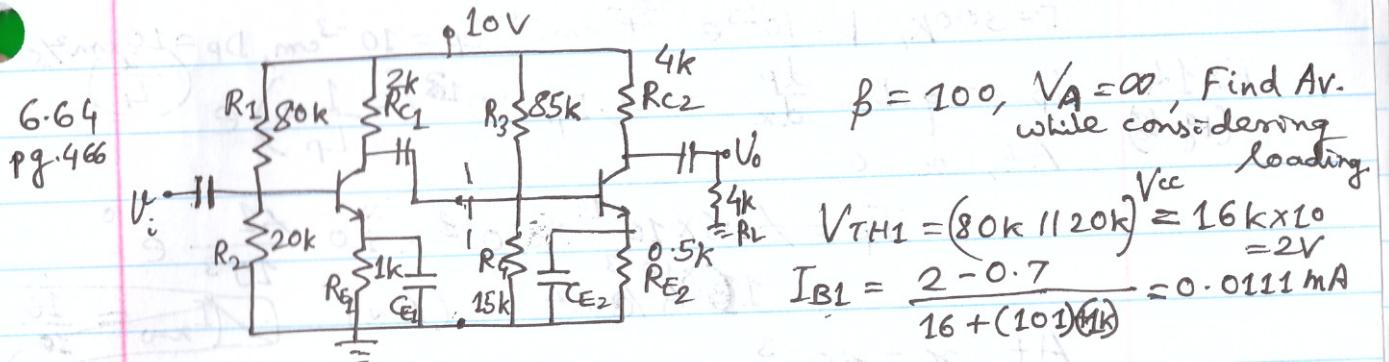
$$R_o = r_o // R_c = 238 k // 2.3 k = 2.28 k\Omega \quad (\text{Ans})$$



$\beta = 100, V_A = \infty$ , Find Av.  
while considering loading

$$V_{TH1} = (80k \parallel 20k) \frac{V_{cc}}{16k} = 2V$$

$$I_{B1} = \frac{2 - 0.7}{16 + (10k)(1k)} = 0.0111mA$$

$$I_{C1} = 100 \times 0.0111mA = 1.11mA$$

$$g_{m1} = \frac{I_{Cq}}{V_T} = \frac{1.11mA}{26m} = 42.74mA/V$$

$$\gamma_{\pi_1} = \frac{\beta \cdot V_T}{I_{Cq}} = \frac{100 \times 26m}{1.11mA} = 2.34k$$

$$\gamma_{o1} = \frac{V_A}{I_{Cq}} = \frac{\infty}{1.11mA} = \infty$$

$$V_{TH2} = (85k \parallel 15k) \frac{V_{cc}}{12.75k} = 1.5V$$

$$R_{TH2} = R_3 \parallel R_4 = 12.75k$$

$$I_{B2} = \frac{1.5 - 0.7}{12.75k + (10k)(0.5)} ; I_{C2} = 1.265mA ; g_{m2} = \frac{1.265mA}{0.026} = 48.65mA/V$$

$$\gamma_{\pi_2} = \frac{100 \times (0.026)}{1.265mA} = 2.06k ; \gamma_{o2} = \infty$$

$$Av_1 = -g_{m1} R_{C1} = -(42.7)(2) = -85.48 \quad (\text{w/o } R_{i_2})$$

$$Av_2 = -g_{m2} (R_{C2} \parallel R_L) = -(48.5)(4k \parallel 4k) = -97.3$$

$$Av = Av_1 \cdot Av_2 = 85.48 \times 97.3 = 8317.204$$

$$R_{i_2} = R_3 \parallel R_4 \parallel \gamma_{\pi_2} = 15k \parallel 85k \parallel 2.06k = 1.773k$$

$$Av'_1 = -g_{m1} (R_{C1} \parallel R_{i_2}) = -(42.7)(2k \parallel 1.773k) = -40.18$$

$$\therefore Av' = Av'_1 \cdot Av_2 = 40.17 \times 97.3 = 3909$$

$\therefore$  Loading of stage 2 reduces overall V-gain.