

$$i_i = \frac{0 - v_i}{R_i} = \frac{v_i - v_o}{R_f}$$


$$\Rightarrow v_o = + \left( 1 + \frac{R_f}{R_i} \right) v_i$$

$$\text{Gain (A}_v\text{)} = + \left( 1 + \frac{R_f}{R_i} \right)$$


$0^\circ$  phase shift

I/P resistance ( $R_i$ ) =  $\infty$  (or  $G \rightarrow 2$ )

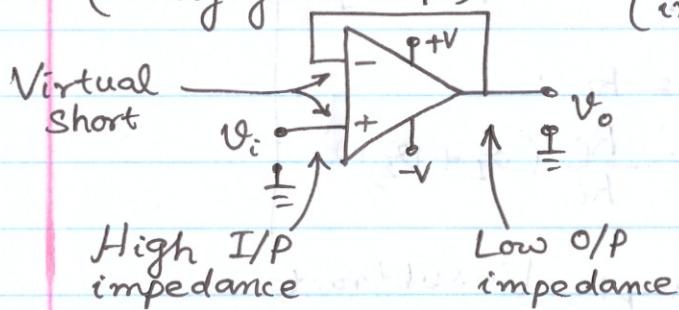→ Voltage follower: Special case of a non-inv. amp.  
(Unity-gain amp.) (impedance converter)




$$A_v = \frac{v_o}{v_i} = 1$$

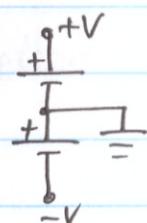

$$v_o = \left( 1 + \frac{R_f}{R_i} \right) v_i = \left( 1 + \frac{0}{\infty} \right) v_i = v_i$$

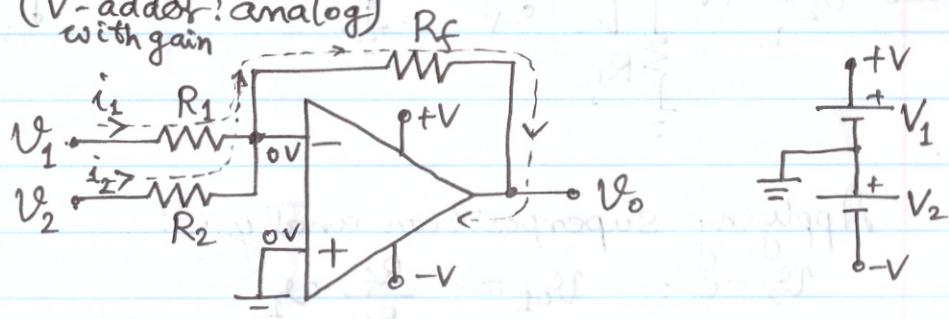iii) Summing amp: Special case of an inv. amp.  
(V-adder: analog with gain)



Analyze by using superposition system.

Assume,  $v_1$  is applied while  $v_2 = 0$

$$v_{o1} = -i_1 \cdot R_f = -\frac{R_f}{R_1} \cdot v_1$$

Assume,  $v_2$  is applied while  $v_1 = 0$

$$v_{o2} = -i_2 \cdot R_f = -\frac{R_f}{R_2} \cdot v_2$$

$$\therefore v_o = v_{o1} + v_{o2}$$


$$\Rightarrow v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2$$

$$\Rightarrow v_o = -\left[\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2\right]$$

If,  $R_1 = R_2 = R_i$ :

$$v_o = -\frac{R_f}{R_i} (v_1 + v_2)$$

iv) Difference amp: V-subtractor

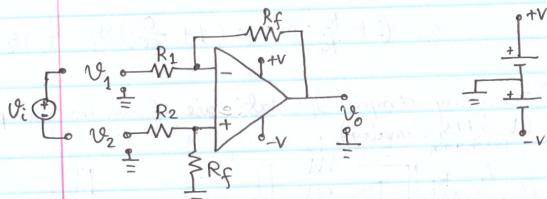

Applying superposition analysis:

$$v_2 = 0 : v_{o1} = -\frac{R_f}{R_1} v_1 \quad (\text{Inv. amp.})$$

$$v_1 = 0 : v_{o2} = \left[ \frac{R_f}{R_2 + R_f} \cdot v_2 \right] \left[ 1 + \frac{R_f}{R_1} \right] \quad (\text{Non-inv. amp.})$$

$$\Rightarrow v_{o2} = \left( 1 + \frac{R_f}{R_1} \right) \left[ \frac{\frac{R_f}{R_2 + R_f}}{1 + \frac{R_f}{R_1}} \right] v_2$$


$$v_o = v_{o1} + v_{o2} = -\frac{R_f}{R_1} v_1 + \left( 1 + \frac{R_f}{R_1} \right) \left[ \frac{\frac{R_f}{R_2 + R_f}}{1 + \frac{R_f}{R_1}} \right] v_2$$

$$\text{If, } R_1 = R_2 = R_i, \text{ or, } \frac{R_f}{R_1} = \frac{R_f}{R_2} = \frac{R_f}{R_i}$$


$$v_o = +\frac{R_f}{R_i} (v_2 - v_1)$$

Differential Gain  
I/P resistance =  $2 \cdot R_i = R_i$

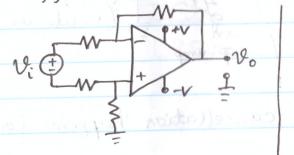Note: Differential I/P V may also be applied.



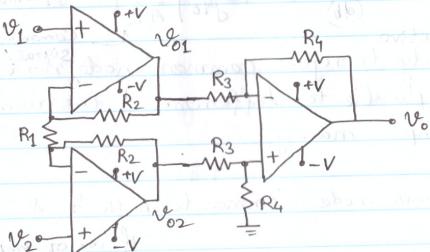
v) Instrumentation Amplifier: Special case of difference amp.



### Special Notes


#### 1. Virtual ground/Short:

i) Open loop analogy:

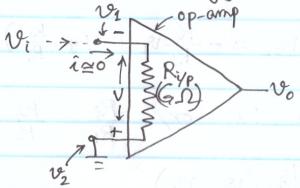

$$\begin{aligned} \text{If, } i &= 0, \quad R_{IP} = G_n \\ V &= V_2 - V_1 \\ &= i \cdot R_{IP} \\ &= 0 \cdot (G_n) \\ &= 0 \end{aligned}$$

ii) Closed loop analogy: Inv. amp.

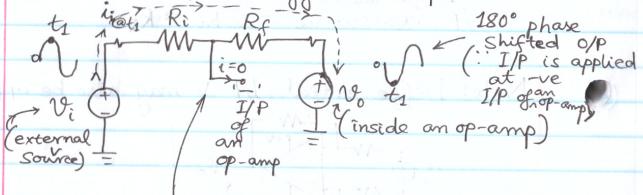

V-cancellation happens for  $V_i$  &  $V_0$


#### 2. Common Mode Rejection Ratio (CMRR):

$$\text{CMRR} = 20 \cdot \log_{10} \left| \frac{\text{Ad}}{\text{Acm}} \right| \quad \text{Differential gain}$$

Selective  
(Ability to reject common mode signal/noise)

Applicable to difference & instrumentation amps. mainly.

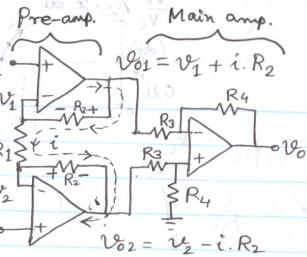Common mode: Common to both '+' & '-' inputs of an op-amp/op-amp ch.




$$V_{02} = V_1 + i \cdot R_2 = \left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2$$

$$V_{02} = V_2 - i \cdot R_2 = \left(1 + \frac{R_2}{R_1}\right) V_2 - \frac{R_2}{R_1} V_1$$


$$\text{Also, } V_0 = \frac{R_4}{R_3} (V_{02} - V_{01})$$

$$\Rightarrow V_0 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right) (V_2 - V_1) \quad \text{Differential gain}$$

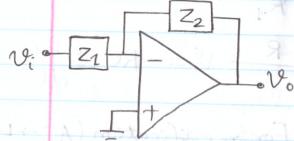vi) Integrator (LPF): Freq. dependent gain



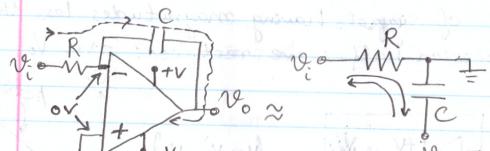
$$\frac{V_0}{V_i} = \pm \frac{Z_2}{Z_1}$$



$$\frac{V_0}{V_i} = -\frac{Z_2}{Z_1} V_i \quad \text{Phase inversion of } 180^\circ \text{ is independent of f}$$

$$X_C = \frac{1}{2\pi f C}$$

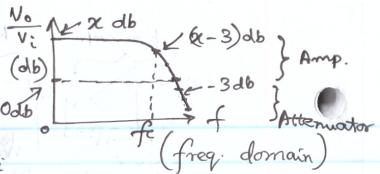

$$V_o = -\frac{1}{SRC} V_i$$


$$\Rightarrow V_o = V_i - \frac{1}{RC} \int_0^t V_i(t) dt \quad (\text{time domain})$$

Initial voltage across 'C' @  $t=0$

If,  $V_C = 0$  at  $t=0$ ;

$$V_o = -\frac{1}{RC} \int_0^t V_i(t) dt$$



vii) Differentiator: HPF

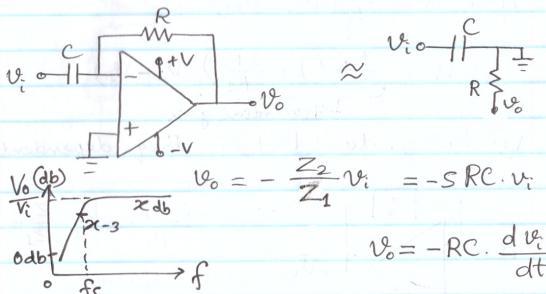


$$V_o = -RC \cdot \frac{dV_i(t)}{dt}$$

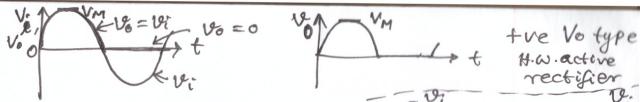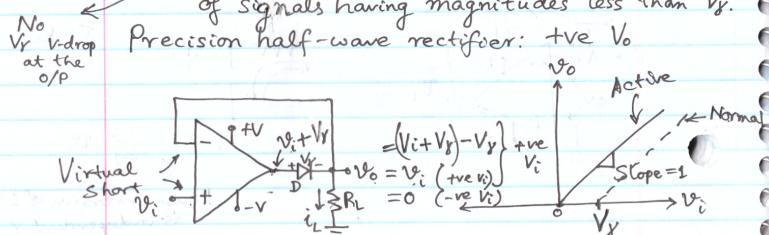viii) Active rectifiers: For rectification ( $AC \rightarrow DC$ ) of signals having magnitudes less than  $V_y$ .


Precision half-wave rectifier: +ve  $V_o$



-ve  $V_o$ :

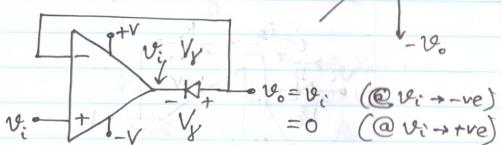

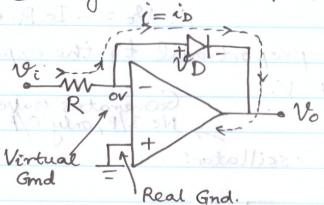ix) Logarithmic amplifier: Natural log computer



$$\text{Diode current eqn: } i_D = I_s (e^{\frac{V_D}{V_T}} - 1) \approx I_s e^{\frac{V_D}{V_T}}$$

(Under sufficient forward bias condition)

$$i_D = I_s e^{\frac{V_D}{V_T}} = \frac{V_o}{R}$$

$$\Rightarrow I_s e^{-\frac{V_o}{V_T}} = \frac{V_i}{R} \Rightarrow e^{-\frac{V_o}{V_T}} = \frac{V_i}{I_s R}$$


Taking natural log on both sides:

$$-\frac{V_o}{V_T} = \ln \left[ \frac{V_i}{I_s R} \right]$$

$$\Rightarrow V_o = -V_T \ln \left[ \frac{V_i}{I_s R} \right]$$

Note:  $\frac{V}{V_i}$  is proportional to natural log of I/P  $V$ .

x) Anti-log or exponential amp:

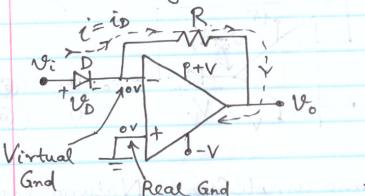

$$i_D \approx I_s \cdot e^{\frac{V_i}{V_T}}$$

$$= I_s \cdot e^{\frac{V_i}{kT}}$$

$$V_o = -i_D \cdot R$$


$$\Rightarrow V_o = -I_s \cdot e^{\frac{V_i}{kT}} \cdot R$$

$$\therefore V_o = -I_s \cdot R \cdot e^{\frac{V_i}{kT}}$$

Note: O/P V is proportional to the exponent of the I/P V.

Generates waveform  
No I/P, only O/P

x) Wein bridge oscillator:

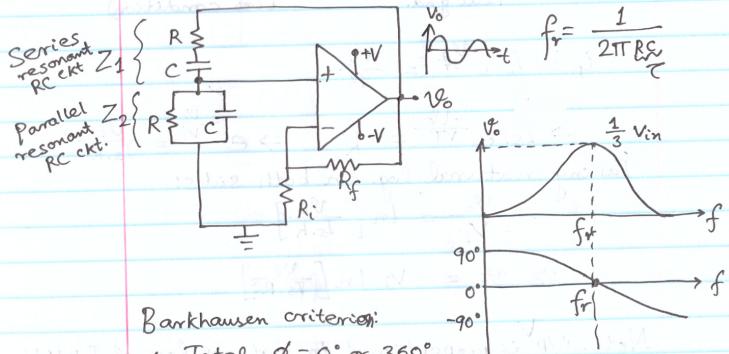


Barkhausen criterion:

1. Total  $\phi = 0^\circ$  or  $360^\circ$
2. +ve f.b. ( $|A_f| = 1$ )

$A_f$  Gain  
Feedback factor  
A combination of +ve f-b.  
-ve f.b.

xii) Comparator: Open-loop V-comparator.

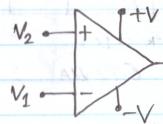

$$\text{If, } V_2 > V_1 \Rightarrow V_o = +V_{sat}$$

$$\text{If, } V_2 < V_1 \Rightarrow V_o = -V_{sat}$$

(assuming  $A_{od} = \infty$ )